
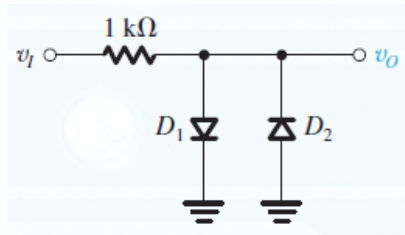


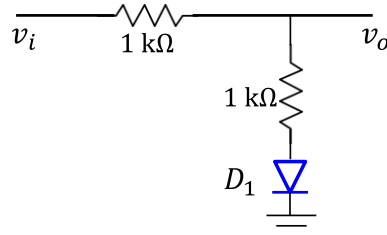


- [1] In each of the ideal-diode circuits shown in Fig. 1, v_i is a 10-kHz, 10-V peak sine wave. Sketch the waveform resulting at v_o . What are its positive and negative peak values?



(a)




(b)

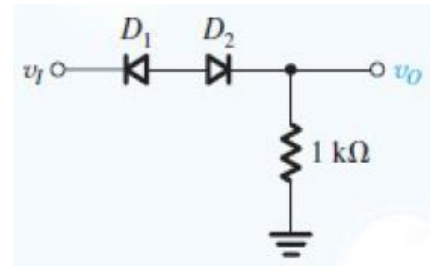


(c)

Fig. 1

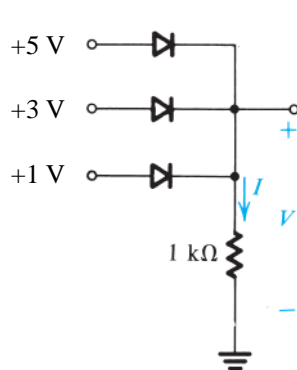- [2] Find the values of I and V in the circuits shown in Fig. 2. Use the Ideal diode model.



(a)

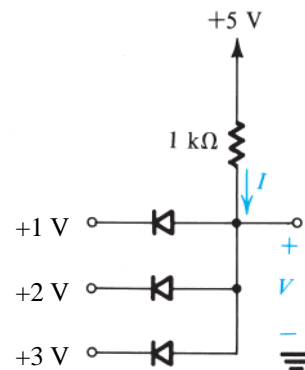

(b)

Fig. 2

- [3] A silicon junction diode has $v = 0.7$ V at $i = 1$ mA. Find the voltage drop at $i = 0.1$ mA and $i = 10$ mA.
- [4] Consider the diode circuit in Fig. 3 Obtain and plot the I_X - V_X characteristics of the circuit given below. Assume the diode is ideal and $R_1 = R_2 = 25$ k

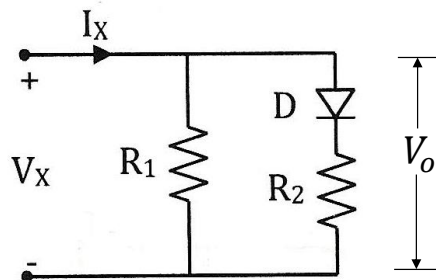


Fig. 3