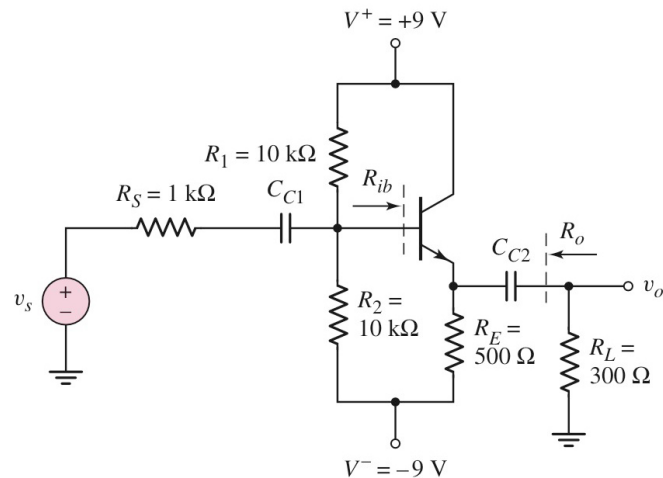




[1] The transistor parameters for the circuit in Figure 1 are $\beta = 180$ and $V_A = \infty$.

- (a) Find I_{CQ} and V_{CEQ} .
- (b) Calculate the small-signal voltage gain.
- (c) Determine the input and output resistances R_{ib} and R_o .



Solution:

(a) For dc analysis, the capacitors $CC1$ and $CC2$ act as *open circuit*.

$$V_{TH} = \frac{R_2}{R_1 + R_2} (V^+ - V^-) + V^- = \left(\frac{10}{10+10} \right) (18) + (-9) = 0 \text{ (V)}$$

$$R_{TH} = R_1 \parallel R_2 = \frac{(10)(10)}{10+10} = 5.0 \text{ (k}\Omega\text{)}$$

$$I_{BQ} = \frac{V_{TH} - V_{BE(on)} - V^-}{R_{TH} + (1 + \beta)R_E} = \frac{0 - 0.7 - (-9)}{5 + (181)(0.5)} = 86.91 \text{ (}\mu\text{A)}$$

$$I_{CQ} = \beta I_{BQ} = 15.644 \text{ (mA)}$$

$$I_{EQ} = (1 + \beta) I_{BQ} = 15.731 \text{ (mA)}$$

$$V_{CEQ} = V^+ - V^- - I_{EQ} R_E = 9 - (-9) - (15.731)(0.5) = 10.13 \text{ (V)}$$

(b) The small-signal parameters are:


$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(180)(0.026)}{15.644} = 0.299 \text{ (k}\Omega\text{)}$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{15.644}{0.026} = 601.692 \text{ (mA/V)}$$

$$r_o = \frac{V_A}{I_{CQ}} = \infty$$



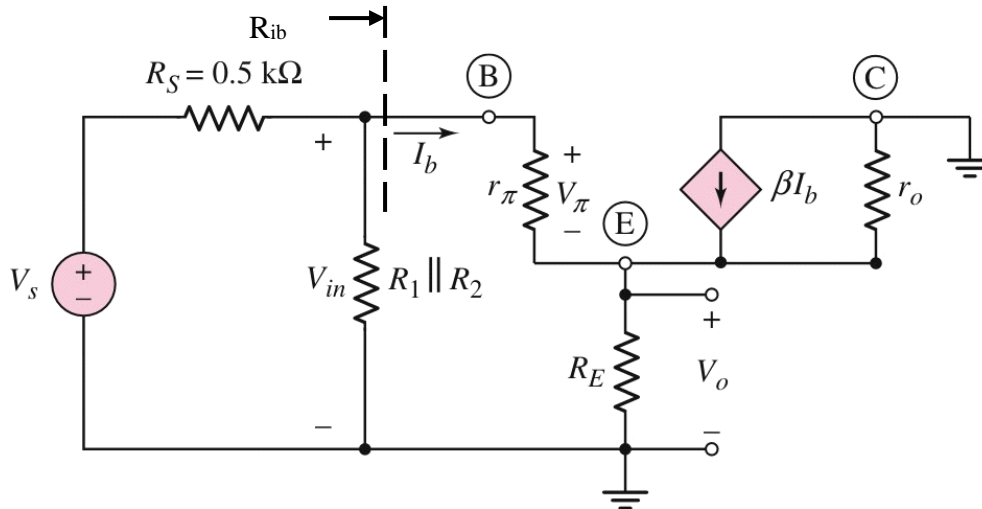The small-signal ac equivalent circuit becomes:



Copyright © The McGraw-Hill Companies, Inc.
 Permission required for reproduction or display.

$$v_o = (1 + \beta)i_b (R_E \parallel R_L)$$

$$\Rightarrow \frac{v_o}{i_b} = (1 + \beta)(R_E \parallel R_L) = (181)(0.1875) = 33.9375$$

$$v_b = V_\pi + v_o = i_b r_\pi + (1 + \beta)i_b (R_E \parallel R_L)$$

$$\Rightarrow \frac{v_b}{i_b} = R_{ib} = r_\pi + (1 + \beta)(R_E \parallel R_L) = 0.299 + 33.9375 = 34.2365$$

$$v_b = \frac{R_{ib} \parallel R_1 \parallel R_2}{R_S + R_{ib} \parallel R_1 \parallel R_2} v_s$$

$$\Rightarrow \frac{v_b}{v_s} = \frac{R_{ib} \parallel R_1 \parallel R_2}{R_S + R_{ib} \parallel R_1 \parallel R_2} = \frac{4.3628}{1 + 4.3628} = 0.8135$$

$$\frac{v_o}{v_s} = \frac{v_o}{i_b} \times \frac{i_b}{v_b} \times \frac{v_b}{v_s}$$

$$= (1 + \beta)(R_E \parallel R_L) \times \frac{1}{R_{ib}} \times \frac{R_{ib} \parallel R_1 \parallel R_2}{R_S + R_{ib} \parallel R_1 \parallel R_2}$$

$$= \frac{(1 + \beta)(R_E \parallel R_L)}{R_{ib}} \left(\frac{R_{ib} \parallel R_1 \parallel R_2}{R_S + R_{ib} \parallel R_1 \parallel R_2} \right)$$

$$= (33.9375) \left(\frac{1}{34.2365} \right) (0.8135) = 0.8064$$



(c) The input resistance R_{ib} is:

$$R_{ib} = r_{\pi} + (1 + \beta)(R_E \parallel R_L)$$

$$= 0.299 + 33.9375 = 34.24 \text{ (k}\Omega\text{)}$$

To calculate the output resistance R_o , the signal source v_s is short-circuited and the following equations can be written by KCL at node v_o and node v_b :

$$v_b = v_o + r_{\pi} i_b$$

$$\frac{v_b}{R_S \parallel R_1 \parallel R_2} + i_b = 0 \text{ (KCL at node } v_b\text{)}$$

$$\frac{v_o + r_{\pi} i_b}{R_S \parallel R_1 \parallel R_2} + i_b = 0 \Rightarrow \frac{v_o}{i_b} = - (r_{\pi} + R_S \parallel R_1 \parallel R_2)$$

$$i_o + (1 + \beta) i_b = \frac{v_o}{R_E} \text{ (KCL at node } v_o\text{)}$$

$$i_o - (1 + \beta) \left(\frac{v_o}{r_{\pi} + R_S \parallel R_1 \parallel R_2} \right) = \frac{v_o}{R_E}$$


$$\Rightarrow \frac{v_o}{i_o} = R_o = R_E \parallel \left(\frac{r_{\pi} + R_S \parallel R_1 \parallel R_2}{1 + \beta} \right) = 6.18 \text{ (}\Omega\text{)}$$

[2] For the transistor in Figure 2, the parameters are $\beta = 100$ and $V_A = \infty$.

(a) Design the circuit such that $I_{EQ} = 1 \text{ mA}$ and the Q-point is in the center of the dc load line.

(b) If the peak-to-peak sinusoidal output voltage is 4 V, determine the peak-to-peak sinusoidal signals at the base of the transistor and the peak-to-peak value of v_s .

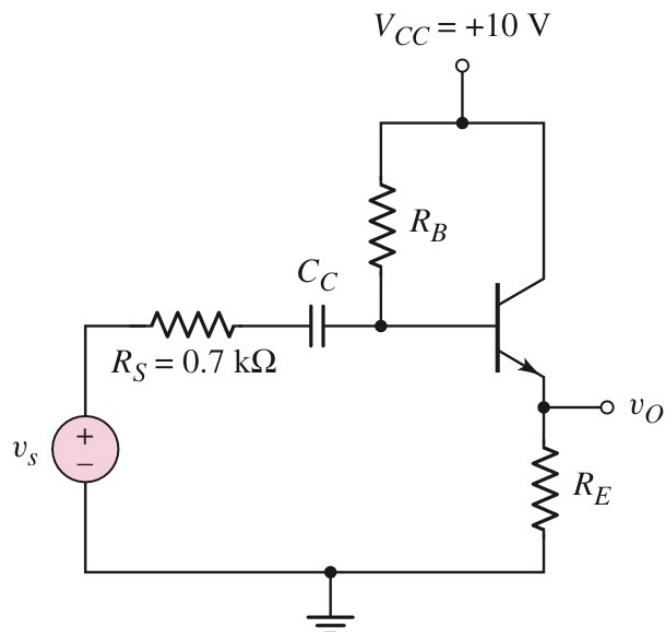(c) If the load resistor $R_L = 1 \text{ k}\Omega$ is connected to the output through a coupling capacitor, determine the peak-to-peak value in the output voltage, assuming v_s is equal to the value determined in part (b).





Solution:

(a) For dc analysis, the capacitor CC acts as *open circuit*.

$$V_{CC} = I_{BQ}R_B + V_{BE(\text{on})} + I_{EQ}R_E$$

$$= \left(\frac{R_B}{1+\beta} + R_E \right) I_{EQ} + V_{BE(\text{on})}$$

$$\frac{R_B}{101} + R_E = \frac{V_{CC} - V_{BE(\text{on})}}{I_{EQ}} = \frac{10 - 0.7}{1} = 9.3 \text{ (k}\Omega) \quad \dots(1)$$

$$V_{CC} = V_{CEQ} + I_{EQ}R_E \quad (V_{CEQ} = \frac{V_{CC}}{2} \text{ for } Q\text{-point is in the center of the dc load line})$$

$$10 = 5 + (1)R_E$$

$$R_E = 5 \text{ (k}\Omega) \quad \dots(2)$$

$$\Rightarrow R_B = (101)(9.3 - R_E) = 434.3 \text{ (k}\Omega)$$


$$I_{CQ} = \left(\frac{\beta}{1+\beta} \right) I_{EQ} = \left(\frac{100}{101} \right) (1) = 0.990 \text{ (mA)}$$

$$r_{\pi} = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{0.990} = 2.6263 \text{ (k}\Omega)$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.990}{0.026} = 38.0769 \text{ (mA/V)}$$

$$r_o = \frac{V_A}{I_{CQ}} = \infty$$

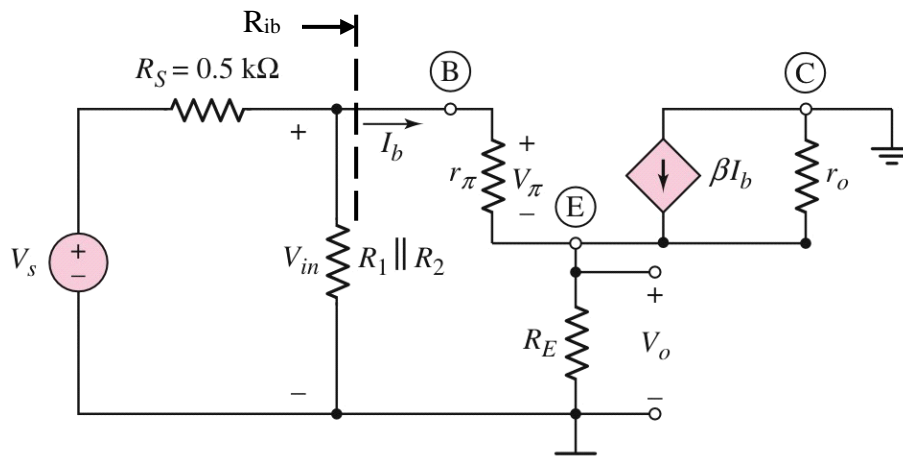(b) The small-signal ac equivalent circuit is given by:





$$v_o = (1 + \beta)R_E i_b$$

$$\Rightarrow \frac{v_o}{i_b} = (1 + \beta)R_E = (101)(5) = 505$$

$$v_b = V_\pi + v_o = i_b r_\pi + (1 + \beta)R_E i_b$$

$$\Rightarrow \frac{v_b}{i_b} = R_{ib} = r_\pi + (1 + \beta)R_E = 2.6263 + 505 = 507.6263$$

$$v_b = V_\pi + v_o = i_b r_\pi + (1 + \beta)R_E i_b$$

$$\Rightarrow \frac{v_b}{i_b} = R_{ib} = r_\pi + (1 + \beta)R_E = 2.6263 + 505 = 507.6263$$

$$v_b = \frac{R_B \parallel R_{ib}}{R_S + R_B \parallel R_{ib}} v_s$$

$$\Rightarrow \frac{v_b}{v_s} = \frac{R_B \parallel R_{ib}}{R_S + R_B \parallel R_{ib}} = \frac{234.0545}{0.7 + 234.0545} = 0.9970$$

$$\frac{v_b}{v_o} = \frac{v_b}{i_b} \times \frac{i_b}{v_o}$$

$$= \frac{r_\pi + (1 + \beta)R_E}{(1 + \beta)R_E}$$

$$= \frac{507.6263}{505} = 1.0052 \quad \dots(3)$$

$$\frac{v_o}{v_s} = \frac{v_o}{i_b} \times \frac{i_b}{v_b} \times \frac{v_b}{v_s}$$

$$= (1 + \beta)R_E \times \frac{1}{R_{ib}} \times \frac{R_B \parallel R_{ib}}{R_S + R_B \parallel R_{ib}}$$

$$= 505 \times \frac{1}{507.6263} \times 0.9970 = 0.9918 \quad \dots(4)$$

If the peak-to-peak output voltage $v_{o(\text{peak-peak})}$ is 4 V,

$$\text{Eq.(3)} \Rightarrow v_{b(\text{peak-peak})} = 1.0052 v_{o(\text{peak-peak})} = 4.021 \text{ (V)}$$

$$\text{Eq.(4)} \Rightarrow v_{s(\text{peak-peak})} = \frac{v_{o(\text{peak-peak})}}{0.9918} = 4.033 \text{ (V)}$$




(c) If the load resistor $R_L = 1 \text{ k}\Omega$ is added in parallel to R_E , Eq. (4) must be modified accordingly:

$$\begin{aligned} \frac{v_o}{v_s} &= \frac{(1 + \beta)(R_E \parallel R_L)}{r_\pi + (1 + \beta)(R_E \parallel R_L)} \left(\frac{R_B \parallel R_{ib}}{R_S + R_B \parallel R_{ib}} \right) \\ &= \frac{(101)(0.8333)}{2.6263 + (101)(0.8333)} (0.9970) = 0.9668 \\ \Rightarrow v_{o(\text{peak-peak})} &= 0.9668 v_{s(\text{peak-peak})} = (0.9668)(4.033) = 3.90 \text{ (V)} \end{aligned}$$

Therefore $v_{o(\text{peak-peak})}$ becomes smaller due to the loading effect by R_L .

[3] An emitter-follower amplifier, with the configuration shown in Figure 3, is to be designed such that an audio signal given by $v_s = 5 \sin(3000t) \text{ V}$ but with a source resistance of $R_S = 10 \text{ k}\Omega$ can drive a small speaker. Assume the supply voltages are $V_+ = +12 \text{ V}$ and $V_- = -12 \text{ V}$ and $\beta = 50$. The load, representing the speaker, is $R_L = 12 \text{ }\Omega$. The amplifier should be capable of delivering approximately 1 W of average power to the load. What is the signal power gain of your amplifier?

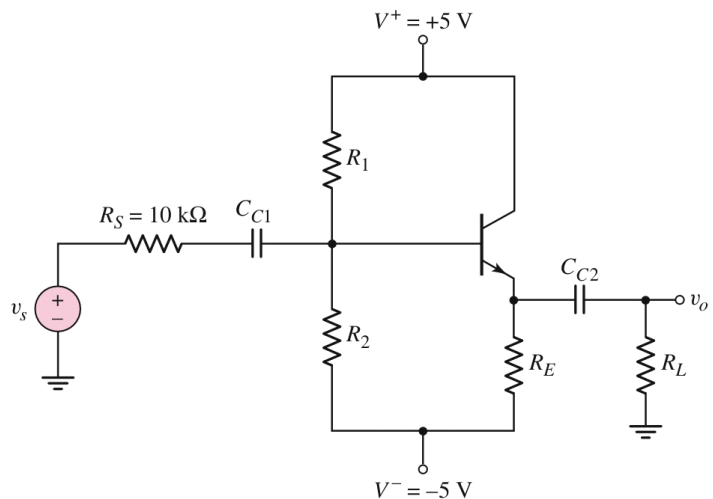

Solution:

To deliver 1 W of average power to the load, the peak-to-peak output voltage should be:

$$\begin{aligned} \frac{v_{o(\text{rms})}^2}{R_L} &= \frac{v_{o(\text{peak})}^2}{2R_L} = 1 \\ \Rightarrow v_{o(\text{peak})} &= 4.899 \text{ (V)} \\ \Rightarrow i_{o(\text{peak})} &= \frac{4.899}{12} = 0.408 \text{ (A)} \\ \Rightarrow v_{o(\text{peak-peak})} &= 9.798 \text{ (V)} \end{aligned}$$



The required voltage gain A_v is:

$$A_v = \frac{v_{o(peak)}}{v_{s(peak)}} = \frac{4.899}{5.0} = 0.9798$$


Choose $I_{EQ} = 0.8$ A and $V_{CEQ} = 12$ V,

$$R_E = \frac{V^+ - V^- - V_{CEQ}}{I_{EQ}} = \frac{12 - (-12) - 12}{0.8} = 15 \text{ } (\Omega)$$

$$R_{TH} = \frac{1}{10} (1 + \beta) R_E = \left(\frac{51}{10} \right) (15) = 76.5 \text{ } (\Omega) \text{ (for bias-stable circuit)}$$

$$\begin{aligned} V_{TH} &= V^- + I_{EQ} R_E + V_{BE(on)} + I_{BQ} R_{TH} \\ &= -12 + (0.8)(15) + 0.7 + \left(\frac{0.8}{51} \right) (76.5) = 1.9 \text{ (V)} \\ &= \frac{R_1}{R_1 + R_2} (V^+ - V^-) + V^- = \frac{1}{R_1} (R_1 \parallel R_2) (V^+ - V^-) + V^- \\ &\Rightarrow R_1 = 132 \text{ } (\Omega) \quad R_2 = 182 \text{ } (\Omega) \end{aligned}$$

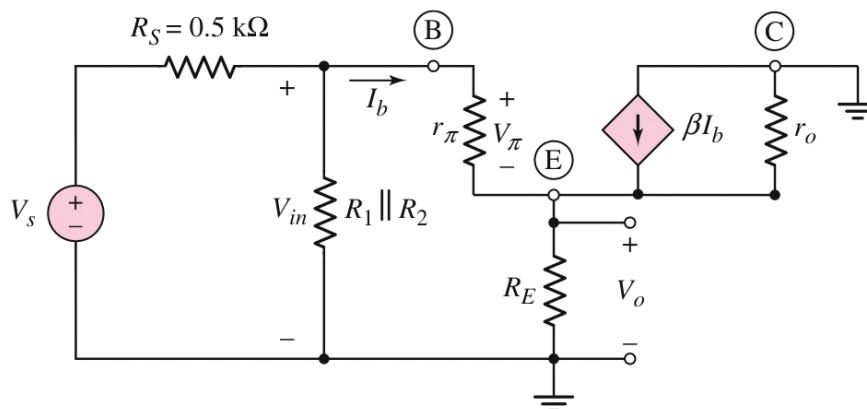The small-signal ac equivalent circuit is given by:



Choosing $I_{EQ} = 0.5$ A gives:

$$I_{CQ} = \frac{\beta}{1 + \beta} I_{EQ} = \left(\frac{50}{51} \right) (0.8) = 0.784 \text{ (A)}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(50)(0.026)}{0.784} = 1.658 \text{ } (\Omega)$$



The small-signal voltage gain is taken from Q.2 with some modifications:

$$\begin{aligned} \frac{v_o}{v_s} &= \frac{(1+\beta)(R_E \parallel R_L)}{r_\pi + (1+\beta)(R_E \parallel R_L)} \left(\frac{R_1 \parallel R_2 \parallel R_{ib}}{R_S + R_1 \parallel R_2 \parallel R_{ib}} \right) \\ &= \frac{(51)(6.667)}{1.658 + (51)(6.667)} \left(\frac{62.5116}{10 + 62.5116} \right) \\ &= 0.8579 \end{aligned}$$

Due to the presence of the source resistance R_S (loading effect) the required voltage gain of $A_v = 0.9798$ cannot be achieved. Note that $A_v = 0.9951$ if $R_S = 0$.

Therefore the maximum achievable peak output voltage is:

$$\frac{v_{o(peak)}}{v_{s(peak)}} = 0.8579 \Rightarrow v_{o(peak)} = 4.290 \text{ (V)}$$

Hence the output power delivered to the load R_L is:

$$P_L = \frac{v_{o(peak)}^2}{2R_L} = 0.767 \text{ (W)}$$

The input power delivered by the signal source v_s is:

$$\begin{aligned} P_S &= v_{s(rms)} i_{s(rms)} \\ i_{s(rms)} &= \frac{v_{s(rms)}}{R_i} = \frac{v_{s(rms)}}{R_S + R_1 \parallel R_2 \parallel R_{ib}} = \frac{5/\sqrt{2}}{10 + 62.5116} = 48.758 \text{ (mA)} \\ \Rightarrow P_S &= v_{s(rms)} i_{s(rms)} = \left(\frac{5}{\sqrt{2}} \right) (48.758) = 172.386 \text{ (mW)} \end{aligned}$$

Hence the signal power gain of the amplifier is:

$$G_{power} = \frac{P_L}{P_S} = \frac{0.767}{172.386 \times 10^{-3}} = 4.45$$