



- Answer all the following question
- Illustrate your answers with sketches when necessary.
- The exam. Consists of two pages
- No. of questions : 4
- Total Mark: 100 Marks
- The first Page – 50 Marks

1.a) For the circuit shown in Fig. 1 , Find V_1 and V_2 . **(8 marks)**

1.b) In Fig. 2 , use the Superposition Theorem to find the current I . **(10 marks)**

1.c) For the circuit shown in Fig. 3, Find: 1- The value of R_L to be connected between a and b to obtain the maximum power dissipated in it **(8 marks)**
2- The value of this maximum power **(2 marks)**
3- The value of R_L to obtain half of the maximum power . **(2 marks)**

2) For the circuit shown in Fig. 4, Find: **(20 marks)**
1- The total impedance 2- The supply current 3- The current in R_2
4- The voltage across R_2 5- The power factor 6- The total active power, reactive power and apparent power 7- Draw the phasor, impedance and the power diagrams for the total equivalent circuit

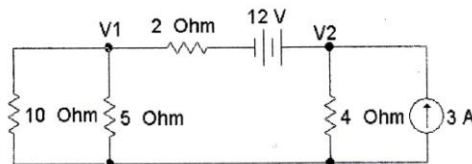


Fig. 1

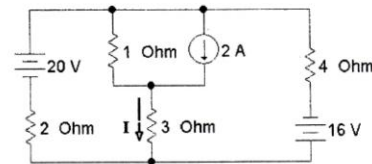


Fig. 2

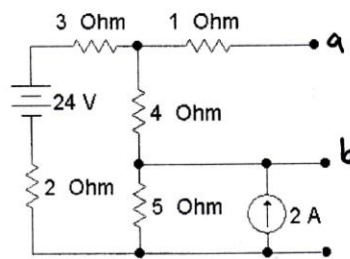


Fig 3

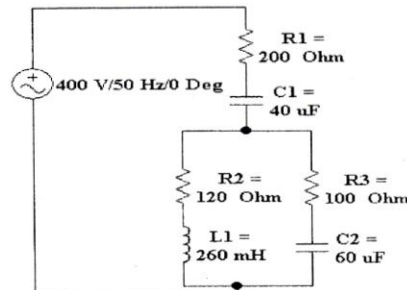


Fig. 4

Good Luck &

Prof. Dr. M. Moenes

Please Turn over the Page