Benha University Faculty of Engineering (Shoubra) Electrical Engineering Department 3<sup>rd</sup> year Electrical Power



Electrical Machines (2)(EPE312) 1<sup>st</sup> Semester 2013/2014 Midterm Exam Time: 1hr

**[1]** Explain briefly, the construction and principle of operation of the three phase synchronous generator.

[2] A 3-phase, star-connected alternator has an armature resistance of 0.1 ohm per phase and a synchronous reactance 0.66 ohm per phase. Calculate the line value of the no load voltage, $E_0$ , when the alternator supplies a load of 5 MW at terminal voltage 11 kV at a load power factor of (a) unity (b) 0.8 lagging and (c) 0.8 leading. Also draw the phasor diagram in each case.

Benha University Faculty of Engineering (Shoubra) Electrical Engineering Department 3<sup>rd</sup> year Electrical Power



Electrical Machines (2)(EPE312) 1<sup>st</sup> Semester 2013/2014 Midterm Exam Time: 1hr

**[1]** Explain briefly, the construction and principle of operation of the three phase synchronous generator.

[2] A 3-phase, star-connected alternator has an armature resistance of 0.1 ohm per phase and a synchronous reactance 0.66 ohm per phase. Calculate the line value of the no load voltage, $E_0$ , when the alternator supplies a load of 5 MW at terminal voltage 11 kV at a load power factor of (a) unity (b) 0.8 lagging and (c) 0.8 leading. Also draw the phasor diagram in each case.

Benha University Faculty of Engineering (Shoubra) Electrical Engineering Department 3<sup>rd</sup> year Electrical Power



Electrical Machines (2)(EPE312) 1<sup>st</sup> Semester 2013/2014 Midterm Exam Time: 1hr

**[1]** Explain briefly, the construction and principle of operation of the three phase synchronous generator.

[2] A 3-phase, star-connected alternator has an armature resistance of 0.1 ohm per phase and a synchronous reactance 0.66 ohm per phase. Calculate the line value of the no load voltage, $E_0$ , when the alternator supplies a load of 5 MW at terminal voltage 11 kV at a load power factor of (a) unity (b) 0.8 lagging and (c) 0.8 leading. Also draw the phasor diagram in each case.