

# *Transmission and Distribution of Electrical Power*



By



*Associate Prof. / Mohamed Ahmed Ebrahim Mohamed*

E-mail: [mohamedahmed\\_en@yahoo.com](mailto:mohamedahmed_en@yahoo.com)

[mohamed.mohamed@feng.bu.edu.eg](mailto:mohamed.mohamed@feng.bu.edu.eg)

Web site: <http://bu.edu.eg/staff/mohamedmohamed033>





# *Lecture (3)*



# Contents

- Chapter 1:  
Transmission Line Constants
- Chapter 2:  
Transmission Line Models and Calculations
- Chapter 3:  
Mechanical Design of Overhead T.L
- Chapter 4:  
D.C. power Transmission Technology

# Chapter 2:

## Transmission Line Models and Calculations


- Classification of transmission lines according to line length:
  - Short transmission line  $\leq 80$  Km
  - Medium transmission line 80 : 240 Km
  - Long transmission line  $\geq 240$  Km

# Chapter 2:


## Transmission Line Models and Calculations

- Classification of transmission lines according to line length:
  - Short transmission line  $\leq 80$  Km
  - Medium transmission line 80 : 240 Km
  - Long transmission line  $\geq 240$  Km

# Long Transmission Line Representation

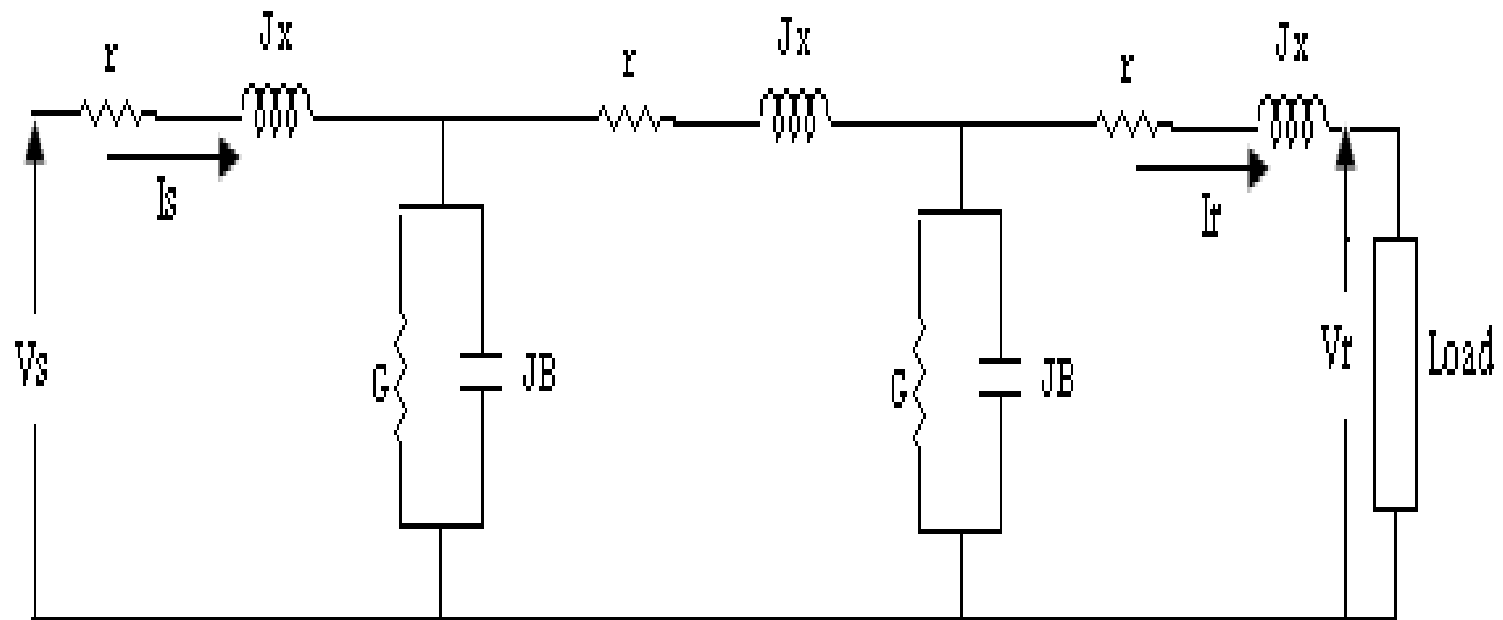

# Continue

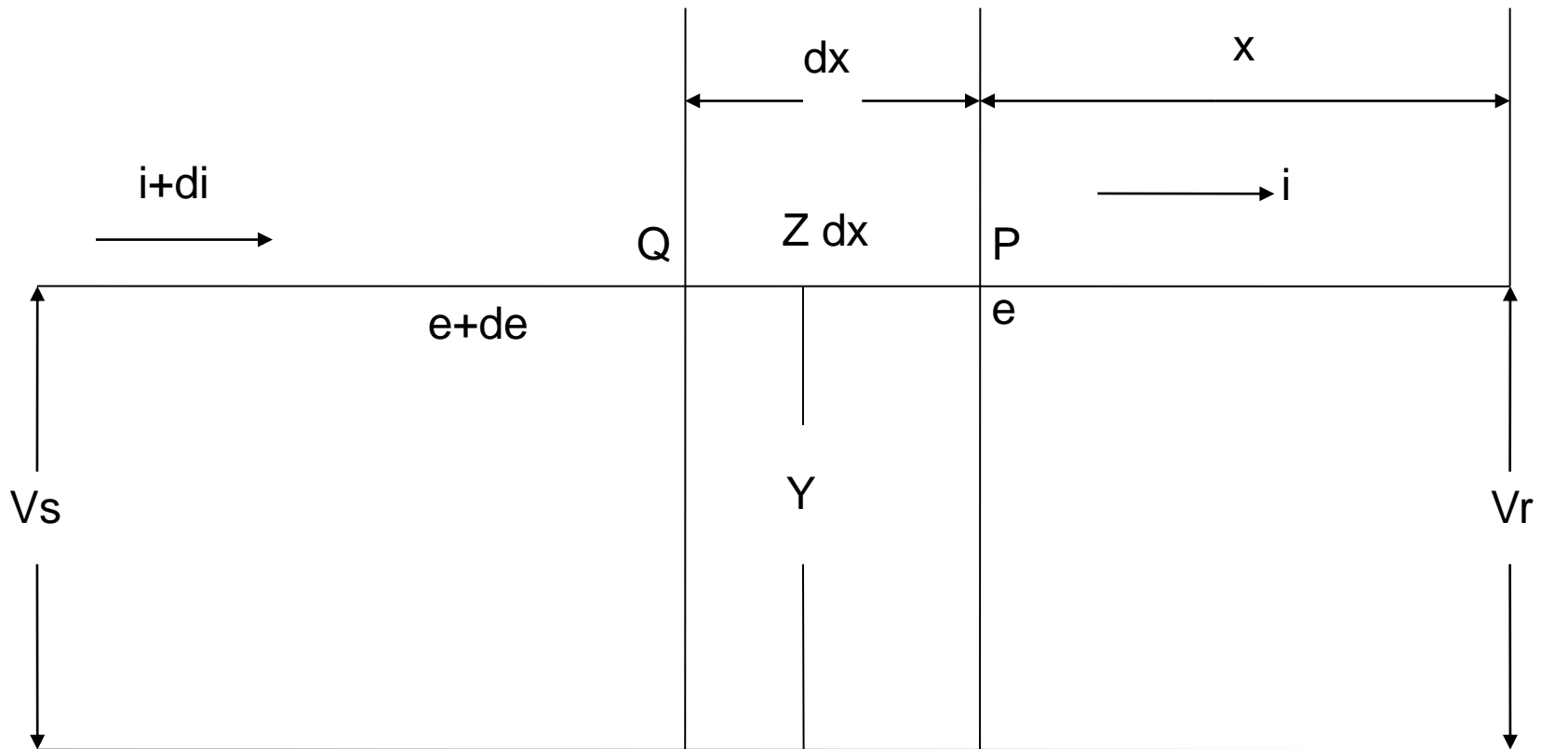

# Continue

$$e + de = e + izdx$$

$$\frac{de}{dx} = iz$$

*also, i + di = i + eydx*

$$\frac{di}{dx} = ey$$

$$\frac{d^2 e}{dx^2} = \frac{di}{dx} z$$

$$= eyz = \alpha^2 e$$



# Continue

Where  $\alpha$  : Propagation const. =  $\sqrt{zy}$

also,

$$\begin{aligned}\frac{d^2 i}{dx^2} &= \frac{de}{dx} y \\ &= izy \\ &= i\alpha^2\end{aligned}$$

solving the two second order differential equations yields,

$$e = A \cosh \alpha x + B \sinh \alpha x$$

$$i = C \cosh \alpha x + D \sinh \alpha x$$

# Continue

Using the receiving end condition yields,

$$e = V_r \cosh \alpha x + I_r Z_o \sinh \alpha x$$

$$i = \frac{V_r}{Z_o} \sinh \alpha x + I_r \cosh \alpha x$$

*Hence,*

$$e_s = V_r \cosh \alpha x + I_r \frac{Z}{\theta} \sinh \alpha x$$

$$i_s = V_r \frac{Y}{\theta} \sinh \alpha x + I_r \cosh \alpha x$$

# Continue

Hence,

$$A = \cosh \theta$$

$$B = Z \frac{\sinh \theta}{\theta}$$

$$C = Y \frac{\sinh \theta}{\theta}$$

$$D = \cosh \theta$$

$$V_s = A V_r + B I_r$$

$$I_s = C V_r + D I_r$$

In matrix form,

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix}$$

# Medium T.L Solution by nominal $\pi$ -Method


$$V_s = V_r + I_l Z$$

$$I_l = V_r \frac{Y}{2} + I_r$$


$$V_s = V_r + \left( V_r \frac{Y}{2} + I_r \right) Z$$

$$V_s = \left( 1 + \frac{YZ}{2} \right) V_r + Z I_r$$

$$I_s = I_l + V_s \frac{Y}{2}$$

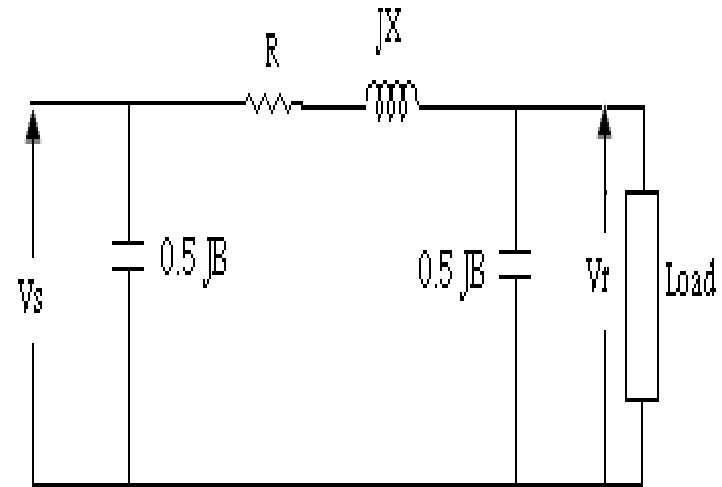

# Continue

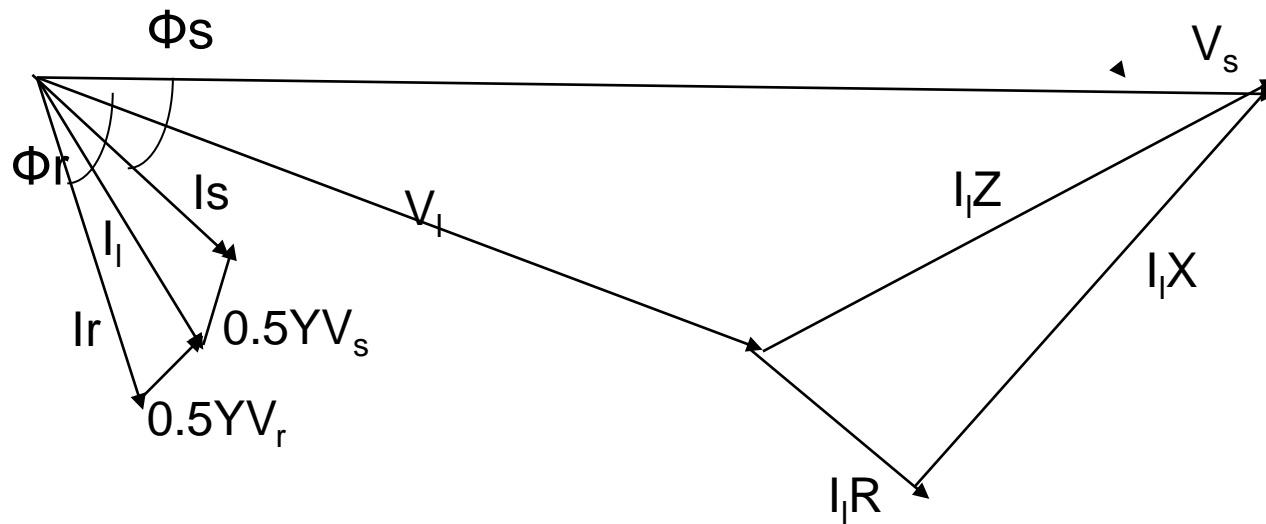

# Continue

$$I_s = V_r \frac{Y}{2} + I_r + \frac{Y}{2} \left[ \left( 1 + \frac{YZ}{2} \right) V_r + Z I_r \right]$$

$$= Y \left( 1 + \frac{YZ}{4} \right) V_r + \left( 1 + \frac{YZ}{2} \right) I_r$$

$$A = D = 1 + \frac{ZY}{2}$$

$$B = Z$$

$$C = Y \left( 1 + \frac{YZ}{4} \right)$$

# Medium T.L Solution by Nominal T-Method



$$V_s = V_c + I_s \frac{Z}{2}$$

$$V_c = V_r + I_r \frac{Z}{2}$$

$$I_s = I_c + I_r$$
$$= V_c Y + I_r$$

$$I_s = (V_r + I_r \frac{Z}{2}) y + I_r$$

# Continue

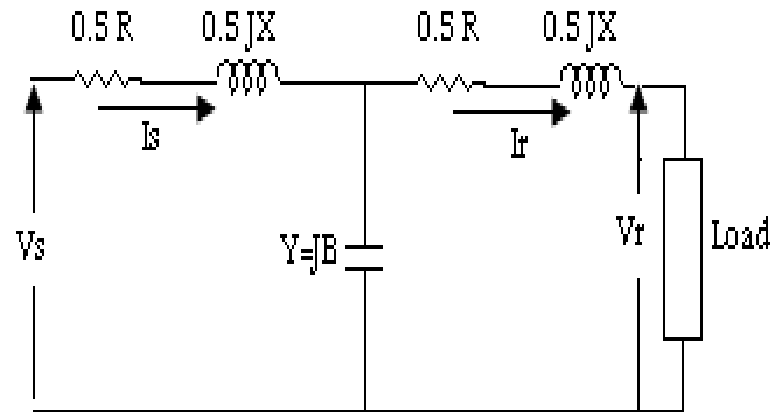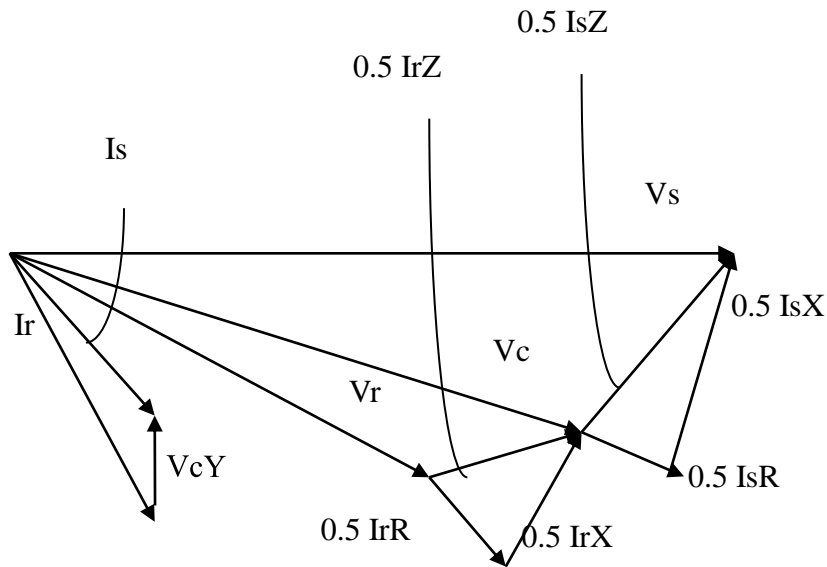



# Continue

$$I_s = YV_r + \left(1 + \frac{YZ}{2}\right)I_r$$

$$V_s = V_r + I_r \frac{Z}{2} + \frac{Z}{2} \left[ YV_r + \left(1 + \frac{YZ}{2}\right)I_r \right]$$

$$V_s = \left(1 + \frac{YZ}{2}\right)V_r + \left(1 + \frac{YZ}{4}\right)ZI_r$$

$$A = D = 1 + \frac{YZ}{2} \qquad B = Z \left(1 + \frac{YZ}{4}\right) \qquad C = Y$$

# Short Transmission Line Representation

$$A = D = 1 + \frac{YZ}{2} + \frac{(YZ)^2}{24} + \dots$$

$$B = Z \left[ 1 + \frac{YZ}{6} + \frac{(YZ)^2}{120} + \dots \right]$$



$$C = Y \left[ 1 + \frac{YZ}{6} + \frac{(YZ)^2}{120} + \dots \right]$$

$C = 0$  Because  $y = 0$

also,  $A = D = 1$ , and  $B = Z$

$$\begin{bmatrix} V_s \\ I_s \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_r \\ I_r \end{bmatrix}$$

# Continue

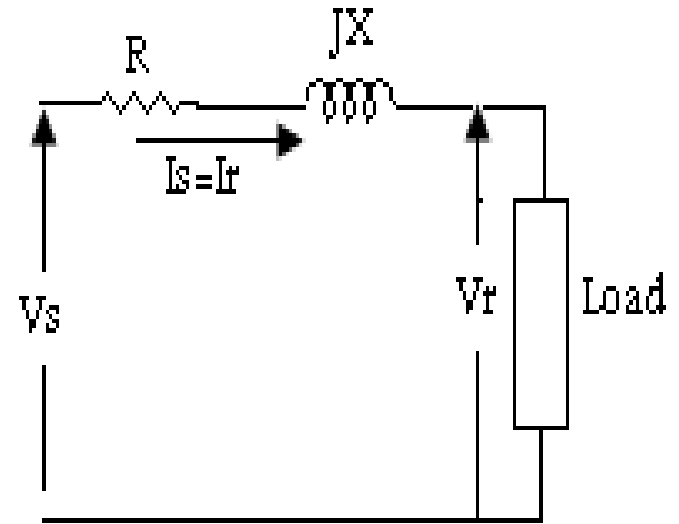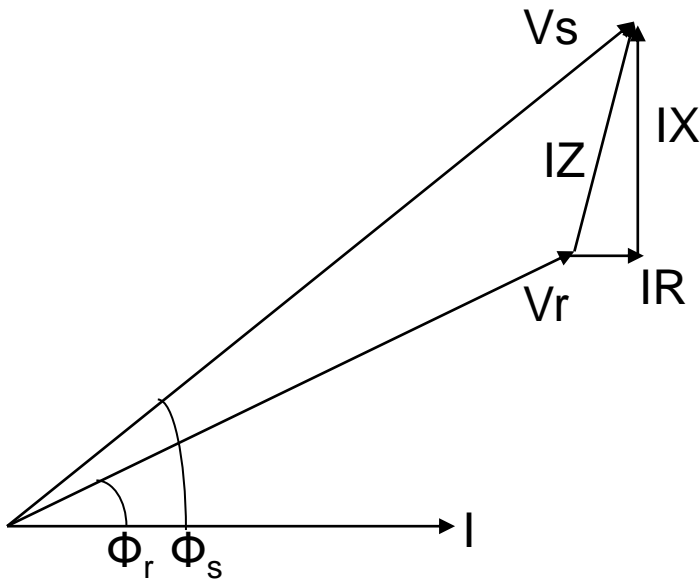

# Notes

$$P_r = 3 V_r I \cos\varphi_r$$

$$I = I_r = I_s$$

$$P_s = 3 V_s I \cos\varphi_s$$

$$\eta = \frac{P_r}{P_s} = \frac{V_r \cos\varphi_r}{V_s \cos\varphi_s}$$

## Solved Examples to Evaluate the Different Types of Transmission Lines

**Example 1** *A single phase overhead transmission line delivers 1100 kW at 33 kV at 0.8 p.f. lagging. The total resistance and inductive reactance of the line are 10  $\Omega$  and 15  $\Omega$  respectively. Determine : (i) sending end voltage (ii) sending end power factor and (iii) transmission efficiency.*

### Solution.

Load power factor,  $\cos \phi_R = 0.8$  lagging

Total line impedance,  $\vec{Z} = R + jX_L = 10 + j15$

Receiving end voltage,  $V_R = 33 \text{ kV} = 33,000 \text{ V}$

$$\text{Line current, } I = \frac{kW \times 10^3}{V_R \cos \phi_R} = \frac{1100 \times 10^3}{33,000 \times 0.8} = 41.67 \text{ A}$$

$$\text{As } \cos \phi_R = 0.8 \quad \therefore \quad \sin \phi_R = 0.6$$

---

# Performance of Single Phase Short Transmission Lines

$$\vec{V}_R = V_R + j 0 = 33000 \text{ V}$$

$$\begin{aligned} \vec{I} &= I (\cos \phi_R - j \sin \phi_R) \\ &= 41.67 (0.8 - j 0.6) = 33.33 - j 25 \end{aligned}$$

(i) Sending end voltage,  $\vec{V}_S = \vec{V}_R + \vec{I} Z$

$$\begin{aligned} &= 33,000 + (33.33 - j 25 \cdot 0) (10 + j 15) \\ &= 33,000 + 333.3 - j 250 + j 500 + 375 \\ &= 33,708.3 + j 250 \end{aligned}$$

$\therefore$  Magnitude of  $V_S = \sqrt{(33,708.3)^2 + (250)^2} = 33,709 \text{ V}$

(ii) Angle between  $\vec{V}_S$  and  $\vec{V}_R$  is

$$\alpha = \tan^{-1} \frac{250}{33,708.3} = \tan^{-1} 0.0074 = 0.42^\circ$$

∴ Sending end power factor angle is

$$\phi_S = \phi_R + \alpha = 36.87^\circ + 0.42^\circ = 37.29^\circ$$

∴ Sending end p.f.,  $\cos \phi_S = \cos 37.29^\circ = \mathbf{0.7956 \text{ lagging}}$

(iii) Line losses =  $I^2 R = (41.67)^2 \times 10 = 17,364 \text{ W} = 17.364 \text{ kW}$

Output delivered = 1100 kW

Power sent =  $1100 + 17.364 = 1117.364 \text{ kW}$

∴ Transmission efficiency =  $\frac{\text{Power delivered}}{\text{Power sent}} \times 100 = \frac{1100}{1117.364} \times 100 = \mathbf{98.44\%}$

**Note.**  $V_S$  and  $\phi_S$  can also be calculated as follows :

$$V_S = V_R + IR \cos \phi_R + IX_L \sin \phi_R \text{ (approximately)}$$

$$= 33,000 + 41.67 \times 10 \times 0.8 + 41.67 \times 15 \times 0.6$$

$$= 33,000 + 333.36 + 375.03$$

$$= 33708.39 \text{ V which is approximately the same as above}$$

$$\cos \phi_S = \frac{V_R \cos \phi_R + IR}{V_S} = \frac{33,000 \times 0.8 + 41.67 \times 10}{33,708.39} = \frac{26,816.7}{33,708.39}$$

$$= 0.7958$$



# Medium Transmission Lines

**Example 2** A (medium) single phase transmission line 100 km long has the following constants :

$$\text{Resistance/km} = 0.25 \Omega ;$$

$$\text{Reactance/km} = 0.8 \Omega$$

$$\text{Susceptance/km} = 14 \times 10^{-6} \text{ siemen} ;$$

$$\text{Receiving end line voltage} = 66,000 \text{ V}$$

Assuming that the total capacitance of the line is localised at the receiving end alone, determine (i) the sending end current (ii) the sending end voltage (iii) regulation and (iv) supply power factor. The line is delivering 15,000 kW at 0.8 power factor lagging. Draw the phasor diagram to illustrate your calculations.

# Medium Transmission Lines

Total resistance,  $R = 0.25 \times 100 = 25 \Omega$

Total reactance,  $X_L = 0.8 \times 100 = 80 \Omega$

Total susceptance,  $Y = 14 \times 10^{-6} \times 100 = 14 \times 10^{-4} S$

Receiving end voltage,  $V_R = 66,000 V$

$\therefore$  Load current,  $I_R = \frac{15,000 \times 10^3}{66,000 \times 0.8} = 284 A$

$$\cos \phi_R = 0.8 ; \quad \sin \phi_R = 0.6$$

Taking receiving end voltage as the reference phasor [see Fig.10.10 (ii)], we have,

$$\vec{V}_R = V_R + j0 = 66,000V$$

Load current,  $\vec{I}_R = I_R (\cos \phi_R - j \sin \phi_R) = 284 (0.8 - j 0.6) = 227 - j 170$

# Medium Transmission Lines

Capacitive current,  $\vec{I}_C = jY \times V_R = j 14 \times 10^{-4} \times 66000 = j 92$

(i) Sending end current,  $\vec{I}_S = \vec{I}_R + \vec{I}_C = (227 - j 170) + j 92$   
 $= 227 - j 78$  ... (i)

Magnitude of  $I_S = \sqrt{(227)^2 + (78)^2} = 240 \text{ A}$

(ii) Voltage drop  $= \vec{I}_S \vec{Z} = \vec{I}_S (R + j X_L) = (227 - j 78) (25 + j 80)$   
 $= 5,675 + j 18,160 - j 1950 + 6240$   
 $= 11,915 + j 16,210$

Sending end voltage,  $\vec{V}_S = \vec{V}_R + \vec{I}_S \vec{Z} = 66,000 + 11,915 + j 16,210$   
 $= 77,915 + j 16,210$  ... (ii)

Magnitude of  $V_S = \sqrt{(77915)^2 + (16210)^2} = 79583 \text{ V}$

# Medium Transmission Lines

(iii) % Voltage regulation  $= \frac{V_S - V_R}{V_R} \times 100 = \frac{79,583 - 66,000}{66,000} \times 100 = 20.58\%$

(iv) Referring to exp. (i), phase angle between  $\vec{V}_R$  and  $\vec{I}_S$  is :

$$\theta_1 = \tan^{-1} -78/227 = \tan^{-1} (-0.3436) = -18.96^\circ$$

Referring to exp. (ii), phase angle between  $\vec{V}_R$  and  $\vec{V}_S$  is :

$$\theta_2 = \tan^{-1} \frac{16210}{77915} = \tan^{-1} (0.2036) = 11.50^\circ$$

$\therefore$  Supply power factor angle,  $\phi_S = 18.96^\circ + 11.50^\circ = 30.46^\circ$

$\therefore$  Supply p.f. =  $\cos \phi_S = \cos 30.46^\circ = 0.86 \text{ lag}$

# Long Transmission Lines

**Example 3** A 3- $\phi$  transmission line 200 km long has the following constants :

$$\text{Resistance/phase/km} = 0.16 \Omega$$

$$\text{Reactance/phase/km} = 0.25 \Omega$$

$$\text{Shunt admittance/phase/km} = 1.5 \times 10^{-6} \text{ S}$$

Calculate by rigorous method the sending end voltage and current when the line is delivering a load of 20 MW at 0.8 p.f. lagging. The receiving end voltage is kept constant at 110 kV.

**Solution :**

$$\text{Total resistance/phase, } R = 0.16 \times 200 = 32 \Omega$$

$$\text{Total reactance/phase, } X_L = 0.25 \times 200 = 50 \Omega$$

$$\text{Total shunt admittance/phase, } Y = j 1.5 \times 10^{-6} \times 200 = 0.0003 \angle 90^\circ$$

$$\text{Series Impedance/phase, } Z = R + j X_L = 32 + j 50 = 59.4 \angle 58^\circ$$

# Long Transmission Lines

The sending end voltage  $V_S$  per phase is given by :

$$V_S = V_R \cosh \sqrt{Y Z} + I_R \sqrt{\frac{Z}{Y}} \sinh \sqrt{Z Y} \quad \dots(i)$$

Now

$$\sqrt{Z Y} = \sqrt{59 \cdot 4 \angle 58^\circ \times 0 \cdot 0003 \angle 90^\circ} = 0 \cdot 133 \angle 74^\circ$$

$$Z Y = 0 \cdot 0178 \angle 148^\circ$$

$$Z^2 Y^2 = 0 \cdot 00032 \angle 296^\circ$$

$$\sqrt{\frac{Z}{Y}} = \sqrt{\frac{59 \cdot 4 \angle 58^\circ}{0 \cdot 0003 \angle 90^\circ}} = 445 \angle -16^\circ$$

$$\sqrt{\frac{Y}{Z}} = \sqrt{\frac{0 \cdot 0003 \angle 90^\circ}{59 \cdot 4 \angle 58^\circ}} = 0 \cdot 00224 \angle 16^\circ$$

$$\begin{aligned} \therefore \cosh \sqrt{Y Z} &= 1 + \frac{Z Y}{2} + \frac{Z^2 Y^2}{24} \text{ approximately} \\ &= 1 + \frac{0 \cdot 0178 \angle 148^\circ}{2} + \frac{0 \cdot 00032 \angle 296^\circ}{24} \\ &= 1 + 0 \cdot 0089 \angle 148^\circ + 0 \cdot 0000133 \angle 296^\circ \\ &= 1 + 0 \cdot 0089 (-0 \cdot 848 + j 0 \cdot 529) + 0 \cdot 0000133 (0 \cdot 438 - j 0 \cdot 9) \\ &= 0 \cdot 992 + j 0 \cdot 00469 = 0 \cdot 992 \angle 0 \cdot 26^\circ \end{aligned}$$

# Long Transmission Lines

$$\begin{aligned}\sinh \sqrt{Y Z} &= \sqrt{Y Z} + \frac{(Y Z)^{3/2}}{6} \text{ approximately} \\ &= 0.133 \angle 74^\circ + \frac{0.0024 \angle 222^\circ}{6} \\ &= 0.133 \angle 74^\circ + 0.0004 \angle 222^\circ \\ &= 0.133 (0.275 + j 0.961) + 0.0004 (-0.743 - j 0.67) \\ &= 0.0362 + j 0.1275 = 0.1325 \angle 74^\circ 6'\end{aligned}$$

Receiving end voltage per phase is

$$V_R = 110 \times 10^3 / \sqrt{3} = 63508 \text{ V}$$

Receiving end current,

$$I_R = \frac{20 \times 10^6}{\sqrt{3} \times 110 \times 10^3 \times 0.8} = 131 \text{ A}$$

# Long Transmission Lines

Putting the various values in exp (i), we get,

$$\begin{aligned}V_S &= 63508 \times 0.992 \angle 0.26^\circ + 131 \times 445 \angle -16^\circ \times 0.1325 \angle 74^\circ 6' \\&= 63000 \angle 0.26^\circ + 7724 \angle 58^\circ 6' \\&= 63000 (0.999 + j 0.0045) + 7724 (0.5284 + j 0.8489) \\&= 67018 + j 6840 = 67366 \angle 5^\circ 50' \text{ V}\end{aligned}$$

Sending end line-to-line voltage =  $67366 \times \sqrt{3} = 116.67 \times 10^3 \text{ V} = \mathbf{116.67 \text{ kV}}$

The sending end current  $I_S$  is given by :

$$I_S = V_R \sqrt{\frac{Y}{Z}} \sinh \sqrt{Y Z} + I_R \cosh \sqrt{Y Z}$$

Putting the various values, we get,

$$\begin{aligned}I_S &= 63508 \times 0.00224 \angle 16^\circ \times 0.1325 \angle 74^\circ 6' + 131 \times 0.992 \angle 0.26^\circ \\&= 18.85 \angle 90^\circ 6' + 130 \angle 0.26^\circ \\&= 18.85 (-0.0017 + j 0.999) + 130 (0.999 + j 0.0045) \\&= 129.83 + j 19.42 = 131.1 \angle 8^\circ \text{ A}\end{aligned}$$

$\therefore$  Sending end current =  $\mathbf{131.1 \text{ A}}$



# Circle diagram at no load ( $\Phi_r=0$ )


$$I_r = 0 \quad \phi_r = 0$$

$$V_s \angle \theta = AV_r \angle \theta_a + BI_r \angle \beta \pm \phi_r$$

$$V_s \angle \theta = AV_r \angle \theta_a$$

$$\theta = \theta_a$$

$$\overline{ab} = |V_s| = |AV_r|$$

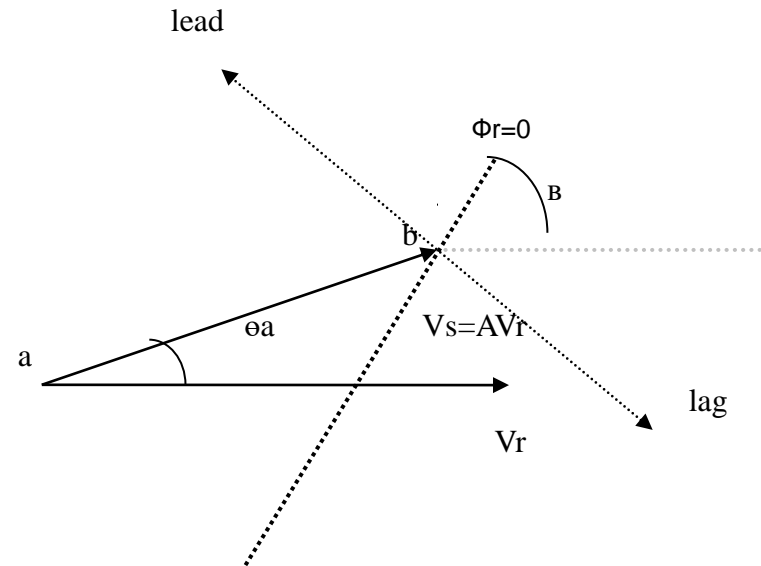

## Circle diagram at Lagging P.f ( $\Phi_r = -ve$ value)

$$V_s \angle \theta = AV_r \angle \theta_a + BI_r \angle \beta - \phi_r$$


$$\overline{ac_1} = V_{s1} \quad \text{at } \frac{1}{4} \text{ load}$$

$$\overline{ac_2} = V_{s2} \quad \text{at } \frac{1}{2} \text{ load}$$

$$\overline{ac_3} = V_{s3} \quad \text{at } \frac{3}{4} \text{ load}$$

$$\overline{ac} = V_s \quad \text{at full load}$$

# Continue

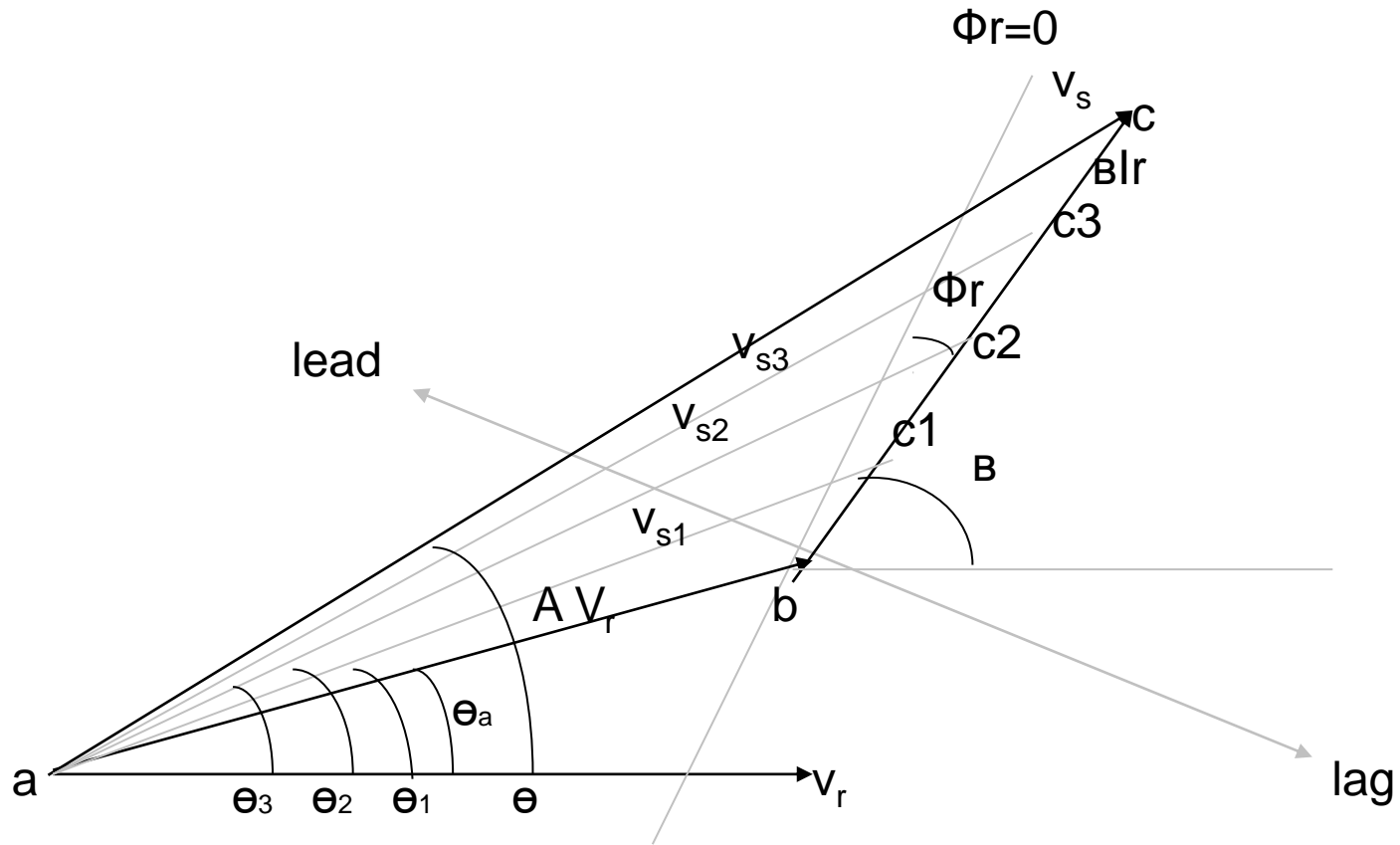

## Circle diagram at Leading P.f ( $\Phi_r = +ve$ value)

$$V_s \angle \theta = AV_r \angle \theta_a + BI_r \angle \beta + \phi_r$$

$$\overline{bc} = BI_r$$


$$\overline{ac} = V_s$$

$$c\hat{a}d = \theta$$


$$\overline{cD} = BI_r \sin \phi_r$$

$$\overline{bD} = BI_r \cos \phi_r$$

# Continue

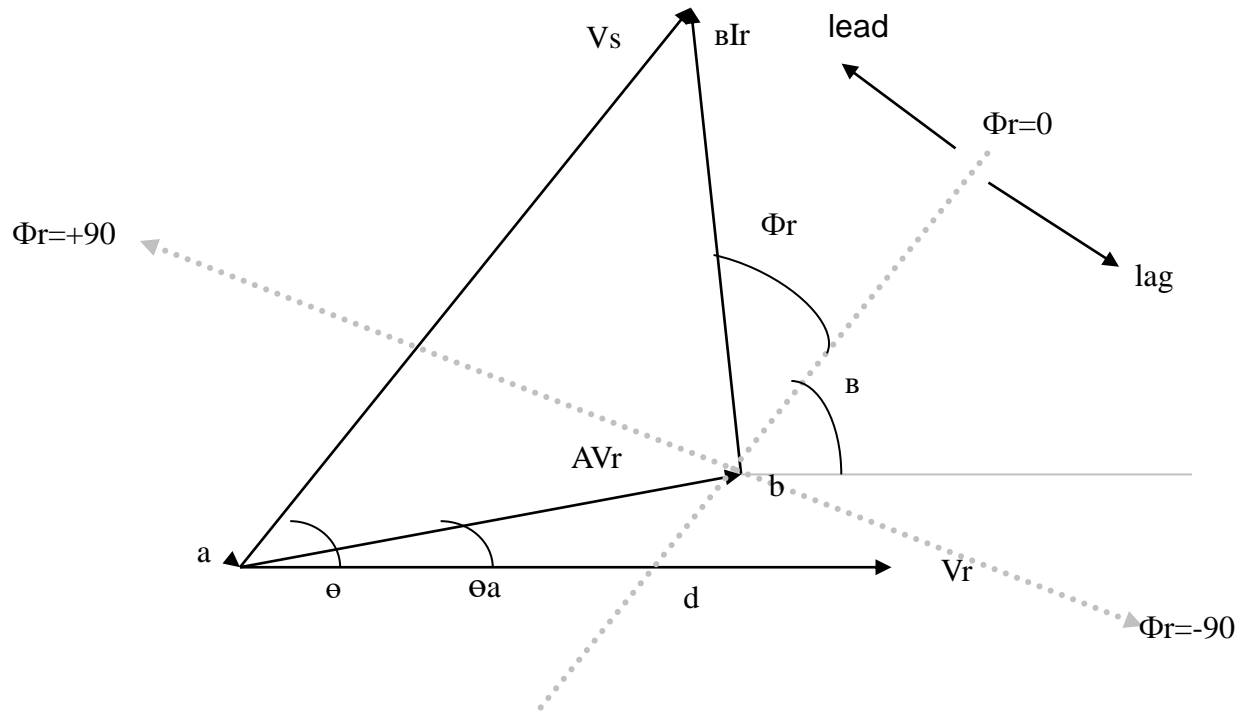

# Receiving-End Power Circle Diagram

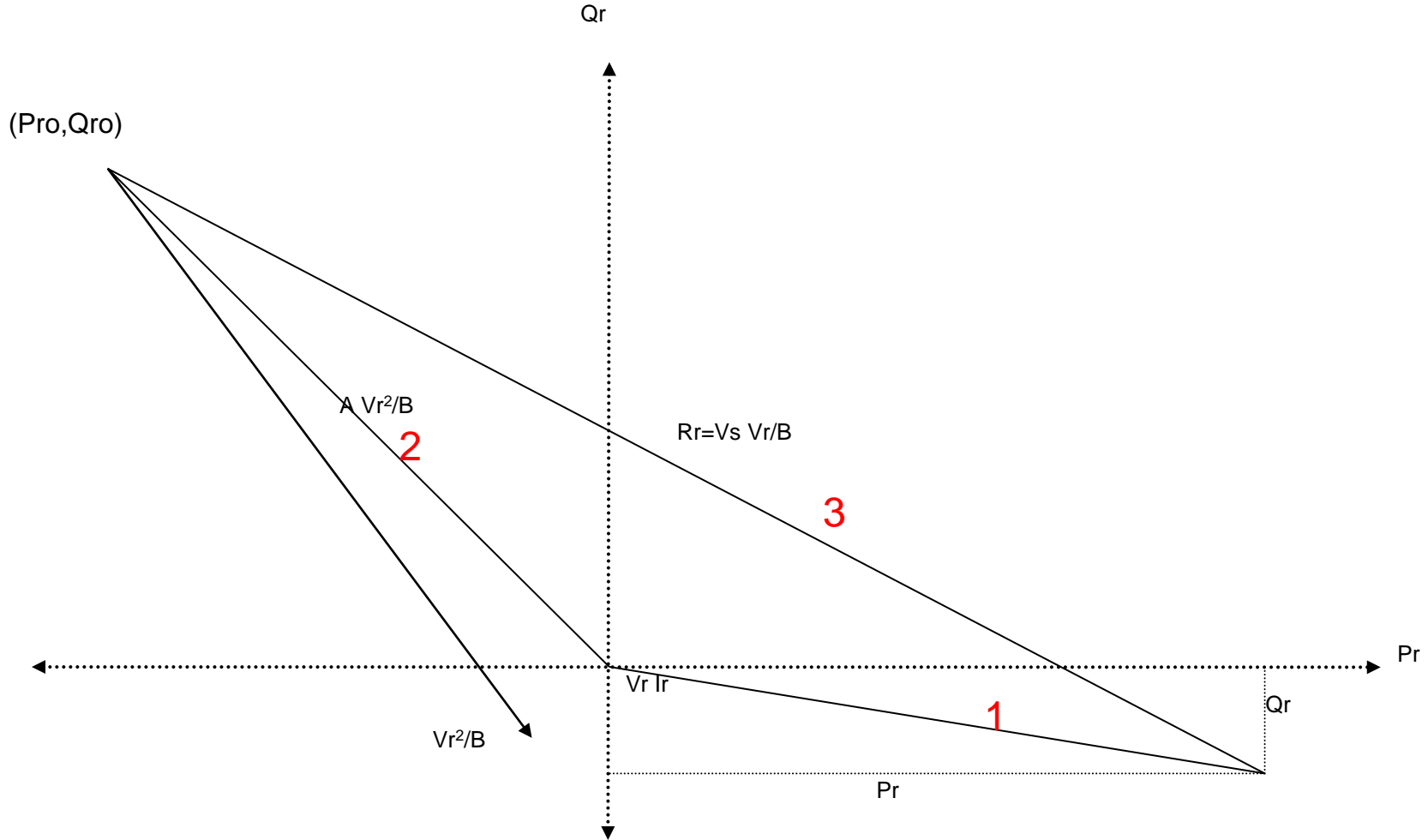

# Continue

$$V_s = AV_r + BI_r \qquad I_r = \frac{V_s}{B} - \frac{AV_r}{B}$$

$$I_r^* = \frac{V_s^*}{B^*} - \frac{A^*V_r^*}{B^*}$$

$$P_r + jQ_r = V_r I_r^*$$

$$P_r + jQ_r = \left( -\frac{A^*V_r^*}{B^*} \right) V_r + \left( \frac{V_s^*}{B^*} \right) V_r$$

$$P_r + jQ_r = -\frac{A^*}{B^*} |V_r|^2 + \frac{|V_r V_s|}{B^*} e^{-j\theta}$$

# Continue

$$P_{ro} = -\frac{AV_r^2}{B} \cos(\beta - \theta_a)$$

$$Q_{ro} = +\frac{AV_r^2}{B} \sin(\beta - \theta_a)$$

$$P_{ro} = -\frac{AV_r^2}{B} (\cos \beta \cos \theta_a + \sin \beta \sin \theta_a)$$

$$Q_{ro} = \frac{AV_r^2}{B} (\sin \beta \cos \theta_a - \cos \beta \sin \theta_a)$$



# Continue

*assume,*

$$A = a_1 + ja_2 = A \angle \theta_a \quad , B = b_1 + jb_2 = B \angle \beta$$

$$\sin \theta_a = \frac{a_2}{A} \quad \cos \theta_a = \frac{a_1}{A}$$

$$\sin \beta = \frac{b_2}{B} \quad \cos \beta = \frac{b_1}{B}$$

$$Q_{ro} = \frac{+AV_r^2}{B} \left[ \frac{b_2a_1}{AB} - \frac{b_1a_2}{AB} \right] = \frac{+V_r^2}{B^2} [a_1b_2 - a_2b_1]$$


$$P_{ro} = \frac{-AV_r^2}{B} \left[ \frac{b_1a_1}{AB} + \frac{b_2a_2}{AB} \right] = \frac{-V_r^2}{B^2} [a_1b_1 + a_2b_2]$$

# Continue

$$(P_r - P_{r0})^2 + (Q_r - Q_{r0})^2 = R_r^2$$

$$\left( P_r + \frac{a_1 b_1 + a_2 b_2}{b_1^2 + b_2^2} V_r^2 \right)^2 + \left( Q_r - \frac{(a_1 b_2 - a_2 b_1)}{b_1^2 + b_2^2} V_r^2 \right)^2 = \frac{V_s^2 V_r^2}{b_1^2 + b_2^2}$$

# Sending End Power Circle Diagram

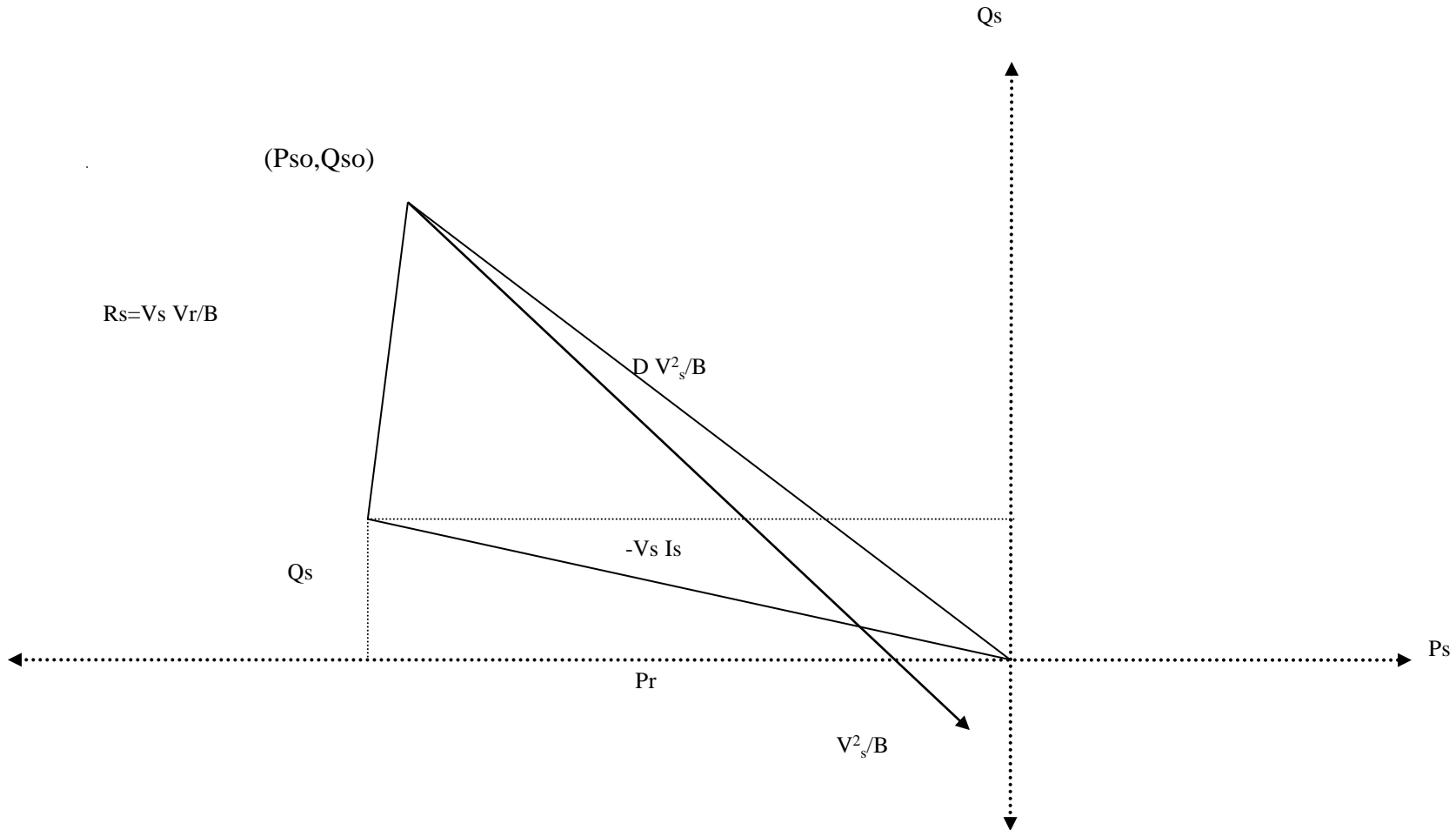

# Continue

$$\begin{aligned} DV_s - BI_s &= DAV_r - BCV_r + BDI_r - BDI_r \\ &= (DA - BC) = V_r \end{aligned}$$

$$\overline{oa} = \frac{DV_s^2}{B}$$

$$\overline{ab} = -\frac{BI_s V_s}{B} = -I_s V_s$$

$$\overline{ob} = \frac{V_s V_r}{B} = R_s$$

# Continue

$$\overline{al} = I_s V_s \cos \phi_s = P_s$$

$$\overline{bl} = V_s I_s \sin \phi_s = Q_s$$

$$P_{so} = \overline{om} = \frac{D V_s^2}{B} \cos(\beta - \theta_a)$$

$$Q_{so} = \overline{on} = \frac{D V_s^2}{B} \sin(\beta - \theta_a)$$

# Continue

$$V_r = DV_s - BI_s$$

$$= (d_1 + jd_2)V_s - (I_{sp} + jI_{sq})(b_1 + jb_2)$$

$$V_r = (d_1V_s - b_1I_{sp} + b_2I_{sq}) + j(d_2V_s - b_2I_{sp} - b_1I_{sq})$$

$$V_r^2 = (d_1^2 + d_2^2)V_s^2 + (b_1^2 + b_2^2)(I_{SP}^2 + I_{SQ}^2) \\ - 2(d_1b_1 + d_2b_2)V_sI_{sp} - 2(d_2b_1 - d_1b_2)V_sI_{sq}$$

# Continue

$$\begin{aligned} \frac{V_r^2}{b_1^2 + b_2^2} &= \frac{d_1^2 + d_2^2}{b_1^2 + b_2^2} V_s^2 \\ &+ \left[ I_{sp}^2 - 2 \frac{(d_1 b_1 + d_2 b_2)}{b_1^2 + b_2^2} V_s I_{sp} \right] + \left[ I_{sq}^2 - 2 \frac{(d_2 b_1 - d_1 b_2)}{b_1^2 + b_2^2} V_s I_{sq} \right] \\ \frac{V_r^2 V_s^2}{b_1^2 + b_2^2} &= \left[ I_{sp} V_s - \frac{(d_1 b_1 + d_2 b_2)}{b_1^2 + b_2^2} V_s^2 \right]^2 \\ &+ \left[ I_{sq} V_s + \frac{(-d_2 b_1 + d_1 b_2)}{b_1^2 + b_2^2} V_s^2 \right]^2 \end{aligned}$$

# Continue

$$R_s^2 = (P_s - P_{so})^2 + (Q_s - Q_{so})^2$$


$$P_{so} = + \frac{(d_1 b_1 + d_2 b_2)}{b_1^2 + b_2^2} V_s^2$$

$$Q_{so} = - \frac{(d_2 b_1 + d_1 b_2)}{b_1^2 + b_2^2} V_s^2$$

$$R_s = \frac{V_s V_r}{B}$$



# The Universal Power Circle Diagram

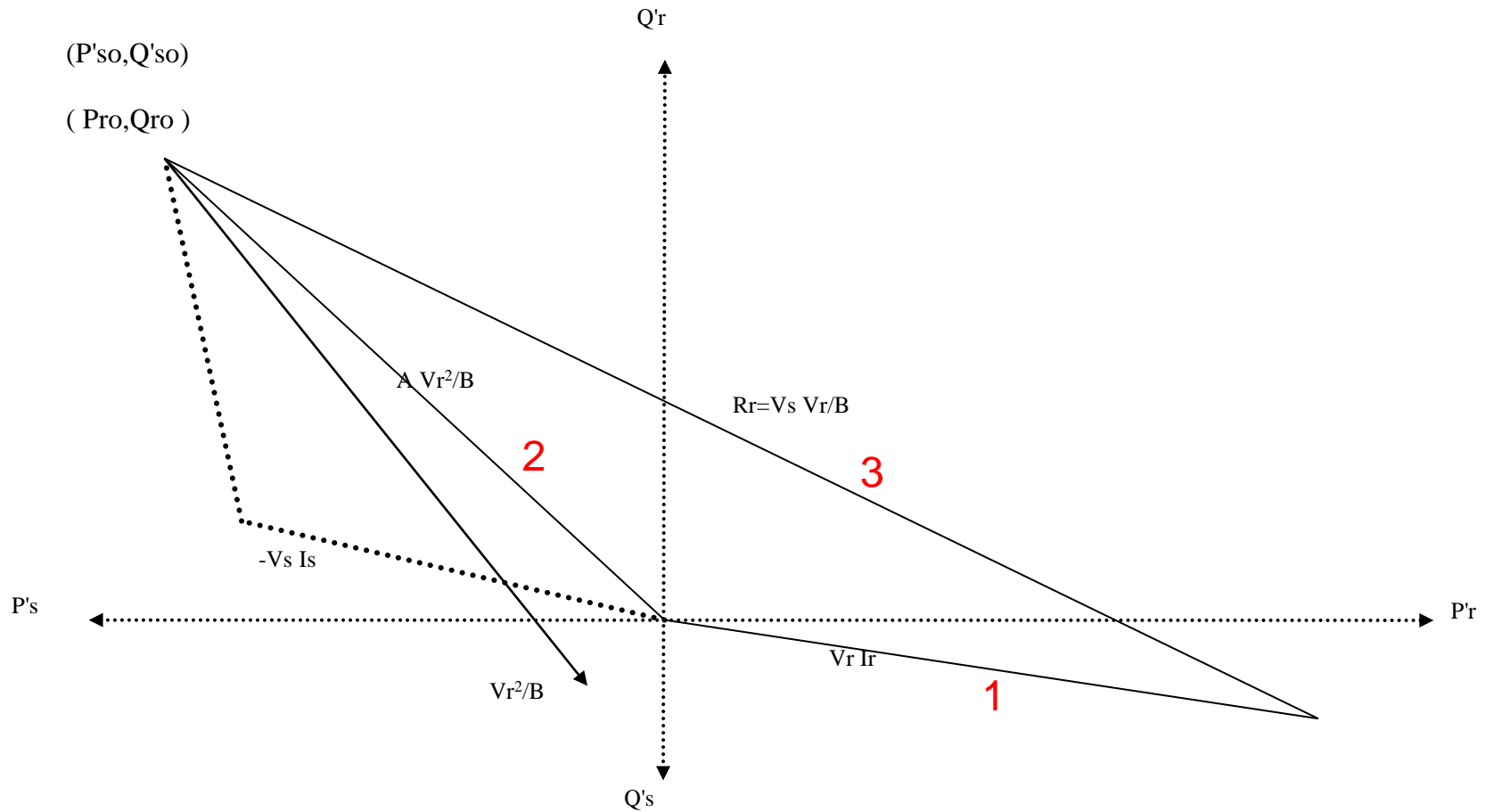

# Continue

from R.E. PCD:

$$\left[ P_r + \frac{a_1 b_1 + a_2 b_2}{b_1^2 + b_2^2} V_r^2 \right]^2 + \left[ Q_r - \frac{(a_1 b_2 - a_2 b_1)}{b_1^2 + b_2^2} V_r^2 \right]^2 = \frac{V_s^2 V_r^2}{B^2}$$

from S.E. PCD:

$$\left[ P_s - \frac{d_1 b_1 + d_2 b_2}{b_1^2 + b_2^2} V_s^2 \right]^2 + \left[ Q_s + \frac{(d_1 b_2 - d_2 b_1)}{b_1^2 + b_2^2} V_s^2 \right]^2 = \frac{V_s^2 V_r^2}{B^2}$$

$$\left[ P_r \left( \frac{V_b}{V_r} \right)^2 + \frac{a_1 b_1 + a_2 b_2}{b_1^2 + b_2^2} V_b^2 \right]^2 + \left[ Q_r \left( \frac{V_b}{V_r} \right)^2 - \frac{(a_1 b_2 - a_2 b_1)}{b_1^2 + b_2^2} V_b^2 \right]^2 = \frac{V_s^2 V_b^4}{V_r^2 B^2}$$

# Continue

$$\left[ P_s \left( \frac{V_b}{V_s} \right)^2 - \frac{a_1 b_1 + a_2 b_2}{b_1^2 + b_2^2} V_b^2 \right]^2 + \left[ Q_s \left( \frac{V_b}{V_s} \right)^2 + \frac{(a_1 b_2 - a_2 b_1)}{b_1^2 + b_2^2} V_b^2 \right]^2$$
$$= \frac{V_b^4 V_r^2}{V_s^2 B^2}$$

$$\left( \bar{P}_r + \bar{P}_{ro} \right)^2 + \left( \bar{Q}_r - \bar{Q}_{ro} \right)^2 = \bar{R}_r^2$$

$$\left( \bar{P}_s - \bar{P}_{so} \right)^2 + \left( \bar{Q}_s + \bar{Q}_{so} \right)^2 = \bar{R}_s^2$$

# Continue

It is noted that :

$$\bar{P}_{ro} = -\bar{P}_{so} = \frac{a_1 b_1 + a_2 b_2}{b_1^2 + b_2^2} V_b^2$$

$$\bar{Q}_{ro} = -\bar{Q}_{so} = \frac{a_1 b_2 - a_2 b_1}{b_1^2 + b_2^2} V_b^2$$

$$\bar{R}_r = \frac{V_s V_b^2}{V_r B}$$

$$\bar{R}_s = \frac{V_r V_b^2}{V_s B}$$

$$\bar{P}_r = P_r \left( \frac{V_b}{V_r} \right)^2$$

$$\bar{Q}_r = Q_r \left( \frac{V_b}{V_r} \right)^2$$

$$\bar{P}_s = P_s \left( \frac{V_b}{V_s} \right)^2$$

$$\bar{Q}_s = Q_s \left( \frac{V_b}{V_s} \right)^2$$



*With Our Best Wishes*  
*Transmission and Distribution of Electrical Power*  
*Course Staff*

*Associate Prof. Dr. Mohamed Ahmed Ebrahim*