# Energy Storage & Transmission

#### By

Prof. Dr. Eng. Mohamed Ahmed Ebrahim Mohamed

E-mail: <u>mohamedahmed\_en@yahoo.com</u>

mohamed.mohamed@feng.bu.edu.eg

Web site: http://bu.edu.eg/staff/mohamedmohamed033



FACULTY OF ENGINEERING- SHOUBRA

# Lecture (3)

# Transmission line Models L Calculation

#### Transmission line models

Transmission line models parameters include:

series resistance & inductance & shunt capacitance.

- In this lecture we shall discuss the various models of the line.
- The line models are classified by their length. These classifications are:
- Short line approximation for lines that are <u>less than 80 km</u> <u>long</u>.
- Medium line approximation for lines whose lengths are between 80 km to 240 km.
- 3. Long line model for lines that are <u>longer than 240 km</u>.

#### **ABCD Parameters**

- Consider the power system In this the sending and receiving end voltages are denoted by V<sub>S</sub> and V<sub>R</sub> respectively.
- Also the currents I<sub>S</sub> and I<sub>R</sub> are entering and leaving the network respectively.
- The sending end voltage and current are then defined in terms of the ABCD parameters as

$$V_{S} = AV_{R} + BI_{R}$$
$$I_{S} = CV_{R} + DI_{R}$$

### 1. Long line model

- For accurate modeling of the transmission line we must not assume that the parameters are lumped but are distributed throughout line.
- The single-line diagram of a long transmission line is shown The length of the line is I.
- $\square$  consider a small strip  $\Delta x$  that is at a distance x from the receiving end.
- □ The voltage and current at the end of the strip are V and I respectively and the beginning of the strip are V +  $\Delta$ V and I +  $\Delta$ I respectively.

□ The voltage drop across the strip is then  $\Delta V$ . Since the length of the strip is  $\Delta x$ , the series impedance and shunt admittance are  $z\Delta x$  and  $y\Delta x$ . It is to be noted here that the total impedance and admittance of the line are  $Z = z \times l$  and  $Y = y \times l$ 



Long transmission line representation.

#### From the circuit

$$\Delta V = Iz \,\Delta x \Longrightarrow \frac{\Delta V}{\Delta x} = Iz \tag{2.25}$$

Again as  $\Delta x \rightarrow 0$ , from (2.25) we get

$$\frac{dV}{dx} = Iz \tag{2.26}$$

Now for the current through the strip, applying KCL we get

$$\Delta I = (V + \Delta V)y \,\Delta x = Vy \,\Delta x + \Delta Vy \,\Delta x \tag{2.27}$$

The second term of the above equation is the product of two small quantities and therefore can be neglected. For  $\Delta x \rightarrow 0$  we then have

$$\frac{dI}{dx} = Vy \tag{2.28}$$

Taking derivative with respect to x of both sides of (2.26) we get

$$\frac{d}{dx}\left(\frac{dV}{dx}\right) = z\frac{dI}{dx}$$

Substitution of (2.28) in the above equation results

$$\frac{d^2 V}{dx^2} - y z V = 0 (2.29)$$

The roots of the above equation are located at  $\pm \sqrt{yz}$ . Hence the solution of (2.29) is of the form

$$V = A_1 e^{x\sqrt{yz}} + A_2 e^{-x\sqrt{yz}}$$
(2.30)

Taking derivative of (2.30) with respect to x we get

$$\frac{dV}{dx} = A_1 \sqrt{yz} e^{x\sqrt{yz}} - A_2 \sqrt{yz} e^{-x\sqrt{yz}}$$
(2.31)

Combining (2.26) with (2.31) we have

$$I = \frac{1}{z} \left( \frac{dV}{dx} \right) = \frac{A_1}{\sqrt{z/y}} e^{x\sqrt{yz}} - \frac{A_2}{\sqrt{z/y}} e^{-x\sqrt{yz}}$$
(2.32)

Let us define the following two quantities

$$Z_{C} = \sqrt{\frac{z}{y}} \Omega \text{ which is called the characteristic impedance}$$
(2.33)

$$\gamma = \sqrt{yz}$$
 which is called the *propagation constant* (2.34)

Then (2.30) and (2.32) can be written in terms of the characteristic impedance and propagation constant as

$$V = A_1 e^{\gamma x} + A_2 e^{-\gamma x}$$
(2.35)  
$$V = A_1 e^{\gamma x} + A_2 e^{-\gamma x}$$
(2.36)

$$I = \frac{1}{Z_C} e^{\gamma x} - \frac{1}{Z_C} e^{-\gamma x}$$
(2.36)

Let us assume that x = 0. Then  $V = V_R$  and  $I = I_R$ . From (2.35) and (2.36) we then get

$$V_{R} = A_{1} + A_{2}$$
(2.37)  
$$I_{R} = \frac{A_{1}}{Z_{C}} - \frac{A_{2}}{Z_{C}}$$
(2.38)

Solving (2.37) and (2.38) we get the following values for  $A_1$  and  $A_2$ .

$$A_1 = \frac{V_R + Z_C I_R}{2}$$
 and  $A_2 = \frac{V_R - Z_C I_R}{2}$ 

Also note that for l = x we have  $V = V_S$  and  $I = I_S$ . Therefore replacing x by l and substituting the values of  $A_1$  and  $A_2$  in (2.35) and (2.36) we get

$$V_{S} = \frac{V_{R} + Z_{C}I_{R}}{2}e^{jl} + \frac{V_{R} - Z_{C}I_{R}}{2}e^{-jl}$$

$$I_{S} = \frac{V_{R}/Z_{C} + I_{R}}{2}e^{jl} - \frac{V_{R}/Z_{C} - I_{R}}{2}e^{-jl}$$
(2.39)
(2.39)

#### Noting that

$$\frac{e^{i\theta} - e^{-i\theta}}{2} = \sinh i\theta \text{ and } \frac{e^{i\theta} + e^{-i\theta}}{2} = \cosh i\theta$$

We can rewrite (2.39) and (2.40) as

$$V_{S} = V_{R} \cosh \gamma l + Z_{C} I_{R} \sinh \gamma l$$

$$I_{S} = V_{R} \frac{\sinh \gamma l}{Z_{C}} + I_{R} \cosh \gamma l$$
(2.41)
(2.42)

# The ABCD parameters of the long transmission line can then be written as

$$A = D = \cosh t$$
$$B = Z_c \sinh t \Omega$$
$$C = \frac{\sinh t}{Z_c} \text{ mho}$$

#### 2. Medium transmission lines

Medium transmission lines are modeled with lumped shunt admittance.

- There are two different representations depending on the nature of the network:
- 2.1 Nominal ( $\pi$ ).
- 2.2 Nominal (T).

## 2.1 Nominal ( $\pi$ )

- in this representation the lumped series impedance is placed in the middle while the shunt admittance is divided into two equal parts and placed at the two ends.
- The nominal (π) representation is used for load flow studies.
- Also a long transmission line can be modeled as an equivalent (π) network for load flow studies.

- Let us define three currents I<sub>1</sub>, I<sub>2</sub> and I<sub>3</sub> as indicated in Figure.
- Applying KCL at nodes M and N we get

$$I_{s} = I_{1} + I_{2} = I_{1} + I_{3} + I_{R}$$
$$= \frac{Y}{2}V_{s} + \frac{Y}{2}V_{R} + I_{R}$$

Again



$$V_{s} = ZI_{2} + V_{R} = Z\left(V_{R}\frac{Y}{2} + I_{R}\right) + V_{R}$$
$$= \left(\frac{YZ}{2} + 1\right)V_{R} + ZI_{R}$$

Nominal- $\pi$  representation.

Substituting

$$I_{z} = \frac{Y}{2} \left[ \left( \frac{YZ}{2} + 1 \right) V_{R} + ZI_{R} \right] + \frac{Y}{2} V_{R} + I_{R}$$
$$= Y \left( \frac{YZ}{4} + 1 \right) V_{R} + \left( \frac{YZ}{2} + 1 \right) I_{R}$$

#### $\square$ the ABCD parameters of the nominal ( $\pi$ ) representation



## 2.2 Nominal (T)

In this representation the shunt admittance is placed in the middle and the series impedance is divided into two equal parts and these parts are placed on either side of the shunt admittance.



Nominal-T representation.

$$\frac{V_{\rm S}-V_{\rm M}}{Z/2}=YV_{\rm M}+\frac{V_{\rm M}-V_{\rm R}}{Z/2}$$

Rearranging the above equation can be written as

$$V_{M} = \frac{2}{YZ + 4} \left( V_{S} + V_{R} \right)$$
(2.16)

Now the receiving end current is given by

$$I_R = \frac{V_M - V_R}{Z/2} \tag{2.17}$$

Substituting the value of  $V_M$  from (2.16) in (2.17) and rearranging we get

$$V_{s} = \left(\frac{YZ}{2} + 1\right)V_{R} + Z\left(\frac{YZ}{4} + 1\right)I_{R}$$
(2.18)

Furthermore the sending end current is

$$I_S = YV_M + I_R \tag{2.19}$$

Then substituting the value of  $V_M$  from (2.16) in (2.19) and solving

$$I_R = YV_R + \left(\frac{YZ}{2} + 1\right)I_R \tag{2.20}$$

# Then the ABCD parameters of the T-network are



### 3. Short line approximation

- The shunt capacitance for a short line is almost negligible.
- □ The series impedance is assumed to be lumped as shown in Figure. If the impedance per km for an I km long line is  $z_0 = r + jx$ , then the total impedance of the line is:

Z = R + jX = lr + jlx.



Short transmission line representation.

The sending end voltage and current for this approximation are given by:

$$V_{S} = V_{R} + ZI_{R}$$
$$I_{S} = I_{R}$$

Therefore the ABCD parameters are given by

 $A = D = 1, B = Z \Omega$  and C = 0

# Transmission line Models J Calculation Practical Solved Examples

1. Long line model

The ABCD parameters of the long transmission line can then be written as

 $A = D = \cosh t$  $B = Z_c \sinh t \Omega$  $C = \frac{\sinh t}{Z_c} \text{ mho}$ 

#### 2. Medium transmission lines

Medium transmission lines are modeled with lumped shunt admittance.

- There are two different representations depending on the nature of the network:
- 2.1 Nominal ( $\pi$ ).
- 2.2 Nominal (T).

## 2.1 Nominal ( $\pi$ )

 $\square$  The ABCD parameters of the nominal ( $\pi$ ) representation



## 2.2 Nominal (T)

□ The ABCD parameters of the nominal (T) representation



#### 3. Short line approximation

The ABCD parameters of the short line representation

#### $A = D = 1, B = Z \Omega$ and C = 0

### Example (1):

**Example** Consider a 500 km long line for which the per kilometer line impedance and admittance are given respectively by  $z = 0.1 + j0.5145 \Omega$  and  $y = j3.1734 \times 10^{-6}$  mho. Therefore

$$Z_{C} = \sqrt{\frac{z}{y}} = \sqrt{\frac{0.1 + j0.5145}{j3.1734 \times 10^{-6}}} = \sqrt{\frac{0.5241 \angle 79^{\circ}}{3.1734 \times 10^{-6} \angle 90^{\circ}}} = \sqrt{\frac{0.5241}{3.1734 \times 10^{-6}}} \angle \left(\frac{79^{\circ} - 90^{\circ}}{2}\right)$$
$$= 406.4024 \angle -5.5^{\circ} \Omega$$

and

$$d = \sqrt{yz} \times l = \sqrt{0.5241 \times 3.1734 \times 10^{-6}} \times 500 \angle \left(\frac{79^\circ + 90^\circ}{2}\right)$$
$$= 0.6448 \angle 84.5^\circ = 0.0618 + j0.6419$$

We shall now use the following two formulas for evaluating the hyperbolic forms

$$\cosh(\alpha + j\beta) = \cosh \alpha \cos \beta + j \sinh \alpha \sin \beta$$
  
 $\sinh(\alpha + j\beta) = \sinh \alpha \cos \beta + j \cosh \alpha \sin \beta$ 

Application of the above two equations results in the following values

$$\cosh \gamma l = 0.8025 + j0.037$$
 and  $\sinh \gamma l = 0.0495 + j0.5998$ 

Therefore from (2.43) to (2.45) the ABCD parameters of the system can be written as

A = D = 0.8025 + j0.037 $B = 43.4 + j240.72 \Omega$  $C = -2.01 \times 10^{-5} + j0.0015$ 

ΔΔΔ

## Example (2):

A single phase overhead transmission line delivers 1100 kW at 33 kV at 0.8 p.f. lagging. The total resistance and inductive reactance of the line are  $10^{\circ}$  and  $15^{\circ}$  respectively. Determine : (i) sending end voltage (ii) sending end power factor and (iii) transmission efficiency.

#### Solution.

Load power factor,  $\cos \phi_R = 0.8$  lagging Total line impedance,  $\vec{Z} = R + j X_L = 10 + j 15$ 

Receiving end voltage,  $V_R = 33 \text{ kV} = 33,000 \text{ V}$ 

Line current, 
$$I = \frac{kW \times 10^3}{V_R \cos \phi_R} = \frac{1100 \times 10^3}{33,000 \times 0.8} = 41.67 \text{ A}$$
  
As  $\cos \phi_R = 0.8$  :  $\sin \phi_R = 0.6$ 



#### Performance of Single Phase Short Transmission Lines

$$\overrightarrow{V_R} = V_R + j \, 0 = 33000 \, \text{V}$$

$$\overset{+}{I} = I \left( \cos \phi_R - j \sin \phi_R \right)$$

$$= 41.67 \left( 0.8 - j \, 0.6 \right) = 33.33 - j \, 25$$
(i) Sending end voltage,  $\overrightarrow{V_S} = \overrightarrow{V_R} + \overset{+}{I} Z$ 

$$= 33,000 + (33.33 - j \, 25.0) \left( 10 + j \, 15 \right)$$

$$= 33,000 + 333.3 - j \, 250 + j \, 500 + 375$$

$$= 33,708.3 + j \, 250$$
Magnitude of  $V_S = \sqrt{(33,708.3)^2 + (250)^2} = 33,709 \, \text{V}$ 

(*ii*) Angle between  $\overrightarrow{V_S}$  and  $\overrightarrow{V_R}$  is  $\alpha = \tan^{-1} \frac{250}{33,708 \cdot 3} = \tan^{-1} 0.0074 = 0.42^{\circ}$ : Sending end power factor angle is

 $\phi_{S} = \phi_{R} + u = 36.87^{\circ} + 0.42^{\circ} = 37.29^{\circ}$ Sending end p.f.,  $\cos \phi_{S} = \cos 37.29^{\circ} = 0.7956$  lagging (*iii*) Line losses  $= I^{2}R = (41.67)^{2} \times 10 = 17,364$  W = 17.364 kW Output delivered = 1100 kW Power sent = 1100 + 17.364 = 1117.364 kW Transmission efficiency  $= \frac{Power delivered}{Power sent} \times 100 = \frac{1100}{1117.364} \times 100 = 98.44\%$ 

**Note.**  $V_s$  and  $\phi_s$  can also be calculated as follows :

- $V_S = V_R + IR \cos \phi_R + IX_L \sin \phi_R$  (approximately)
  - $= 33,000 + 41.67 \times 10 \times 0.8 + 41.67 \times 15 \times 0.6$
  - = 33,000 + 333.36 + 375.03
  - =  $33708 \cdot 39$  V which is approximately the same as above

$$\cos \phi_{S} = \frac{V_{R} \cos \phi_{R} + IR}{V_{S}} = \frac{33,000 \times 0.8 + 41.67 \times 10}{33,708.39} = \frac{26,816.7}{33,708.39}$$
$$= 0.7958$$

# Example (3):

A (medium) single phase transmission line 100 km long has the following constants :

Resistance/km = 0.25 (1); Susceptance/km =  $14 \times 10^{-6}$  siemen ; Reactance/km = 0.8  $\square$ 

Receiving end line voltage = 66,000 V

Assuming that the total capacitance of the line is localised at the receiving end alone, determine (i) the sending end current (ii) the sending end voltage (iii) regulation and (iv) supply power factor. The line is delivering 15,000 kW at 0.8 power factor lagging. Draw the phasor diagram to illustrate your calculations.

**Solution.** Figs. 10.10 (*i*) and (*ii*) show the circuit diagram and phasor diagram of the line respectively.



 $R = 0.25 \times 100 = 25$ Total resistance,  $X_L = 0.8 \times 100 = 80$  Å Total reactance,  $Y = 14 \times 10^{-6} \times 100 = 14 \times 10^{-4} S$ Total susceptance, Receiving end voltage,  $V_{p} = 66,000 \text{ V}$  $I_R = \frac{15,000 \times 10^3}{66,000 \times 0.8} = 284 \text{ A}$ Load current, Ŀ  $\cos \phi_P = 0.8$ ;  $\sin \phi_P = 0.6$ Taking receiving end voltage as the reference phasor [see Fig. 10.10 (*ii*)], we have,  $\overrightarrow{v} = V + (0 - 66000)$ 

Load current,

$$\vec{V}_{R} = \vec{V}_{R} + j \, 0 = 00,000 \, V$$
  
$$\vec{I}_{R} = I_{R} \left( \cos \phi_{R} - j \sin \phi_{R} \right) = 284 \, (0.8 - j \, 0.6) = 227 - j \, 170$$

Capacitive current, $\overrightarrow{I_C}$		$\overrightarrow{I_C}$	$= j Y \times V_R = j 14 \times 10^{-4} \times 66000 = j 92$	
( <i>i</i> )	Sending end current,	$\overrightarrow{I_S}$	$= \vec{I}_R + \vec{I}_C = (227 - j170) + j92$	
			= 227 - j78	(i)
	Magnitude o	f I <sub>s</sub>	$= \sqrt{(227)^2 + (78)^2} = 240 \text{ A}$	
(ii)	Voltage drop		$= \vec{I}_{S} \vec{Z} = \vec{I}_{S} (R + j X_{L}) = (227 - j 78) (25 + j 80)$	
			= 5,675 + j 18, 160 - j 1950 + 6240	
			= 11,915 + j 16,210	
Sending end voltage, $\overrightarrow{V_s}$		$\overrightarrow{V_{s}}$	$= \overrightarrow{V_R} + \overrightarrow{I_S} \overrightarrow{Z} = 66,000 + 11,915 + j 16,210$	
		5	= 77,915 + j 16,210	<u>(ii)</u>
	Magnitude of	f V <sub>s</sub>	$= \sqrt{(77915)^2 + (16210)^2} = 79583V$	

(*iii*) % Voltage regulation = 
$$\frac{V_S - V_R}{V_R} \times 100 = \frac{79,583 - 66,000}{66,000} \times 100 = 20.58\%$$
  
(*iv*) Referring to exp. (*i*), phase angle between  $\overrightarrow{V}$  and  $\overrightarrow{L}$  is :

(*iv*) Referring to exp. (*i*), phase angle between  $\overline{V_R}$  and  $\overline{I_s}$  is :  $\theta_1 = \tan^{-1} - \frac{78}{227} = \tan^{-1}(-0.3436) = -18.96^\circ$ 

Referring to exp. (*ii*), phase angle between  $\overrightarrow{V_R}$  and  $\overrightarrow{V_S}$  is :

$$\theta_2 = \tan^{-1} \frac{16210}{77915} = \tan^{-1} (0.2036) = 11.50^{\circ}$$

Supply power factor angle,  $\phi_s = 18.96^\circ + 11.50^\circ = 30.46^\circ$ Supply p.f.  $= \cos \phi_s = \cos 30.46^\circ = 0.86 \log 10^\circ$ 

## Example (4):

A 3- $\phi$  transmission line 200 km long has the following constants : Resistance/phase/km = 0.16  $\square$ Reactance/phase/km = 0.25  $\square$ Shunt admittance/phase/km =  $1.5 \times 10^{-6}$  S

Calculate by rigorous method the sending end voltage and current when the line is delivering a load of 20 MW at 0.8 p.f. lagging. The receiving end voltage is kept constant at 110 kV.

#### Solution :

Total resistance/phase, $R = 0.16 \times 200 = 32$   $\[mathbb{N}]$ Total reactance/phase, $X_L = 0.25 \times 200 = 50$   $\[mathbb{N}]$ Total shunt admittance/phase, $Y = j 1.5 \times 10^{-6} \times 200 = 0.0003 \[mathbb{L}]$ Series Impedance/phase, $Z = R + j X_L = 32 + j 50 = 59.4 \[mathbb{L}]$ 

The sending end voltage  $V_s$  per phase is given by :

-

$$V_{S} = V_{R} \cosh \sqrt{Y Z} + I_{R} \sqrt{\frac{Z}{Y}} \sinh \sqrt{Z Y} \qquad \dots(i)$$

$$\sqrt{Z Y} = \sqrt{59 \cdot 4 \, \ell \, 58\% \ 0 \ 0003 \ 90^{\circ}} \cdot 0 \ 133 \ 74^{\circ}$$

$$Z Y = 0.0178 \, \ell \, 148^{\circ}$$

$$Z^{2}Y^{2} = 0.00032 \, \ell \, 296^{\circ}$$

$$\sqrt{\frac{Z}{Y}} = \sqrt{\frac{59 \cdot 4 \, \ell \, 58^{\circ}}{0.0003 \, \ell \, 90^{\circ}}} = 445 \, \ell - 16^{\circ}$$

$$\sqrt{\frac{Y}{Z}} = \sqrt{\frac{0.0003 \, \ell \, 90^{\circ}}{59 \cdot 4 \, \ell \, 58^{\circ}}} = 0 \cdot 00224 \, \ell \, 16^{\circ}$$

$$\cosh \sqrt{Y Z} = 1 + \frac{Z Y}{2} + \frac{Z^{2} Y^{2}}{24} \text{ approximately}$$

$$= 1 + \frac{0.0178}{2} \, \ell \, 148^{\circ} + \frac{0.00032}{24} \, \ell \, 296^{\circ}$$

$$= 1 + 0.0089 \, \ell \, 148^{\circ} + 0.0000133 \, \ell \, 296^{\circ}$$

$$= 1 + 0.0089 \, (-0.848 + j \, 0.529) + 0.0000133 \, (0.438 - j \, 0.9)$$

$$= 0.992 + j \, 0.00469 = 0.992 \, \ell \, 0.26^{\circ}$$

Now

.

$$\sinh \sqrt{Y Z} = \sqrt{Y Z} + \frac{(Y Z)^{3/2}}{6} \text{ approximately}$$
  
= 0.133 / 744  $\frac{0.0024 / 222^{\circ}}{6}$   
= 0.133 / 74^{\circ} + 0.0004 / 222^{\circ}  
= 0.133 (0.275 + j 0.961) + 0.0004 (-0.743 - j 0.67)  
= 0.0362 + j 0.1275 = 0.1325 / 74^{\circ}6'

Receiving end voltage per phase is

$$V_R = 110 \times 10^3 / \sqrt{3} = 63508 \text{ V}$$
$$I_R = \frac{20 \times 10^6}{\sqrt{3} \times 110 \times 10^3 \times 0.8} = 131 \text{ A}$$

Receiving end current,

Putting the various values in exp(i), we get,

- $V_{S} = 63508 \times 0.992 \ / 0.26^{\circ} + 131 \times 445 \ / 16^{\circ}0' \times 0.1325 \ / 74^{\circ}6'$ 
  - = 63000 / 0.26° + 7724 / 58°6'
  - $= 63000 (0.999 + j \ 0.0045) + 7724 (0.5284 + j \ 0.8489)$
  - $= 67018 + j 6840 = 67366 \angle 5^{\circ}50' V$

Sending end line-to-line voltage =  $67366 \times \sqrt{3} = 116.67 \times 10^3 \text{ V} = 116.67 \text{ kV}$ The sending end current  $I_s$  is given by :

$$I_S = V_R \sqrt{\frac{Y}{Z}} \sinh \sqrt{Y Z} + I_R \cosh \sqrt{Y Z}$$

Putting the various values, we get,

- $$\begin{split} I_S &= 63508 \times 0.00224 \, \text{(} 16^{\circ} \times 0.1325 \, \text{(} 74^{\circ}6' + 131 \times 0.992 \, \text{(} 0.26^{\circ} \\ &= 18.85 \, \text{(} 90^{\circ}6' + 130 \, \text{(} 0.26^{\circ} \\ &= 18.85 \, (-0.0017 + j \, 0.999) + 130 \, (0.999 + j \, 0.0045) \\ &= 129.83 + j \, 19.42 = 131.1 \, \text{(} 8^{\circ} \text{ A} \end{split}$$
- Sending end current =  $131 \cdot 1 A$