

Contents

- CH1: *Sinusoids and Phasors*
- CH2: *Sinusoidal steady-State Analysis*
- CH3: *AC Power Analysis*
- CH4: *Three Phase Circuits*
- CH5: *Transient Response of Circuits*
- CH6: *Fourier Analysis and Circuit Applications*
- CH7: *Two-Port Circuits*




References



- ❑ Mahmood Nahvi, Joseph A. Edminster, "Electric Circuits", Schaum's Outlines, Mc Graw Hill. ISBN: 9780071633727, 2011.
- ❑ James W. Nilsson, Susan A. Riedel, "Electric Circuits", Prentice Hall, New Jersey, ISBN:9780137050512-0137050518, 2011.
- ❑ Jhon Bird, "Electrical Theory and Technology", Elsevier, Oxford, ISBN:9780080549798-0080549799, 2007.




Chapter I

SinuSoidS, PhaSorS and Resonance

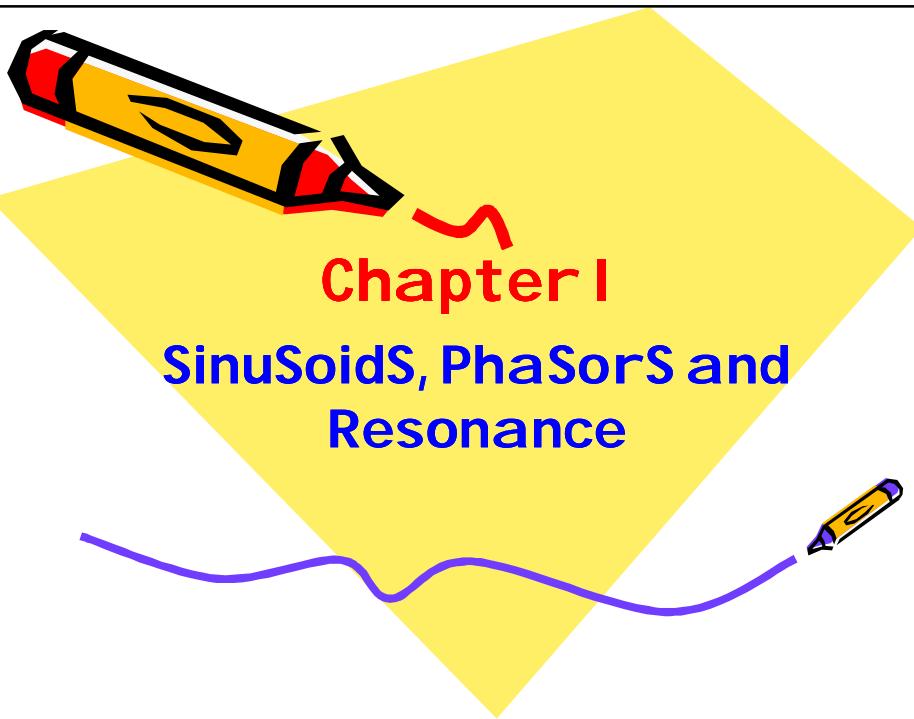

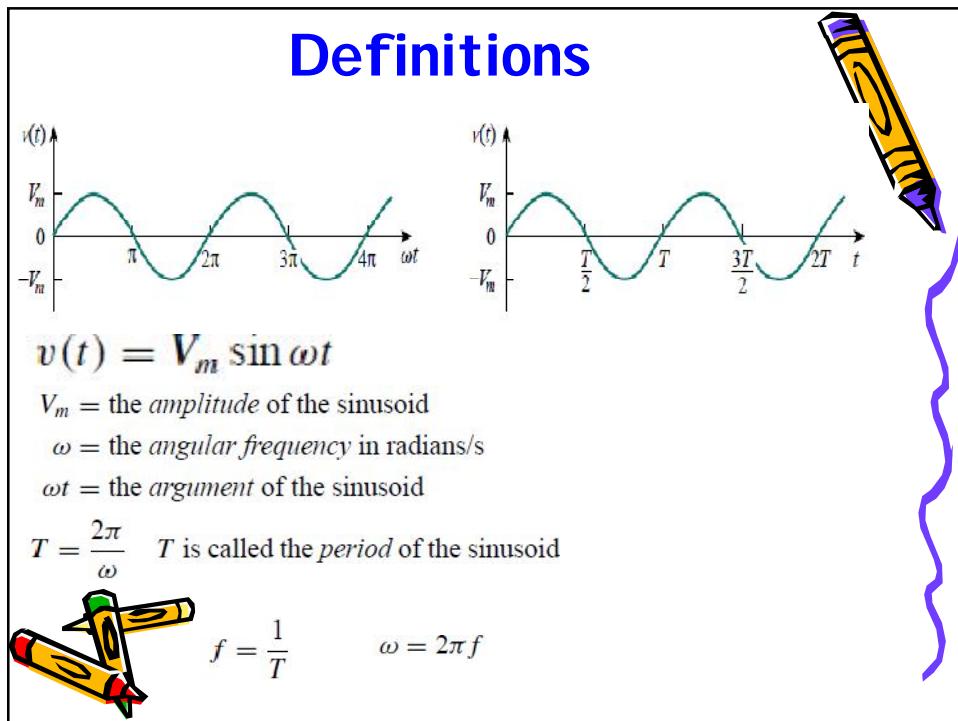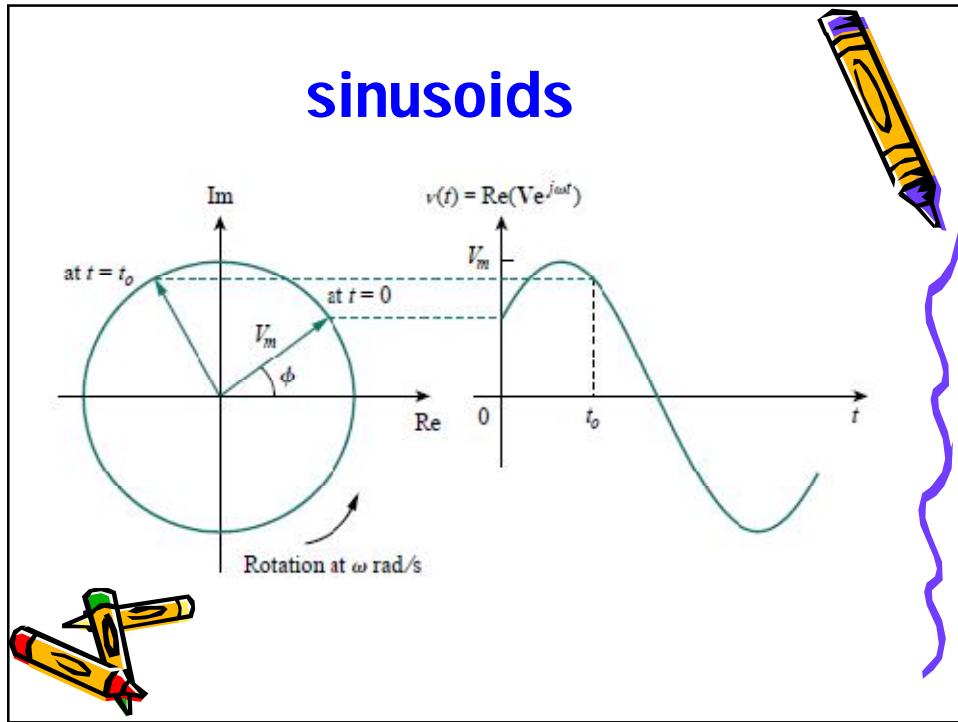

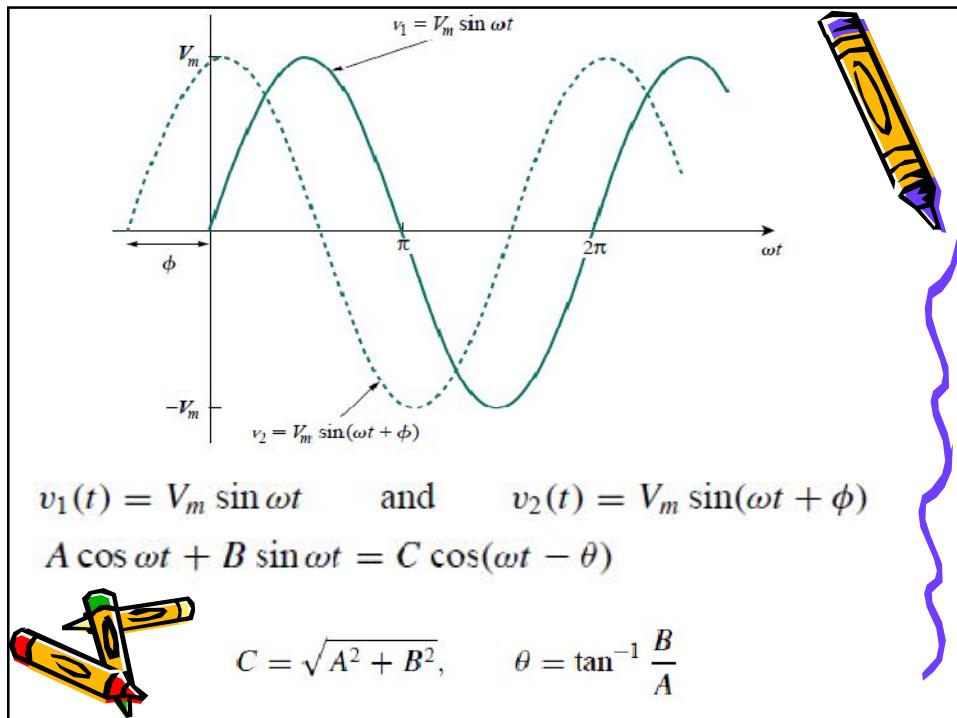

Ex.1: Find the amplitude, phase, period, and frequency of the sinusoid: $v(t)=12\cos(50t+10^\circ)$

Solution:

The amplitude is: $V_m = 12 \text{ V}$

The phase is : $\phi = 10^\circ$

The angular frequency is $\omega = 50 \text{ rad/s}$

The period is: $T = (2\pi/\omega) = (2\pi/50) = 0.1257 \text{ s}$

The frequency is $f = (1/T) = (1/0.1257) = 7.958 \text{ Hz}$

**Ex.2 : Calculate the phase angle between
 $v_1 = -10 \cos(\omega t + 50^\circ)$ & $v_2 = 12 \sin(\omega t - 10^\circ)$
 state which sinusoid is leading**

Solution


$$v_1 = -10 \cos(\omega t + 50^\circ) = 10 \cos(\omega t + 50^\circ - 180^\circ)$$

$$v_1 = 10 \cos(\omega t - 130^\circ)$$


$$v_2 = 12 \sin(\omega t - 10^\circ) = 12 \cos(\omega t - 10^\circ - 90^\circ)$$

$$v_2 = 12 \cos(\omega t - 100^\circ)$$

v_2 leads v_1 by 30° .

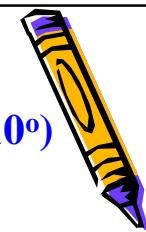

Phasor diagram

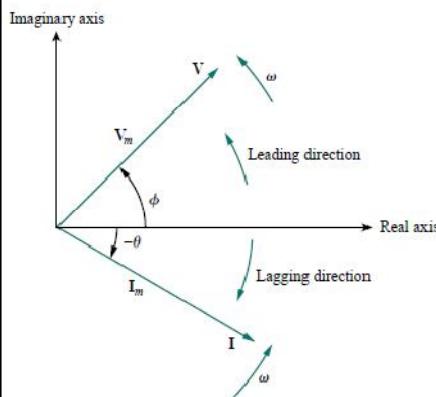


$$v(t) = V_m \sin(\omega t + \phi) = \text{Im}(V_m e^{j(\omega t + \phi)})$$

$$v(t) = \text{Im}(V_m e^{j\omega t} e^{j\phi}) = \text{Im}(V e^{j\omega t})$$

$$V = \text{Im}(V_m e^{j\phi}) = V_m e^{j\phi} = V_m \angle \phi$$

Phasors

$$V = V_m \angle \phi \quad I = I_m \angle \theta$$

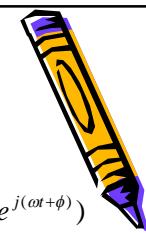

Ex. 3 : Transform these sinusoids to phasors:

$$(a) v = -4 \sin(30t+50^\circ)$$

$$(b) i = 6 \cos(50t-40^\circ)$$



Solution

$$(a) v = -4 \sin(30t+50^\circ) = 4 \cos (30t+50+90^\circ)$$

$$= 4 \cos (30t + 140^\circ)$$

The phasor form of v is $V = 4 \angle 140^\circ$

$$(b) i = 6 \cos(50t - 40^\circ)$$

The phasor $I = 6 \angle -40^\circ$



**Ex.4: Given $i_1(t)=4\cos(\omega t+30^\circ)$ and
 $i_2(t)=5\sin(\omega t-20^\circ)$, find their sum.**



Solution:

$$i_1(t)= 4 \cos(\omega t+30^\circ) \quad I_1 = 4 \angle 30^\circ$$

$$i_2(t)= 5 \sin(\omega t-20^\circ) = 5 \cos(\omega t - 20^\circ - 90^\circ) = 5 \cos(\omega t - 110^\circ)$$

$$I_2 = 5 \angle -110^\circ$$

$$I = I_1 + I_2 = 4 \angle 30^\circ + 5 \angle -110^\circ = 3.464 + j2 - 1.71 - j4.698$$

$$= 1.754 - j2.698 = 3.218 \angle -56.97^\circ$$





Phasor relationship for circuit elements

(a) Resistor

$$i = I_m \cos(\omega t + \phi)$$

$$v = i R = RI_m \cos(\omega t + \phi)$$
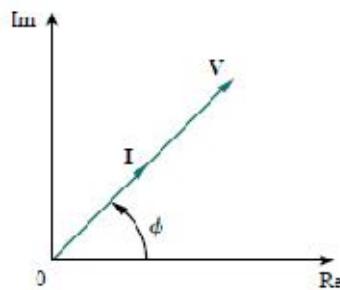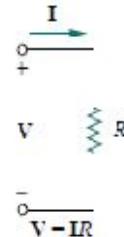
$$I = I_m \angle \phi \quad v = R I_m \angle \phi$$




(b) Inductor

$$i = I_m \cos(\omega t + \phi)$$


$$v = L(di/dt) = -\omega L I_m \sin(\omega t + \phi)$$

$$v = \omega L I_m \cos(\omega t + \phi + 90^\circ)$$
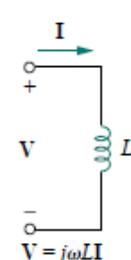
$$I = I_m \angle \phi \quad \text{and} \quad V = V_m \angle \phi + 90^\circ$$



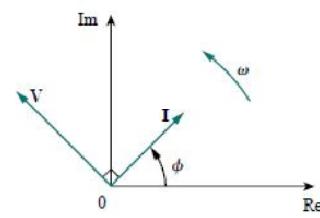The voltage lead the current by $90^\circ \rightarrow X_L = j \omega L$




(b) capacitor

$$v(t) = V_m \cos(\omega t + \phi) \quad i = C \frac{dv}{dt}$$


$$i = C \frac{d}{dt} V_m \cos(\omega t + \phi) = -\omega C V_m \sin(\omega t + \phi)$$

$$i = \omega C V_m \cos(\omega t + \phi + 90^\circ)$$
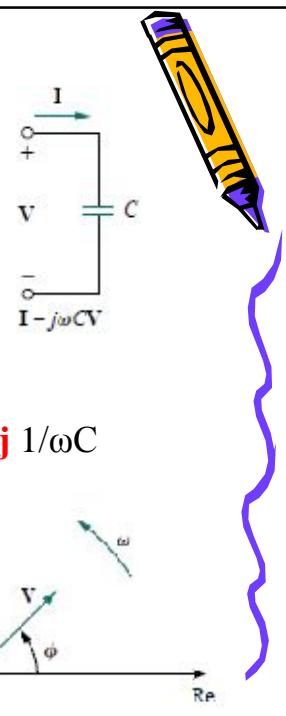
$$V = V_m \angle \phi \quad I = I_m \angle \phi + 90^\circ$$



The voltage lags the current by $90^\circ \rightarrow X_C = -j \frac{1}{\omega C}$

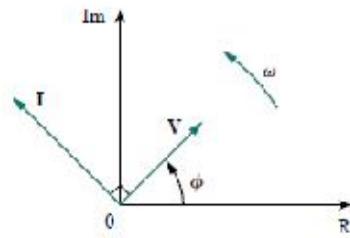**Impedance and Admittance**

$$Z = R + jX = |Z| \angle \theta \quad |Z| = \sqrt{R^2 + X^2}, \quad \theta = \tan^{-1} \frac{X}{R}$$

$$R = |Z| \cos \theta, \quad X = |Z| \sin \theta$$

$$Y = \frac{1}{Z} = \frac{I}{V} \quad Y = G + jB \quad G + jB = \frac{1}{R + jX}$$


$$G + jB = \frac{1}{R + jX} \cdot \frac{R - jX}{R - jX} = \frac{R - jX}{R^2 + X^2}$$

$$G = \frac{R}{R^2 + X^2}, \quad B = \frac{-X}{R^2 + X^2}$$

G conductance, B susceptance



Series Circuit

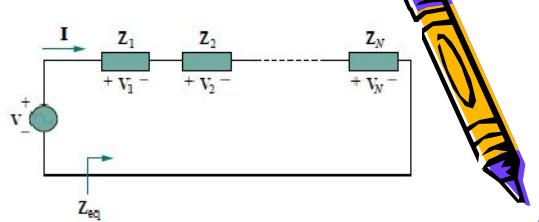


$$V = V_1 + V_2 + \dots + V_N = I(Z_1 + Z_2 + \dots + Z_N)$$

$$Z_{eq} = \frac{V}{I} = Z_1 + Z_2 + \dots + Z_N$$


$$I = \frac{V}{Z_1 + Z_2}$$

Since $V_1 = Z_1 I$ and $V_2 = Z_2 I$, then
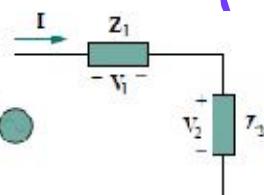
$$V_1 = \frac{Z_1}{Z_1 + Z_2} V, \quad V_2 = \frac{Z_2}{Z_1 + Z_2} V$$



Parallel Circuit

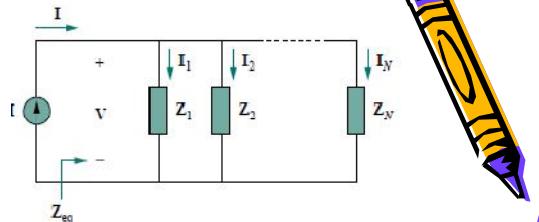


$$I = I_1 + I_2 + \dots + I_N = V \left(\frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_N} \right)$$

$$\frac{1}{Z_{eq}} = \frac{I}{V} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_N} \quad Y_{eq} = Y_1 + Y_2 + \dots + Y_N$$


$$Z_{eq} = \frac{1}{Y_{eq}} = \frac{1}{Y_1 + Y_2} = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2}} = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

$$V = I Z_{eq} = I_1 Z_1 = I_2 Z_2$$
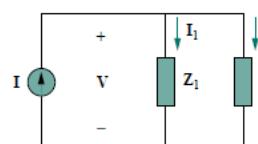
$$I_1 = \frac{Z_2}{Z_1 + Z_2} I, \quad I_2 = \frac{Z_1}{Z_1 + Z_2} I$$



Δ - Y -Conversion

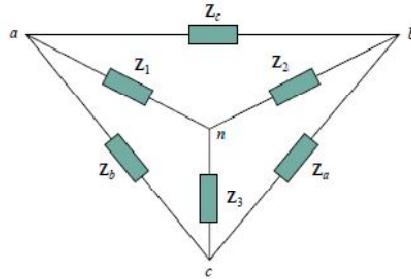

Y- Δ Conversion:

$$\left| \begin{array}{l} \mathbf{Z}_a = \frac{\mathbf{Z}_1 \mathbf{Z}_2 + \mathbf{Z}_2 \mathbf{Z}_3 + \mathbf{Z}_3 \mathbf{Z}_1}{\mathbf{Z}_1} \\ \mathbf{Z}_b = \frac{\mathbf{Z}_1 \mathbf{Z}_2 + \mathbf{Z}_2 \mathbf{Z}_3 + \mathbf{Z}_3 \mathbf{Z}_1}{\mathbf{Z}_2} \\ \mathbf{Z}_c = \frac{\mathbf{Z}_1 \mathbf{Z}_2 + \mathbf{Z}_2 \mathbf{Z}_3 + \mathbf{Z}_3 \mathbf{Z}_1}{\mathbf{Z}_3} \end{array} \right|$$

Δ -Y Conversion:

$$\left| \begin{array}{l} \mathbf{Z}_1 = \frac{\mathbf{Z}_b \mathbf{Z}_c}{\mathbf{Z}_a + \mathbf{Z}_b + \mathbf{Z}_c} \\ \mathbf{Z}_2 = \frac{\mathbf{Z}_c \mathbf{Z}_a}{\mathbf{Z}_a + \mathbf{Z}_b + \mathbf{Z}_c} \\ \mathbf{Z}_3 = \frac{\mathbf{Z}_a \mathbf{Z}_b}{\mathbf{Z}_a + \mathbf{Z}_b + \mathbf{Z}_c} \end{array} \right|$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$V_{av} = \frac{1}{T} \int_0^T v(t) dt$$

Ex.5: consider the circuit,

- Calculate the sinusoidal voltages v_1 and v_2 using phasors and voltage divider rule
- Sketch the phasor diagram showing E , V_1 and V_2 .
- Sketch the sinusoidal waveforms of e , v_1 and v_2 .

Solution:

(a) The phasor form of the voltage source is determined as


$$e = 100 \sin(\omega t) \Leftrightarrow E = 70.71 \angle 0^\circ V$$

$$V_1 = \left(\frac{40 - j80}{(40 - j80) + (30 + j40)} \right) (70.71 \angle 0^\circ) = 78.4 \angle -33.69^\circ V$$

and

$$V_2 = \left(\frac{30 + j40}{(40 - j80) + (30 + j40)} \right) (70.71 \angle 0^\circ) = 43.9 \angle 82.87^\circ V$$

(b) Phasor diagram

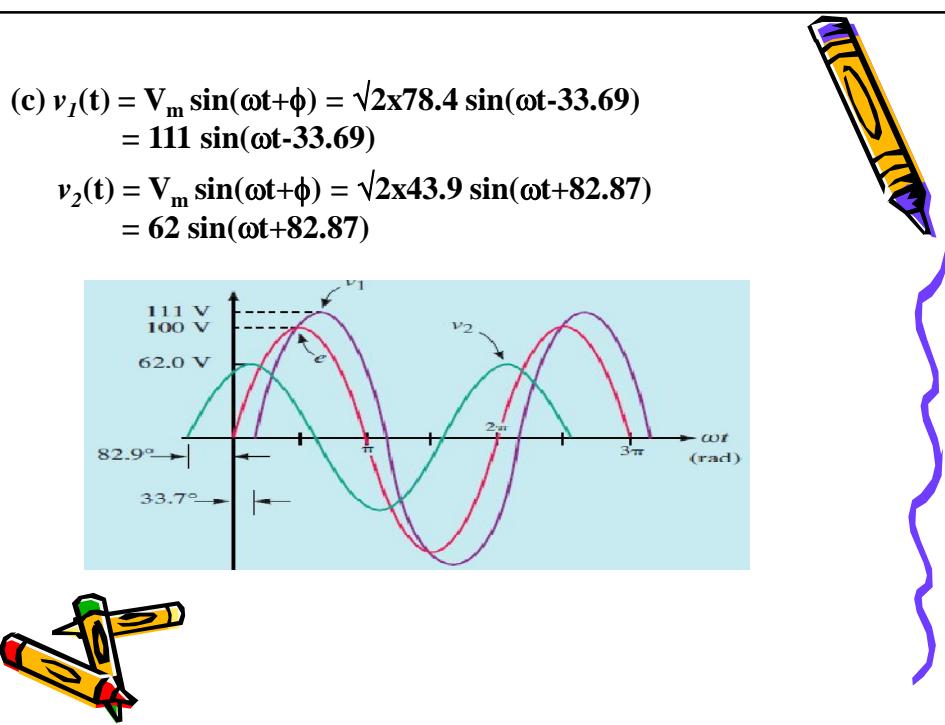

Ex. 6: Refer to the circuit;

- Find the total impedance, Z_T**
- Determine the supply current, I_T**
- Calculate I_1 , I_2 , using current divider rule.**
- Verify Kirchhoff's current law at node a.**

Solution

$$a. \frac{1}{Z_T} = \frac{1}{20} + \frac{1}{j1} + \frac{1}{-j1} = \frac{1}{20} \quad Z_T = 20\angle 0^\circ k\Omega$$


$$b. I_T = \frac{V}{Z_T} = \frac{5\angle 0^\circ}{20\angle 0^\circ} = 250 \times 10^{-6} \angle 0^\circ A = 250\angle 0^\circ \mu A$$

$$c. I_1 = \frac{20\angle 0^\circ}{20\angle 0^\circ} \times 250\angle 0^\circ = 250\angle 0^\circ \mu A$$

$$I_2 = \frac{20\angle 0^\circ}{1\angle 90^\circ} \times 250\angle 0^\circ = 5000\angle -90^\circ \mu A$$

$$I_3 = \frac{20\angle 0^\circ}{1\angle -90^\circ} \times 250\angle 0^\circ = 5000\angle 90^\circ \mu A$$

 d. $I_1 + I_2 + I_3 = 250\angle 0^\circ + 5000\angle -90^\circ + 5000\angle 90^\circ = 250\angle 0^\circ$
 $\therefore I_T = I_1 + I_2 + I_3 \therefore$ Kirchhoff's current law is verified.

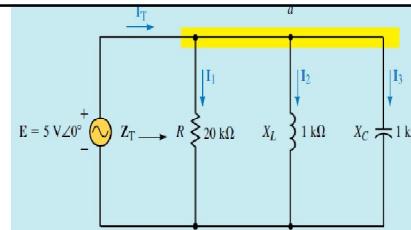**Ex. 7: Find the current I in the circuit.****Solution:**



$$Z_{an} = \frac{j4(2-j4)}{j4+2-j4+8} = \frac{16+j8}{10} = 1.6 + j0.8 \Omega$$

$$Z_{bn} = \frac{j4(8)}{10} = j3.2 \Omega \quad Z_{cn} = \frac{8(2-j4)}{10} = 1.6 - j3.2 \Omega$$

$$Z_1 = Z_{an} + 12 = 13.6 + j0.8 \quad , \quad Z_2 = Z_{bn} - j3 = j0.2 \quad \text{and} \quad Z_3 = Z_{cn} + j6 + 8 = 9.6 + j2.8$$

$$Z_T = Z_1 + \frac{Z_2 Z_3}{Z_2 + Z_3} = 13.6 + j0.8 + \frac{j0.2(9.6 + j2.8)}{9.6 + j3} = 13.6 + j1 \Omega$$
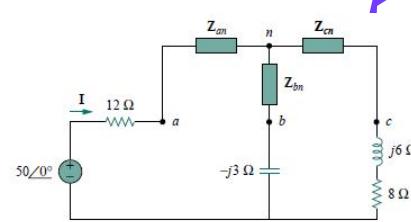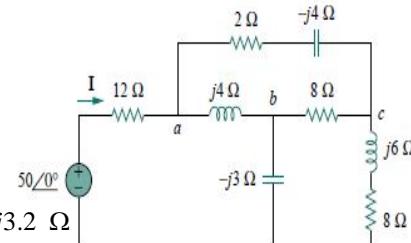
$$\text{The source current } I = \frac{V}{Z_T} = \frac{50\angle 0^\circ}{13.6 + j1} = 3.666\angle -4.2^\circ \Omega$$




AC Bridges

At balance $V_1=V_2$

$$V_1 = V_s \frac{Z_2}{Z_1 + Z_2} \quad V_2 = V_s \frac{Z_x}{Z_3 + Z_x}$$

$$\frac{Z_2}{Z_1 + Z_2} = \frac{Z_x}{Z_3 + Z_x}$$

$$\therefore Z_x = \frac{Z_3}{Z_1} Z_2$$

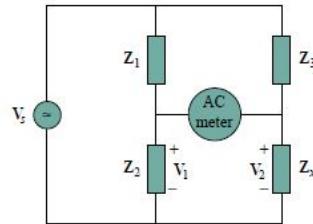


Series Resonance

$$Z = R + j(\omega L - \frac{1}{\omega C})$$

$$\text{At resonance} \quad \text{Im}(z) = 0$$
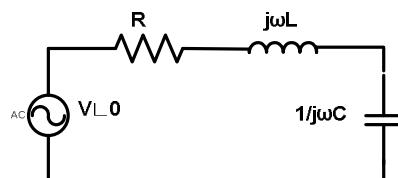
$$\omega L - \frac{1}{\omega C} = 0 \quad \omega_o L = \frac{1}{\omega_o C}$$



$$\omega_o = \frac{1}{\sqrt{LC}} \text{ rad/s}$$

$$f_o = \frac{1}{2\pi\sqrt{LC}} \text{ Hz}$$

$$|I| = \frac{V}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

The highest power is at ω_0


$$P(\omega_0) = I^2 R = \frac{V^2}{R}$$

The half power frequencies are at:

$$I = \frac{I}{\sqrt{2}} = 0.707I$$

$$P(\omega_1) = P(\omega_2) = \frac{1}{2} \frac{V^2}{R}$$

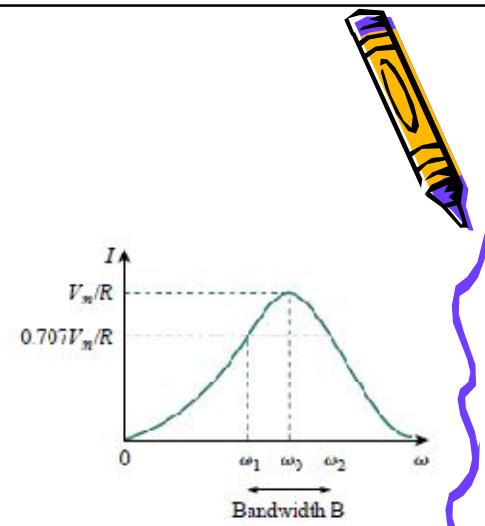ω_1 & ω_2 can be get by setting $Z = \sqrt{2}R$




$$\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2} = \sqrt{2}R$$

$$\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2} = \sqrt{2}R$$

By solving the above equation for ω

$$\omega_1 = \frac{-R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$
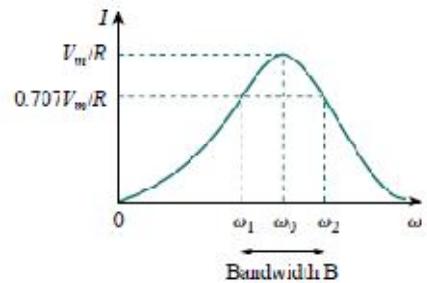
$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$



Bandwidth "It is defined as the half power bandwidth"

$$B = \omega_2 - \omega_1 = (R/L)$$

$$\omega_o = \sqrt{\omega_1 \omega_2}$$



Quality Factor Q


"Measure the sharpness of resonance "

$$Q = 2\pi \frac{\text{Peak energy stored in the circuit}}{\text{Energy dissipated by the circuit}}$$

$$Q = 2\pi \frac{\frac{1}{2}LI^2}{\frac{1}{2}I^2R(1/f)} = \frac{2\pi fL}{R}$$

$$Q = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 C R}$$

$$B = \frac{R}{L} = \frac{\omega_0}{Q}$$

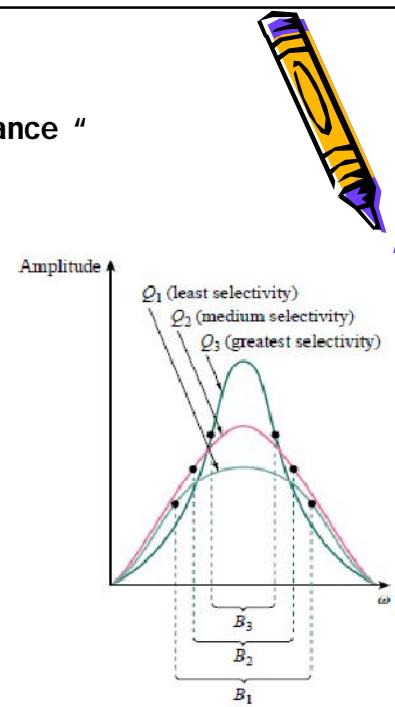

A resonant circuit is designed to operate at or near its resonant frequency.

For high- Q circuits ($Q \geq 10$)

$$\omega_1 \approx \omega_0 - \frac{R}{2}, \quad \omega_2 \approx \omega_0 + \frac{R}{2}$$

Example: For the circuit shown:

- Find the resonant frequency and the half power frequencies
- Calculate the quality factor and bandwidth
- Determine the amplitude of the current at ω_0 , ω_1 and ω_2

Solution

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-3} \times 0.4 \times 10^{-6}}} = 50 \text{ krad/s}$$


$$\begin{aligned}\omega_1 &= -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \\ &= -\frac{2}{2 \times 10^{-3}} + \sqrt{(10^3)^2 + (50 \times 10^3)^2}\end{aligned}$$

$$= -1 + \sqrt{1 + 2500} \text{ krad/s} = 49 \text{ krad/s}$$

$$Q = \frac{\omega_0}{B} = \frac{50}{2} = 25$$

At $\omega = \omega_0$,

At $\omega = \omega_1, \omega_2$,

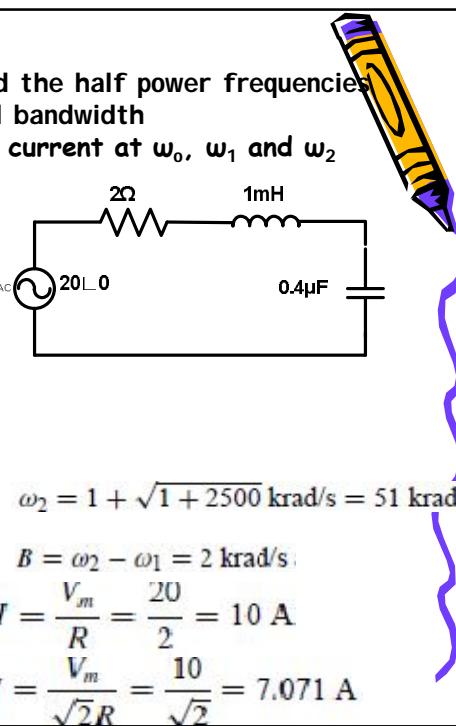

$$\omega_2 = 1 + \sqrt{1 + 2500} \text{ krad/s} = 51 \text{ krad/s}$$

$$B = \omega_2 - \omega_1 = 2 \text{ krad/s}$$

$$I = \frac{V_m}{R} = \frac{20}{2} = 10 \text{ A}$$


$$I = \frac{V_m}{\sqrt{2}R} = \frac{10}{\sqrt{2}} = 7.071 \text{ A}$$

Parallel Resonance

$$\mathbf{Y} = \frac{1}{R} + j \left(\omega C - \frac{1}{\omega L} \right)$$

At resonance $\text{Im}(Y)=0$
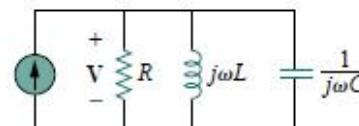
$$\omega C - \frac{1}{\omega L} = 0 \quad \omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/s}$$



At resonance:

(1) The parallel LC combination acts like open circuit.
i.e. the entire current flows through R

(2) The inductor and capacitor currents can be much
more than the source current

$$\omega_1 = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

$$\omega_2 = \frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$


$$B = \omega_2 - \omega_1 = \frac{1}{RC}$$

$$Q = \frac{\omega_0}{B} = \omega_0 RC = \frac{R}{\omega_0 L}$$

$$\omega_1 = \omega_0 \sqrt{1 + \left(\frac{1}{2Q}\right)^2 - \frac{\omega_0}{2Q}}, \quad \omega_2 = \omega_0 \sqrt{1 + \left(\frac{1}{2Q}\right)^2 + \frac{\omega_0}{2Q}}$$

for high-Q circuits ($Q \geq 10$)
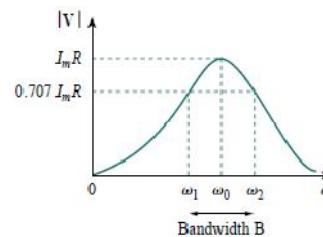
$$\omega_1 \simeq \omega_0 - \frac{B}{2}, \quad \omega_2 \simeq \omega_0 + \frac{B}{2}$$





Example: For the circuit shown:

(a) Calculate ω_0 , Q and B

(b) Find ω_1 and ω_2

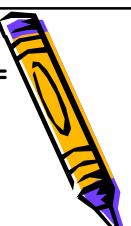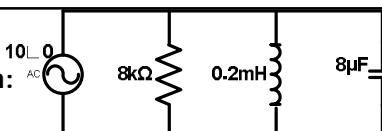(c) Determine the power dissipated at ω_0 , ω_1 and ω_2



Solution


$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.2 \times 10^{-3} \times 8 \times 10^{-6}}} = \frac{10^5}{4} = 25 \text{ krad/s}$$

$$Q = \frac{R}{\omega_0 L} = \frac{8 \times 10^3}{25 \times 10^3 \times 0.2 \times 10^{-3}} = 1600$$

$$B = \frac{\omega_0}{Q} = 15.625 \text{ rad/s}$$

$$\omega_1 = \omega_0 - \frac{B}{2} = 25,000 - 7.8125 = 24,992 \text{ rad/s}$$
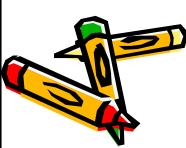
$$\omega_2 = \omega_0 + \frac{B}{2} = 25,000 + 7.8125 = 25,008 \text{ rad/s}$$



At $\omega = \omega_0$, $\mathbf{Y} = 1/R$ or $\mathbf{Z} = R = 8 \text{ k}\Omega$.

$$\mathbf{I}_o = \frac{\mathbf{V}}{\mathbf{Z}} = \frac{10 \angle -90^\circ}{8000} = 1.25 \angle -90^\circ \text{ mA}$$

at $\omega = \omega_0$ $P = I_o^2 R = (1.25 \times 10^{-3})^2 (8000) = 12.5 \times 10^{-3} W$

At $\omega = \omega_1, \omega_2$, $P = \frac{V^2}{2R} = \frac{10^2}{2 \times 8000} = 6.25 \times 10^{-3} W$

