

ECE121: Electronics (1)

Lecture 1: Regulated Power Supply

Dr. Haitham El-Hussey

Electronics and Communications Engineering
Faculty of Engineering (Shoubra)
Benha University



Spring 2017

Lecture Outline:

- 1 Introduction.
- 2 Concept of Voltage Regulation.
- 3 A Zener-Regulated DC Power Supply.
- 4 Basic Linear Voltage Regulator.
- 5 Integrated Circuit Voltage Regulators.

Table of Contents

- 1 Introduction.
- 2 Concept of Voltage Regulation.
- 3 A Zener-Regulated DC Power Supply.
- 4 Basic Linear Voltage Regulator.
- 5 Integrated Circuit Voltage Regulators.

Introduction:

DC Power supply:

- Around 95% of the electronic equipments are powered from low voltage DC supplies.

Introduction:

DC Power supply:

- Around 95% of the electronic equipments are powered from low voltage DC supplies.
- The source will be either a battery or a power supply converting AC mains into one or more low voltage DC supplies.

Introduction:


DC Power supply:

- Around 95% of the electronic equipments are powered from low voltage DC supplies.
- The source will be either a battery or a power supply converting AC mains into one or more low voltage DC supplies.
- Electronic components require a DC supply that is **well regulated**, has **low noise characteristics** and provides a **fast response to load changes**.



Introduction:


Components of DC Power Supplies:

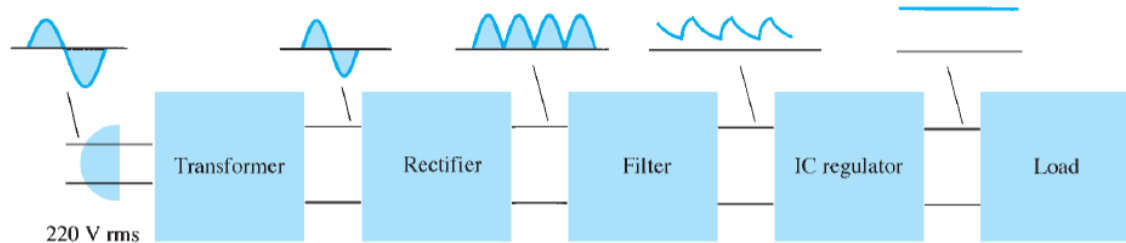

- 1 The AC voltage, typically 220 V RMS, is connected to a transformer, which steps that ac voltage down to the level for the desired dc output.

Introduction:


Components of DC Power Supplies:

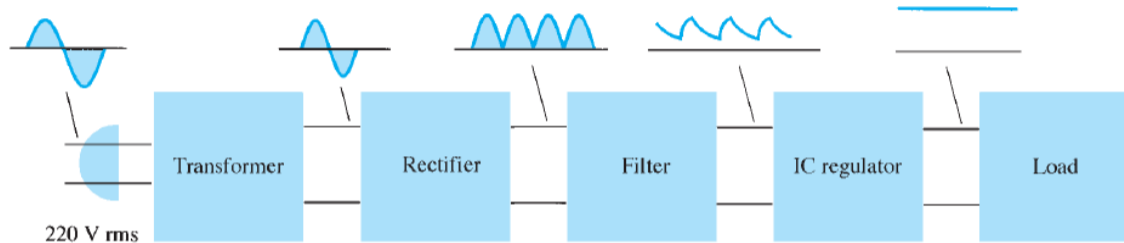

- 1 The AC voltage, typically 220 V RMS, is connected to a transformer, which steps that ac voltage down to the level for the desired dc output.
- 2 A diode rectifier then provides a full-wave rectified voltage, which is initially filtered by a basic capacitor filter to produce a dc voltage.

Introduction:

Components of DC Power Supplies:

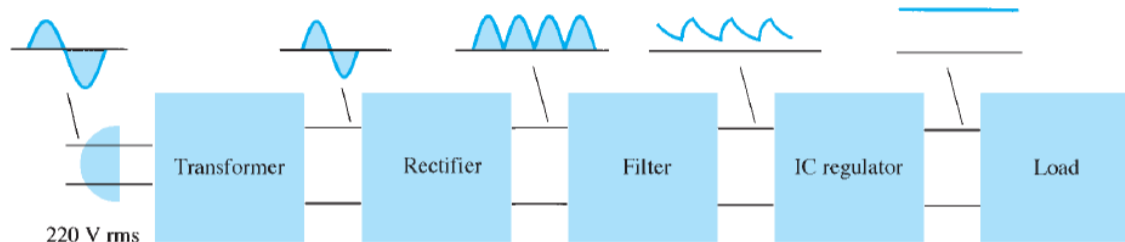


- 1 The AC voltage, typically 220 V RMS, is connected to a transformer, which steps that ac voltage down to the level for the desired dc output.
- 2 A diode rectifier then provides a full-wave rectified voltage, which is initially filtered by a basic capacitor filter to produce a dc voltage.
- 3 A regulator circuit can use this dc input to provide a dc voltage that **remains constant if input or load changes.**

Introduction:

Ideal Vs. Real DC Regulated Power Supply:

Ideal Power Supply:

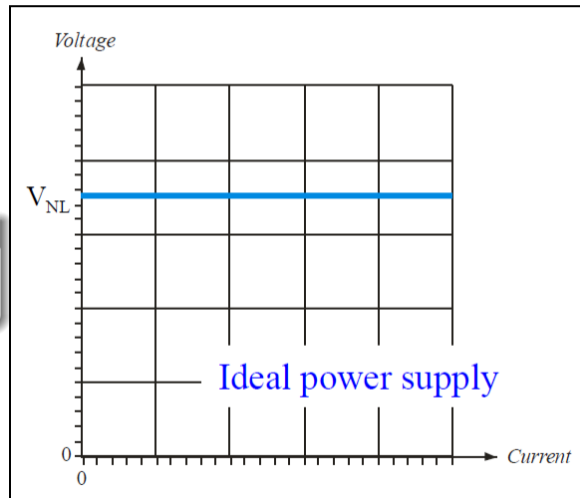It provides a constant dc voltage despite changes to the input voltage or load conditions.



Introduction:

Ideal Vs. Real DC Regulated Power Supply:

Real Power Supply:

The output voltage of a real power supply changes under load or line (input) change.


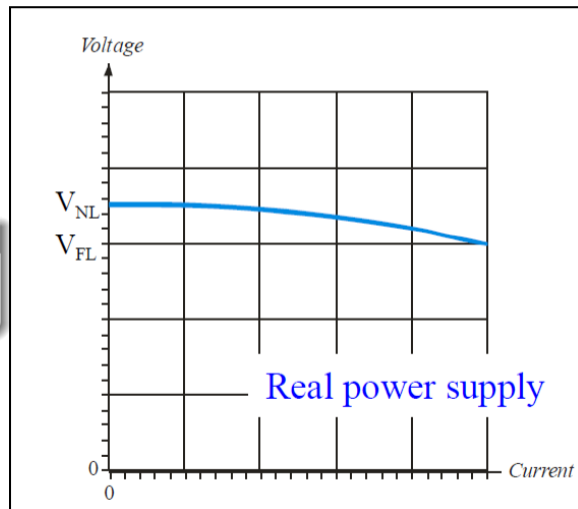


Table of Contents

- 1 Introduction.
- 2 Concept of Voltage Regulation.**
- 3 A Zener-Regulated DC Power Supply.
- 4 Basic Linear Voltage Regulator.
- 5 Integrated Circuit Voltage Regulators.

Concept of Voltage Regulation:

Line Regulation:

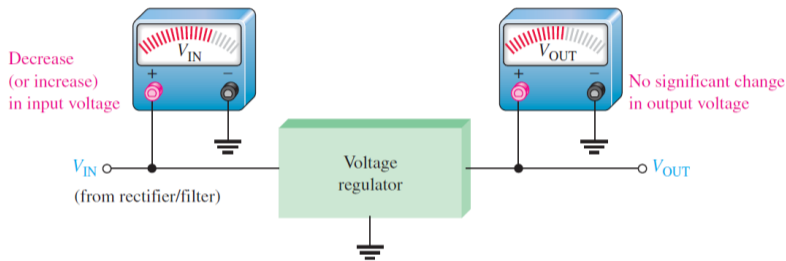

Line Regulation:

It is the percentage change in the output voltage for a given change in the input voltage. It can be expressed in units of (%/V).

$$\text{Line regulation} = \frac{(\Delta V_{OUT}/V_{OUT})100\%}{\Delta V_{IN}}$$

Concept of Voltage Regulation:

Line Regulation:

Line Regulation: (Example)

When the ac input voltage of a certain power supply changes, the input to the voltage regulator decreases by 5 V as a result, and the output of the regulator decreases by 0.25 V. The nominal output is 15 V. Determine the line regulation in %/V.


Solution:

The line regulation as a percentage change per volt is:

$$\text{Line regulation} = \frac{(\Delta V_{out}/V_{out})100\%}{\Delta V_{in}} = \frac{(0.25 \text{ V}/15 \text{ V})100\%}{5 \text{ V}} = 0.333\%/V$$

Concept of Voltage Regulation:

Load Regulation:

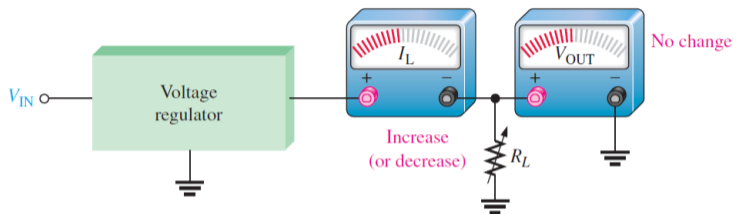

Load Regulation:

It is the percentage change in output voltage for a given change in load current.

One way to express load regulation is as a percentage change in output voltage from no-load (NL) to full-load (FL).

$$\text{Load regulation} = \left(\frac{V_{NL} - V_{FL}}{V_{FL}} \right) 100\%$$

Concept of Voltage Regulation:

Load Regulation:

Load Regulation: (Example)

A certain voltage regulator has a 12 V output when there is no load. When there is a full-load output voltage is 11.9 V. Express the voltage regulation as a percentage change from no-load to full-load.

Solution:

The load regulation as a percentage change from no-load to full-load is:



$$\text{Load regulation} = \frac{(V_{NL} - V_{FL})}{V_{FL}} 100\% = \frac{(12 \text{ V} - 11.9 \text{ V})}{11.9 \text{ V}} 100\% = 0.840\%$$

Table of Contents

- 1 Introduction.
- 2 Concept of Voltage Regulation.
- 3 A Zener-Regulated DC Power Supply.**
- 4 Basic Linear Voltage Regulator.
- 5 Integrated Circuit Voltage Regulators.



A Zener-Regulated DC Power Supply:

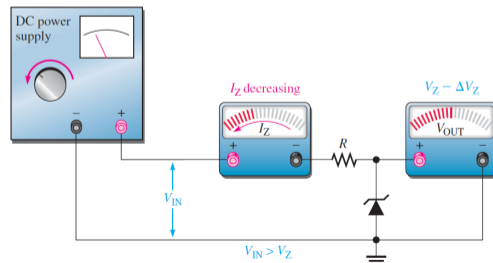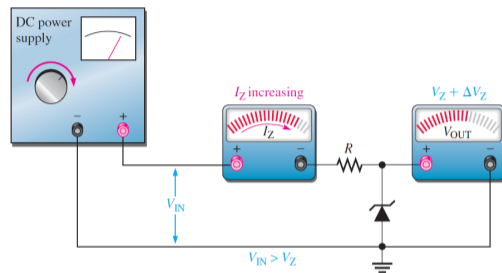- The zener diode can be used as a type of voltage regulator for providing stable reference voltages.





A Zener-Regulated DC Power Supply:

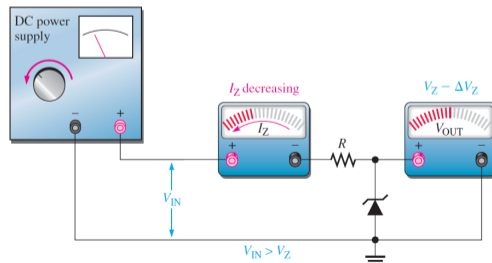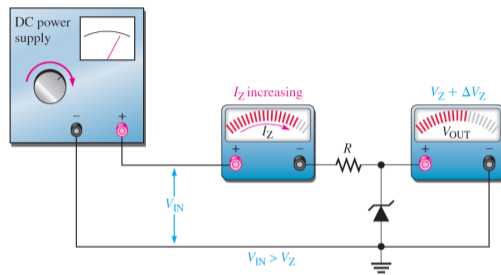- The zener diode can be used as a type of voltage regulator for providing stable reference voltages.
- As the input voltage varies (within limits), the zener diode maintains a nearly constant output voltage across its terminals.




A Zener-Regulated DC Power Supply:

- The zener diode can be used as a type of voltage regulator for providing stable reference voltages.
- As the input voltage varies (within limits), the zener diode maintains a nearly constant output voltage across its terminals.
- However, as V_{IN} changes, I_Z will change proportionally so that the limitations on the input voltage variation are set by the minimum and maximum current values (I_{ZK} and I_{ZM}) with which the zener can operate.

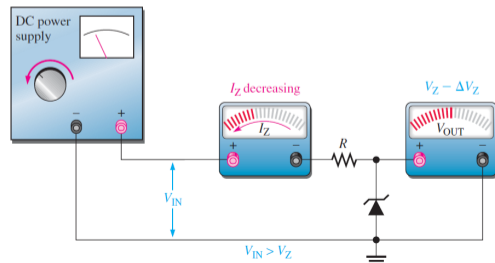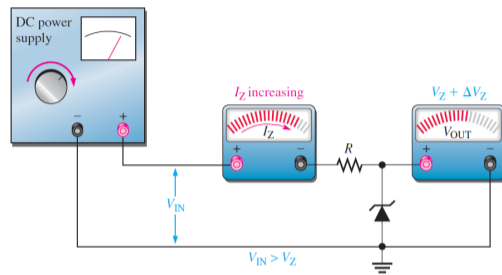

A Zener-Regulated DC Power Supply:

At No-load

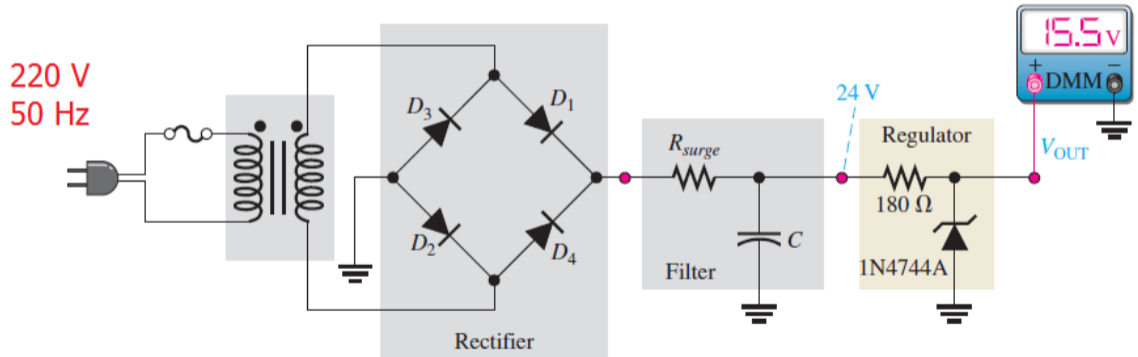

A Zener-Regulated DC Power Supply:

At Full-load


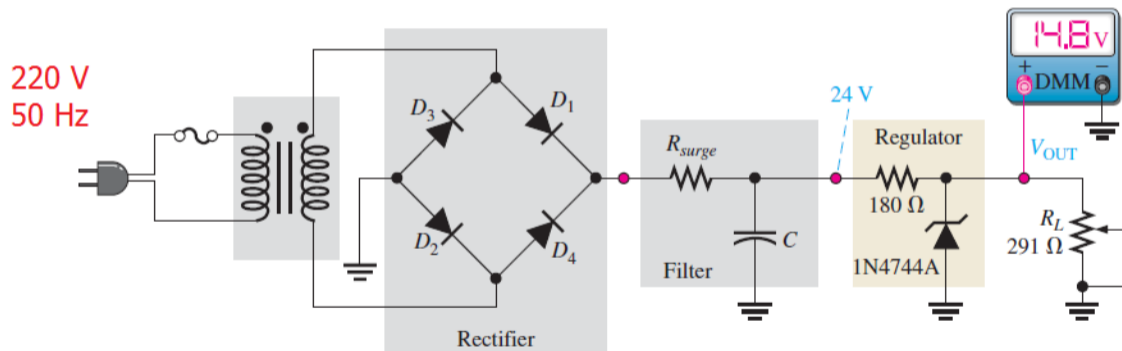


Table of Contents

- 1 Introduction.
- 2 Concept of Voltage Regulation.
- 3 A Zener-Regulated DC Power Supply.
- 4 Basic Linear Voltage Regulator.**
- 5 Integrated Circuit Voltage Regulators.


Basic Linear Voltage Regulator:

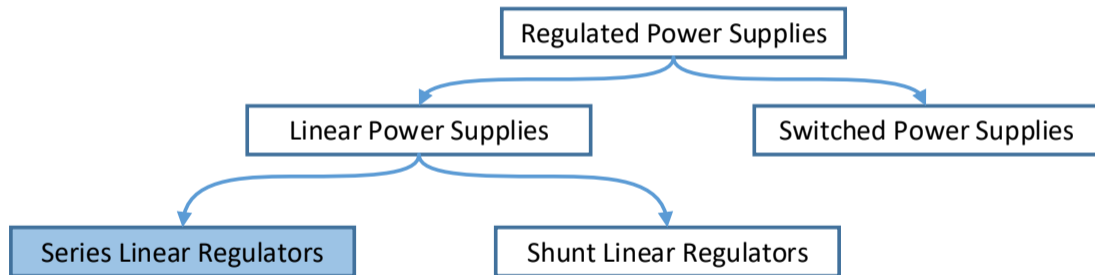

Basic Linear Voltage Regulator:

Series Linear VR:

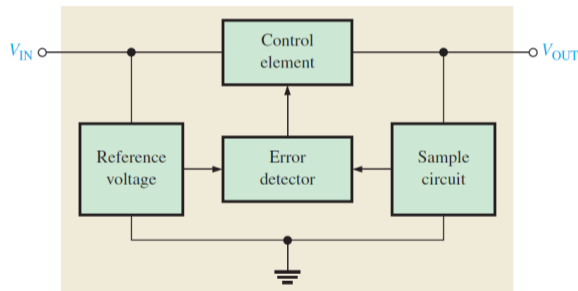- The control element is a pass transistor in series with the load between the input and output.




Simple series voltage regulator

Basic Linear Voltage Regulator:

Series Linear VR:

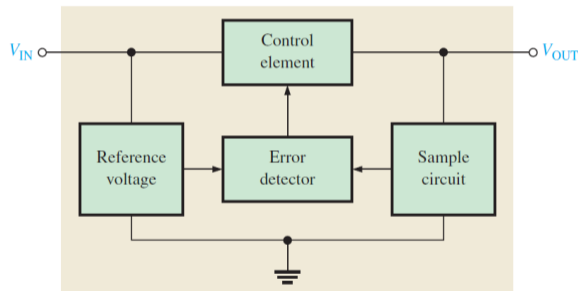- The control element is a pass transistor in series with the load between the input and output.
- The output sample circuit senses a change in the output voltage.




Simple series voltage regulator

Basic Linear Voltage Regulator:

Series Linear VR:

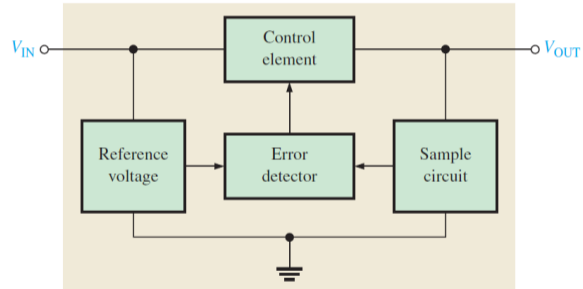
- The control element is a pass transistor in series with the load between the input and output.
- The output sample circuit senses a change in the output voltage.
- The error detector compares the sample voltage with a reference voltage and causes the control element to compensate in order to maintain a constant output voltage.



Simple series voltage regulator

Basic Linear Voltage Regulator:

Series Linear VR:

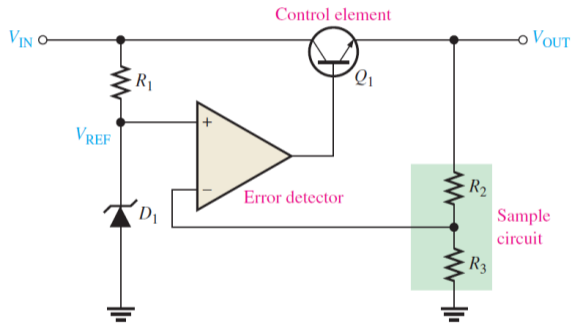

Basic op-amp series regulator

- The resistive voltage divider senses any change in the output voltage.
- The op-amp circuit amplifies the difference voltage (error voltage) between the reference and the sensed values.
- This amplified difference voltage is applied to the transistor Q_1 to make the load voltage equal to the reference.




$$V_{\text{OUT}} \cong \left(1 + \frac{R_2}{R_3} \right) V_{\text{REF}}$$

Table of Contents

- 1 Introduction.
- 2 Concept of Voltage Regulation.
- 3 A Zener-Regulated DC Power Supply.
- 4 Basic Linear Voltage Regulator.
- 5 Integrated Circuit Voltage Regulators.**

Integrated Circuit Voltage Regulators:

- Integrated circuit voltage regulators are available as series regulators.
- The IC regulator contains the reference voltage, the error detector and the control unit in one package.

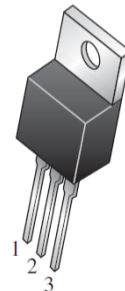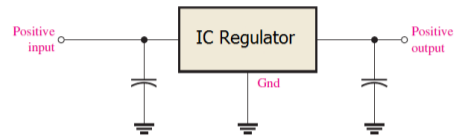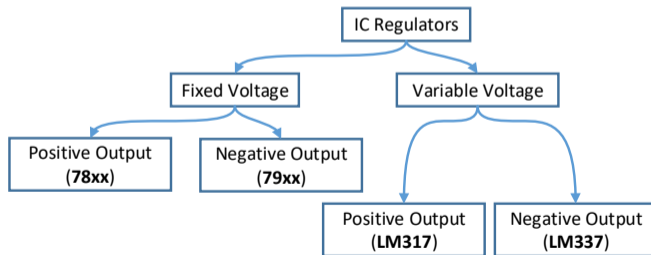


Pin 1. Input
2. Ground
3. Output

Heatsink surface
connected to Pin 2.

Integrated Circuit Voltage Regulators:

Fixed Positive Linear Regulator (78xx)

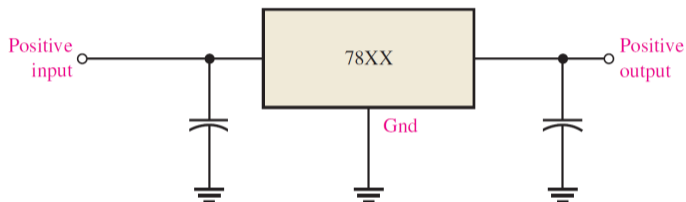


- The last two digits in the part number designate the output voltage. For example, the 7805 is a 5 V regulator.

Type number	Output voltage
7805	+5.0 V
7806	+6.0 V
7808	+8.0 V
7809	+9.0 V
7812	+12.0 V
7815	+15.0 V
7818	+18.0 V
7824	+24.0 V

The 78XX series

Integrated Circuit Voltage Regulators:

Fixed Negative Linear Regulator (79xx)

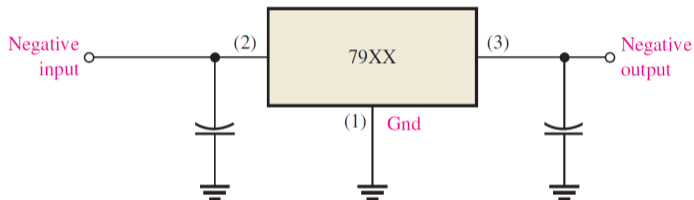


- The last two digits in the part number designate the output voltage. For example, the 7905 is a -5 V regulator.

Type number	Output voltage
7905	-5.0 V
7905.2	-5.2 V
7906	-6.0 V
7908	-8.0 V
7912	-12.0 V
7915	-15.0 V
7918	-18.0 V
7924	-24.0 V

The 79XX series

Integrated Circuit Voltage Regulators:

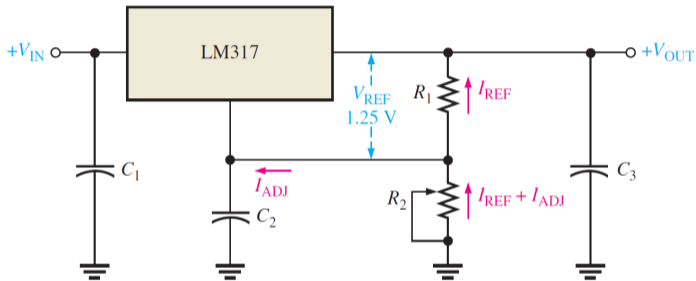Variable Positive Linear Regulator (LM317)




$$V_{\text{OUT}} = V_{\text{REF}} \left(1 + \frac{R_2}{R_1} \right) + I_{\text{ADJ}} R_2$$

- The external fixed resistor R_1 and the external variable resistor R_2 provide the output voltage adjustment.
- The output can be varied from 1.2 V to 37 V depending on the resistor values.
- The LM317 can provide over 1.5 A of output current to a load.
- We can neglect I_{ADJ} which is small $50 \mu\text{A}$.

Integrated Circuit Voltage Regulators:

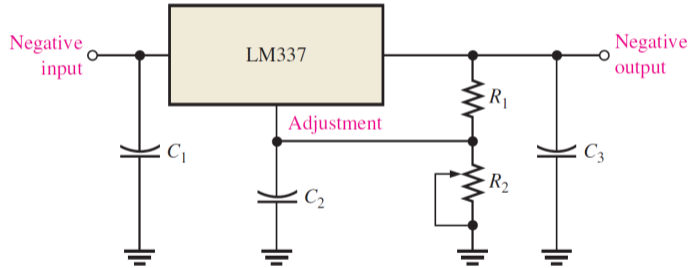Variable Negative Linear Regulator (LM337)




- The external fixed resistor R_1 and the external variable resistor R_2 provide the output voltage adjustment.
- The output can be varied from -1.2 V to -37 V depending on the resistor values.
- The LM337 can provide over 1.5 A of output current to a load.
- We can neglect I_{ADG} which is small $50\ \mu\text{A}$.

Integrated Circuit Voltage Regulators:

Power Supply Project:

Example of a typical 12 V power supply:

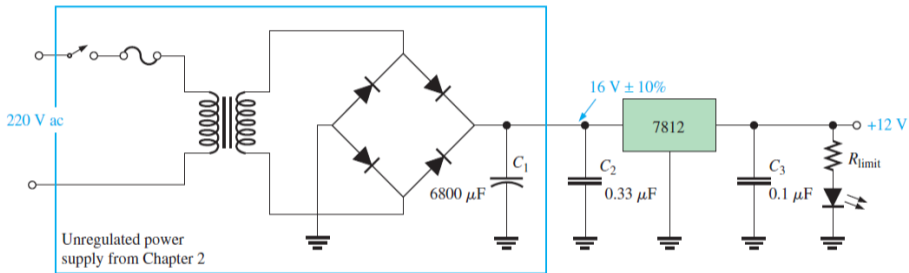

- Select one of the IC regulator and simulate it **individually** using Proteus. Send it by **Sunday 19 Feb. 2017.**
- Each team (one to four members) should deliver a variable (+ve or -ve) power supply by **Sunday 26 Feb. 2017.**

End of Lecture

Best Wishes

haitham.elhussieny@gmail.com