

# ECE121: Electronics (1)

## Lecture 7: Tunnel Diodes Diode AC Resistance

**Dr. Haitham El-Hussieny**

Electronics and Communications Engineering  
**Faculty of Engineering (Shoubra)**  
**Benha University**



Spring 2017

## Lecture Outline:

- 1 Tunnel Diodes.
- 2 Networks with AC and DC Sources.


# Table of Contents

1 Tunnel Diodes.

2 Networks with AC and DC Sources.
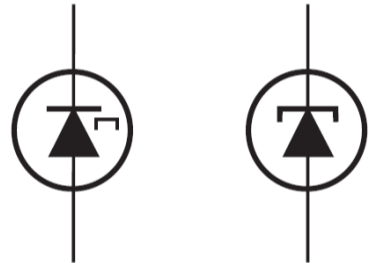
## Introduction:


- The tunnel diode was first introduced by *Leo Esaki* in 1958. It is mainly used in **low voltage high frequency applications**.



Tunnel diode Symbols
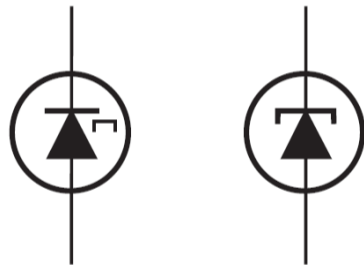
## Introduction:


- The tunnel diode was first introduced by *Leo Esaki* in 1958. It is mainly used in **low voltage high frequency applications**.
- It is fabricated by doping the semiconductor materials a level **100 to several thousand times** that of a typical semiconductor diode.



Tunnel diode Symbols
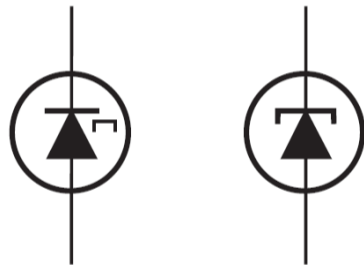
## Introduction:

- The tunnel diode was first introduced by *Leo Esaki* in 1958. It is mainly used in **low voltage high frequency applications**.
- It is fabricated by doping the semiconductor materials a level **100 to several thousand times** that of a typical semiconductor diode.
- This results a thin depletion region which many carriers can “**tunnel**” at low forward-bias potentials




Tunnel diode Symbols

## Introduction:

- The tunnel diode was first introduced by *Leo Esaki* in 1958. It is mainly used in **low voltage high frequency applications**.
- It is fabricated by doping the semiconductor materials a level **100 to several thousand times** that of a typical semiconductor diode.
- This results a thin depletion region which many carriers can “**tunnel**” at low forward-bias potentials
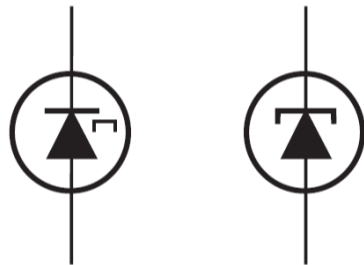
### Negative Resistance:


Tunnel diodes are different from any ordinary diode in that it has a negative-resistance region. In this region, an **increase in terminal voltage results in a reduction in diode current**.



Tunnel diode Symbols
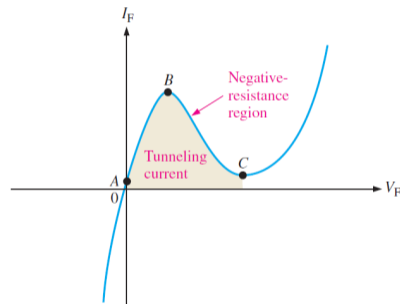
## Tunnel Diode Characteristic:

- Tunnel diodes are constructed with **germanium or gallium arsenide** by doping the p and n regions **much more heavily** than in a conventional diode.




Tunnel diode Characteristics


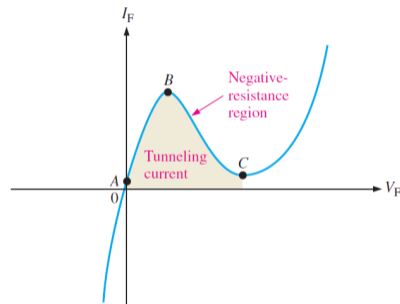
## Tunnel Diode Characteristic:


- Tunnel diodes are constructed with **germanium or gallium arsenide** by doping the p and n regions **much more heavily** than in a conventional diode.
- The heavy doping results in an extremely narrow depletion region.



Tunnel diode Characteristics
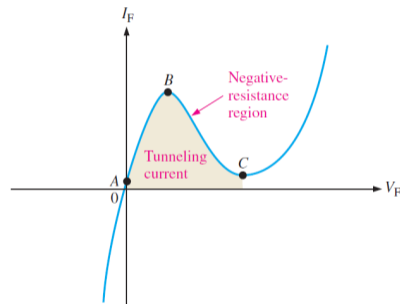
## Tunnel Diode Characteristic:


- Tunnel diodes are constructed with **germanium or gallium arsenide** by doping the p and n regions **much more heavily** than in a conventional diode.
- The heavy doping results in an extremely narrow depletion region.
- It allows conduction for all reverse voltages.



Tunnel diode Characteristics
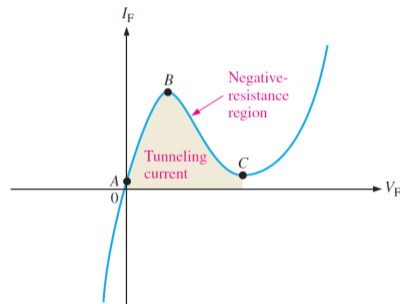
## Tunnel Diode Characteristic:


- Tunnel diodes are constructed with **germanium or gallium arsenide** by doping the p and n regions **much more heavily** than in a conventional diode.
- The heavy doping results in an extremely narrow depletion region.
- It allows conduction for all reverse voltages.
- Also, the extremely narrow depletion region allows electrons to “tunnel” through the pn junction at very low forward-bias voltages (point A to B)



Tunnel diode Characteristics
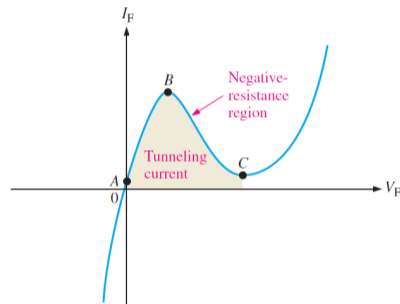
## Tunnel Diode Characteristic:


- Tunnel diodes are constructed with **germanium or gallium arsenide** by doping the p and n regions **much more heavily** than in a conventional diode.
- The heavy doping results in an extremely narrow depletion region.
- It allows conduction for all reverse voltages.
- Also, the extremely narrow depletion region allows electrons to “tunnel” through the pn junction at very low forward-bias voltages (point A to B)
- At point B, the forward voltage begins to decrease as the forward voltage continues to increase.



Tunnel diode Characteristics
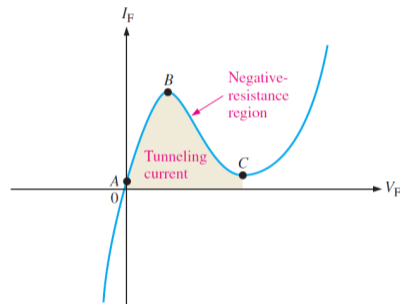
## Tunnel Diode Characteristic:

- Tunnel diodes are constructed with **germanium or gallium arsenide** by doping the p and n regions **much more heavily** than in a conventional diode.
- The heavy doping results in an extremely narrow depletion region.
- It allows conduction for all reverse voltages.
- Also, the extremely narrow depletion region allows electrons to “tunnel” through the pn junction at very low forward-bias voltages (point A to B)
- At point B, the forward voltage begins to decrease as the forward voltage continues to increase.
- At point C, the diode begins to act as a conventional forward biased diode.




Tunnel diode Characteristics


## Tunnel Diode Application:

A tunnel diode can be used to **generate a sinusoidal voltage using simply a dc supply and a resonant circuit.**
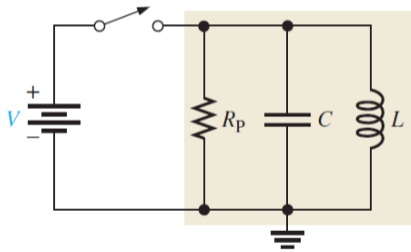
### [1] Resonant circuit without tunnel diode:



(a)

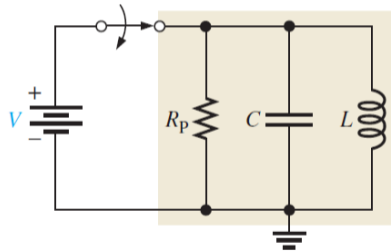


(b)

A damped sinusoidal output results

## Tunnel Diode Application:

A tunnel diode can be used to **generate a sinusoidal voltage using simply a dc supply and a resonant circuit.**
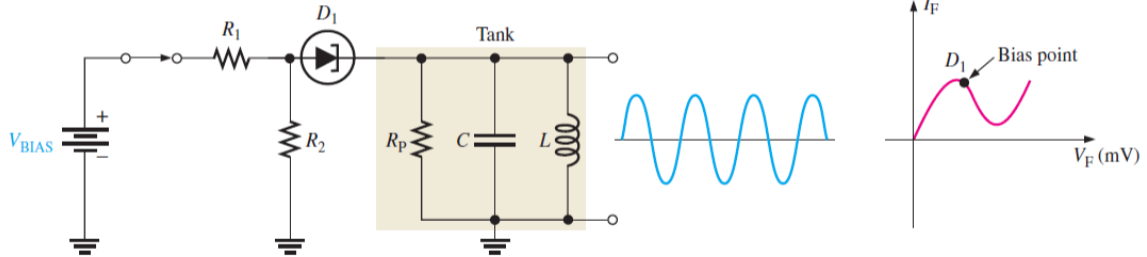
### [2] Resonant circuit with a tunnel diode:



A non-damped sinusoidal output results if the diode is biased **to work at the middle of the negative resistance region.**

# Table of Contents


1 Tunnel Diodes.

2 Networks with AC and DC Sources.


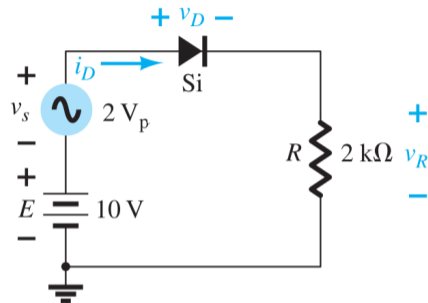
## Networks with AC and DC Sources:


- We need to analyze diode circuits in case of both a dc and an ac input source.
- We can solve for the two sources by using the **Superposition Theorem**.



Network with a dc and ac supply
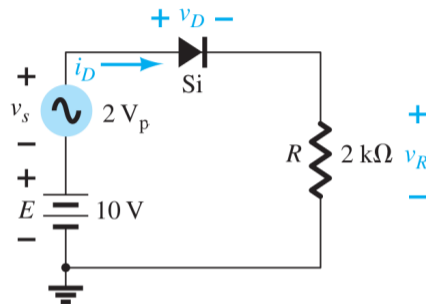
## Networks with AC and DC Sources:

- We need to analyze diode circuits in case of both a dc and an ac input source.
- We can solve for the two sources by using the **Superposition Theorem**.



Network with a dc and ac supply

### Superposition Theorem:

The response of any network with both an AC and a DC source can be found by finding the response to **each source independently** and then **combining the results**.

## Networks with AC and DC Sources:


### [1] DC Source Only:

- The **DC source is only applied** while the **AC source is removed** by replacing it with a **short-circuit**.
- Voltage across the  $R$ :

$$V_R = E - V_D = 10 \text{ V} - 0.7 \text{ V} = 9.3 \text{ V}$$

- Current  $I_D$ :
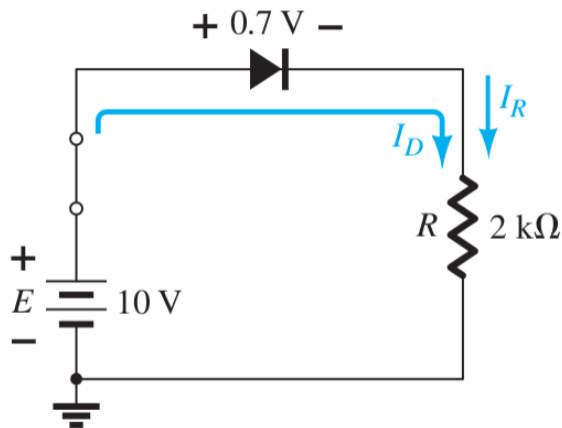
$$I_D = I_R = \frac{V_R}{R} = \frac{9.3 \text{ V}}{2 \text{ k}\Omega} = 4.65 \text{ mA}$$




Network with a DC source only

## Networks with AC and DC Sources:
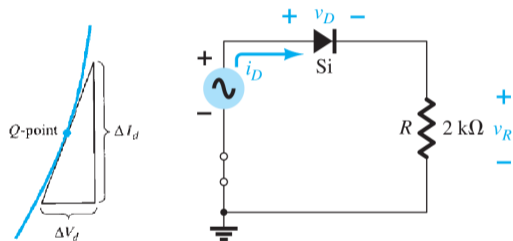
### [2] AC Source Only:

- The **AC source is only applied** while the **DC source is removed** by replacing it with a **short-circuit**.
- If a **sinusoidal rather than a DC input** is applied, the Q-Point will move up and down in a region of the characteristics.
- The change in current and voltage is specified by the **AC resistance**,  $r_D$ .
- The diode will be replaced by the **ac resistance**,  $r_D$ :



Network with an AC source only

$$r_D = \frac{\Delta V_d}{\Delta I_d}; \quad r_D = \frac{26 \text{ mV}}{I_D} = \frac{26 \text{ mV}}{4.65 \text{ mA}} = 5.59 \Omega$$


## Networks with AC and DC Sources:

### [2] AC Source Only:

- The Voltage  $V_{Rpeak}$  across the resistance  $R$  is:

$$V_{Rpeak} = \frac{2 \text{ k}\Omega}{2 \text{ k}\Omega + 5.59 \Omega} 2 \text{ V} \approx 1.99 \text{ V}$$
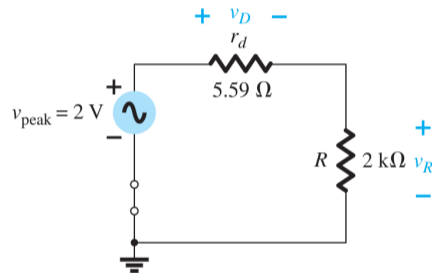
$$V_{Dpeak} = V_s - V_{Rpeak} = 2 \text{ V} - 1.99 \text{ V} = 10 \text{ mV}$$





Network with an AC source only

## Networks with AC and DC Sources:
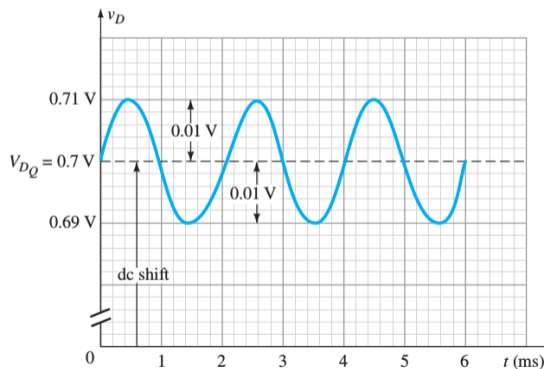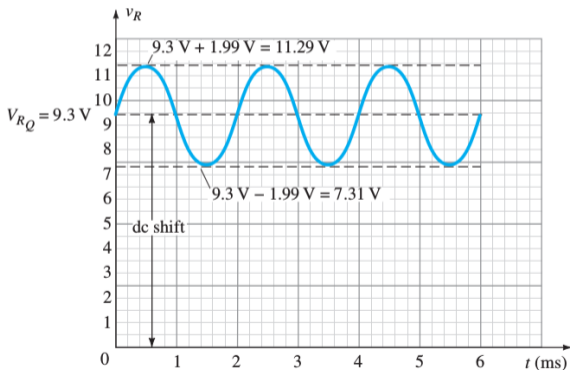
### [3] Combining both the AC and DC:

Combining the results of the DC and AC analysis will result in the waveforms for  $V_R$  and  $V_D$ :



# End of Lecture

Best Wishes

haitham.elhussieny@gmail.com