

ECE121: Electronics (1)

Lecture 7: Zener Diodes

Dr. Haitham El-Hussieny

Electronics and Communications Engineering
Faculty of Engineering (Shoubra)
Benha University



Spring 2017

Lecture Outline:


- 1 Introduction.
- 2 Fixed V_i , Fixed R_L .
- 3 Fixed V_i , Variable R_L .

Table of Contents

- 1 Introduction.
- 2 Fixed V_i , Fixed R_L .
- 3 Fixed V_i , Variable R_L .

Introduction:

- The Zener diode has three regions of operations. Each region has its own approximation model.
- It can be used as a part of protection circuit or as a voltage regulator.
- The use of the Zener diode as a regulator is so common that three conditions surrounding the analysis of the basic Zener regulator are considered:
 - ① Fixed load and fixed supply voltage.
 - ② Fixed supply voltage and variable load.
 - ③ Variable supply voltage and fixed load.
- The first case is already studied in the previous semester and will be briefly reviewed.

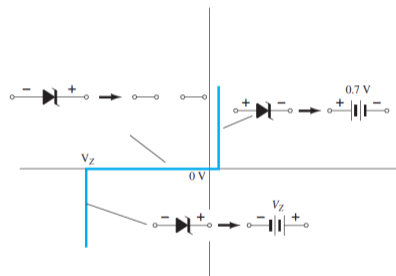

Zener diode characteristics

Table of Contents

- 1 Introduction.
- 2 Fixed V_i , Fixed R_L .
- 3 Fixed V_i , Variable R_L .


Fixed V_i , Fixed R_L :

Example

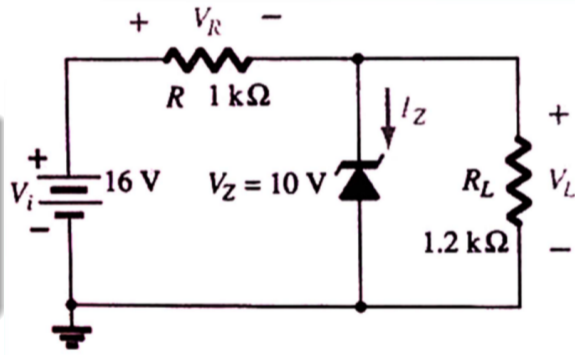Example

For the Zener diode regulator,

- 1 Determine V_L , V_R , I_Z and P_Z .
- 2 If the load is changed to $R_L = 3 \text{ k}\Omega$, repeat the above problem.



Example

Fixed V_i , Fixed R_L :

Solution:

- 1 Determine the voltage across the Zener diode to determine its state:

$$V_{zener} = V_L = \frac{V_i R_L}{R_L + R} = 16 \frac{1.2}{1 + 1.2} = 8.73 \text{ V}$$


Since the voltage across the Zener is smaller than V_Z and the diode is reverse, then the Zener is OFF.

$$V_L = V_{zener} = 8.73 \text{ V}$$

$$V_R = V_i - V_L = 16 - 8.73 = 7.27 \text{ V}$$

$$I_Z = 0$$

$$P_Z = 0 \text{ Watts}$$

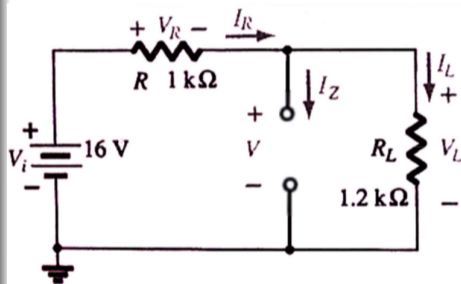

Example

Fixed V_i , Fixed R_L :

Solution:

② If $R_L = 3 \text{ k}\Omega$:


$$V_{zener} = V_i \frac{R_L}{R + R_L} = \frac{16 \times 3}{1 + 3} = 12 \text{ V}$$

Since the voltage across the zener is greater than V_Z then the zener is operating in the zener region and can be approximated as battery with V_Z :

$$V_L = V_Z = 10 \text{ V}$$

$$V_R = V_i - V_L = 16 - 10 = 6 \text{ V}$$
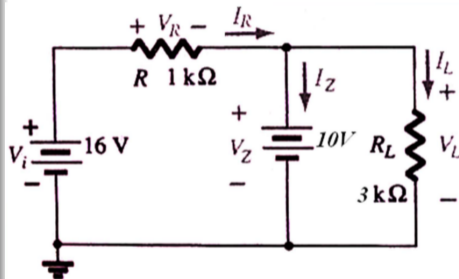
$$I_R = \frac{V_R}{R} = \frac{6 \text{ V}}{1 \text{ k}\Omega} = 6 \text{ mA}$$



Example

Fixed V_i , Fixed R_L :


Solution:

$$I_L = \frac{V_L}{R_L} = \frac{10V}{3k\Omega} = 3.33 \text{ mA}$$

$$I_Z = I_R - I_L = 6 - 3.33 = 2.67 \text{ mA}$$

The power dissipated by the Zener diode is:
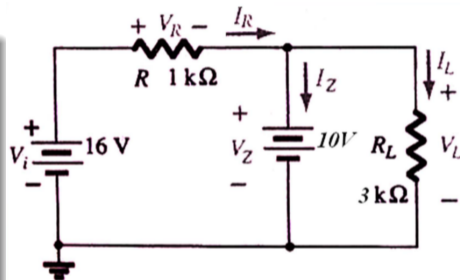
$$P_Z = I_Z \times V_Z = 26.7 \text{ mW}$$




Example

Table of Contents

- 1 Introduction.
- 2 Fixed V_i , Fixed R_L .
- 3 Fixed V_i , Variable R_L .

Fixed V_i , Variable R_L :

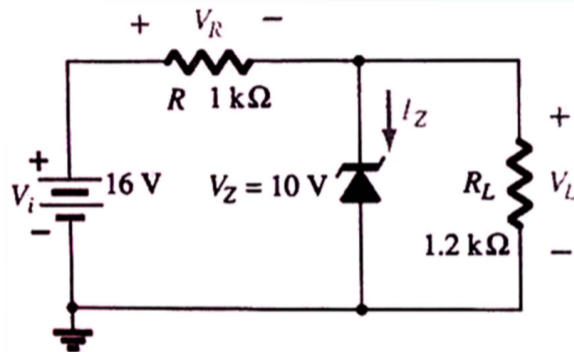- The load resistance R_L determines the state of the Zener (on or off).
- Too small a R_L will result in a voltage V_L across the load resistor less than V_Z , and the Zener device will be in the “off” state.
- We need to find the range of load resistance that ensure the on state for the zener diode



$$V_L = V_i \frac{R_L}{R + R_L}$$

Fixed V_i , Variable R_L :

To determine the minimum load resistance, R_{Lmin} :


It is the resistance that will result in a load voltage $V_L = V_Z$:

$$V_L = V_Z = V_i \frac{R_L}{R + R_L}$$

$$R_{Lmin} = \frac{R V_Z}{V_i - V_Z}$$

So, if a load resistance is greater than R_{Lmin} then the Zener will be on and:
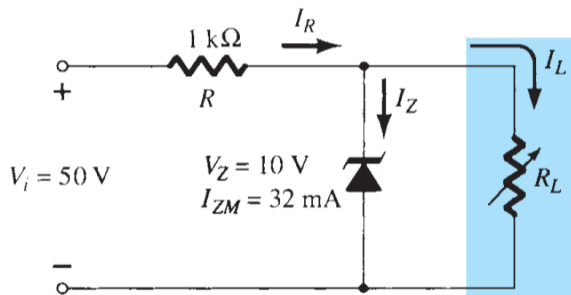
$$I_{Lmax} = \frac{V_L}{R_L} = \frac{V_Z}{R_{Lmin}}$$



Fixed V_i , Variable R_L :

To determine the maximum load

resistance, R_{Lmax} :

Once the diode is ON, the voltage across R is fixed at:

$$V_R = V_i - V_Z$$

and,

$$I_R = \frac{V_R}{R}$$


The Zener current is:

$$I_Z = I_R - I_L$$

I_Z is limited to the maximum zener current I_{ZM} from the data sheet.

$$I_{Lmin} = I_R - I_{ZM}$$


$$R_{Lmax} = \frac{V_Z}{I_{Lmin}}$$

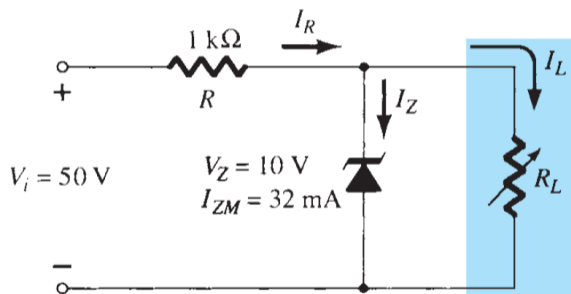

Fixed V_i , Variable R_L :

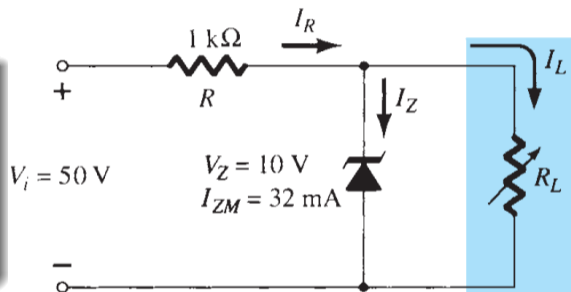Example:

- 1 For the shown network, determine the range of R_L and I_L that will result in V_L being maintained at 10 V.
- 2 Determine the maximum wattage rating of the diode.




Fixed V_i , Variable R_L :

Solution:

$$R_{Lmin} = \frac{R V_Z}{V_i - V_Z} = \frac{1 \text{ k}\Omega \cdot 10\text{V}}{50\text{V} - 10\text{V}}$$

$$R_{Lmin} = 250 \Omega$$
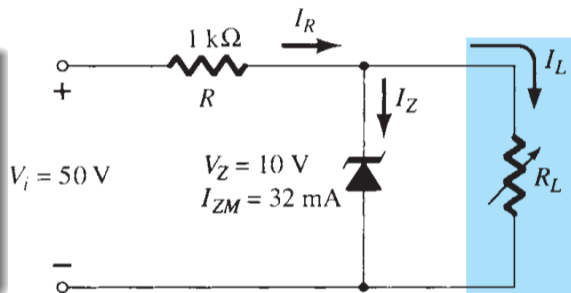
$$I_{Lmax} = \frac{V_L}{R_L} = \frac{V_Z}{R_{Lmin}} = \frac{10}{250} = 40\text{mA}$$



Fixed V_i , Variable R_L :


Solution:




$$V_R = V_i - V_Z = 50 - 10 = 40 \text{ V}$$

$$I_R = \frac{V_R}{R} = \frac{40 \text{ V}}{1 \text{ k}\Omega} = 40 \text{ mA}$$

$$I_{Lmin} = I_R - I_{ZM} = 40 - 32 = 8 \text{ mA}$$
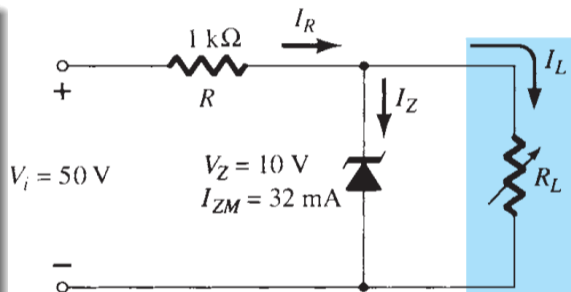
$$R_{Lmax} = \frac{V_Z}{I_{Lmin}} = \frac{10 \text{ V}}{8 \text{ mA}}$$




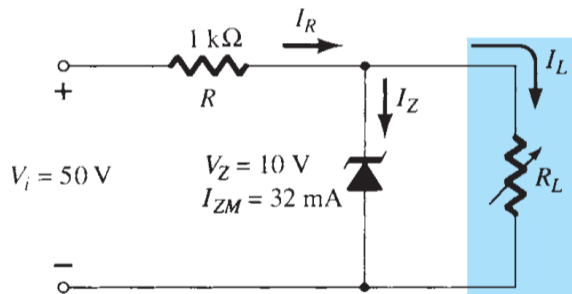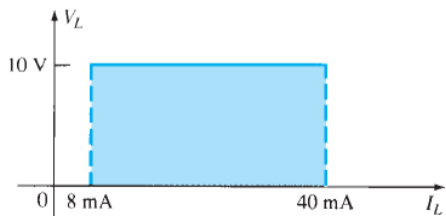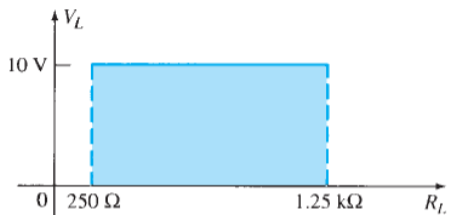Fixed V_i , Variable R_L :

Fixed V_i , Variable R_L :

Solution:
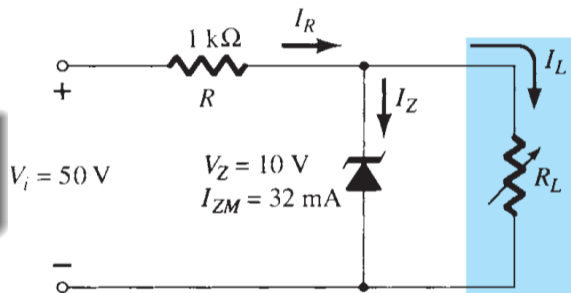
$$P_{Z_{max}} = V_Z I_{ZM} = (10 \text{ V})(32 \text{ mA}) = 320 \text{ mW}$$



End of Lecture

Best Wishes

haitham.elhussieny@gmail.com