

Electrical and Electronic Measurements

Lecture 5: Analog Electronic Voltmeters

Dr. Haitham El-Hussieny

Electronics and Communications Engineering
Faculty of Engineering (Shoubra)
Benha University



October 2018

Lecture Outline:

- 1 Introduction.
- 2 Emitter-Follower Voltmeter.
- 3 FET-input Voltmeter.

Table of Contents

1 Introduction.

2 Emitter-Follower Voltmeter.

3 FET-input Voltmeter.

Introduction:

- The electromechanical instruments have some limitations: as **having low resistance (loading effect)** and **cannot measure very low voltages**.
- The low input voltages need to be **amplified** to measurable levels and electronic circuits are required to **offer high input resistance**.
- Electronic circuits voltmeters with **transistors**, **operational amplifiers** (or op-amp) can be used to amplify small voltage and provide high input resistance .
- These analog circuits include:
 - ① Emitter-Follower Voltmeter.
 - ② FET-input Voltmeter.

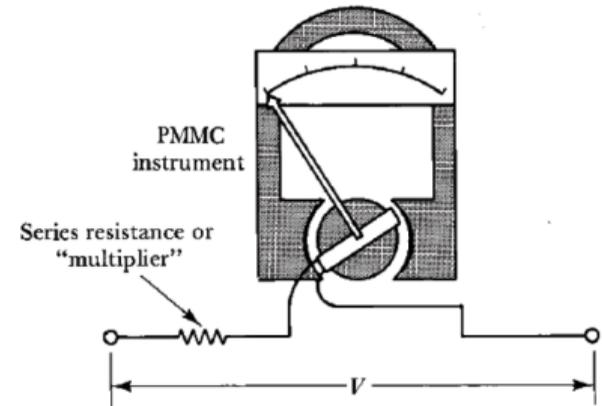


Table of Contents

1 Introduction.

2 Emitter-Follower Voltmeter.

3 FET-input Voltmeter.

Emitter-Follower Voltmeter:


- A BJT emitter follower is used where the PMMC and R_s are connected to the Emitter.
- The voltage to be measured, that is, E , is connected to the base of the transistor.
- The base current, I_b is:

$$I_b = \frac{I_m}{\beta}, \quad \beta : (\text{Transistor gain})$$

- The input resistance, R_i is:

$$R_{in} \approx \frac{E}{I_b}$$

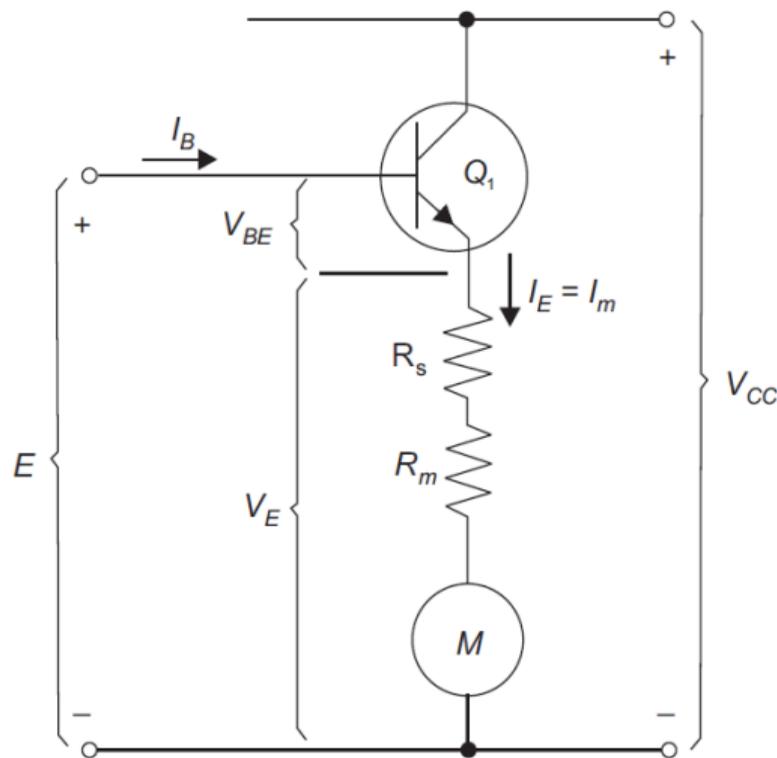which is **much larger** than $R_s + R_m$ since I_b is small.



Emitter-Follower Voltmeter:

Example

A simple emitter-follower voltmeter with: $V_{CC} = 12\text{ V}$, $R_m = 2\text{ k}\Omega$, 1 mA FSD meter current, and current gain $\beta = 50$.


Determine :

- Appropriate multiplier resistance that can give FSD 5 V .
- Input resistance

(a)

$$R_s = \frac{V_E}{I_m} - R_m = \frac{E - V_{BE}}{I_m} - R_m = \frac{5 - 0.7}{1\text{ mA}} - 2 = 2.3\text{ k}\Omega$$

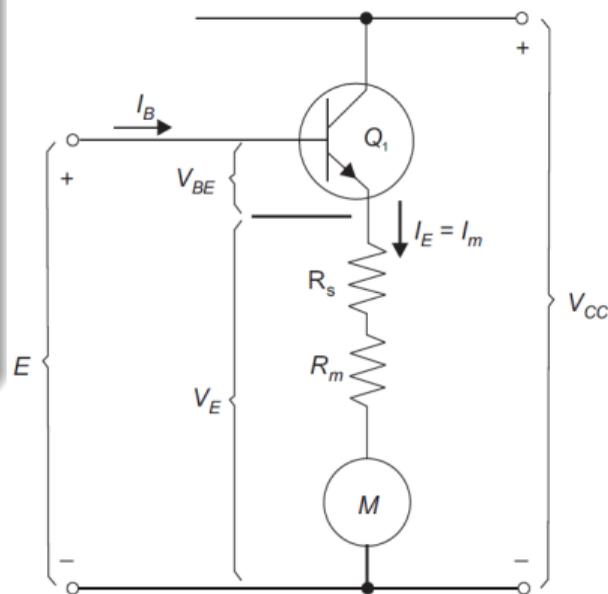(b) $R_{in} = \frac{E}{I_b} = \beta \cdot \frac{E}{I_m} = 50 \cdot \frac{5}{1\text{ mA}} = 250\text{ k}\Omega$




Emitter-Follower Voltmeter:

- To **reduce the drop** V_{BE} , a one more emitter-follower and a voltage divider are used with a $\pm 12\text{ V}$ dual polarity supply is connected.
- When $E = 0$, the resistance R_5 is adjusted to make $V_{E2} = 0.7$ and $V_m = 0$.
- When E is exist, the PMMC voltage is:

$$V_m = E - 0.7 - (-0.7) = E$$

- So, the voltage drop is removed.

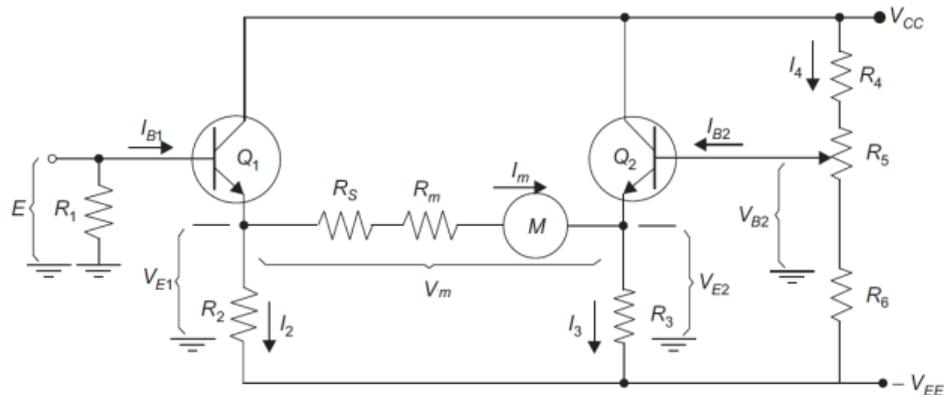

Modified Emitter-Follower Voltmeter


Table of Contents

1 Introduction.

2 Emitter-Follower Voltmeter.

3 FET-input Voltmeter.

FET-input Voltmeter:

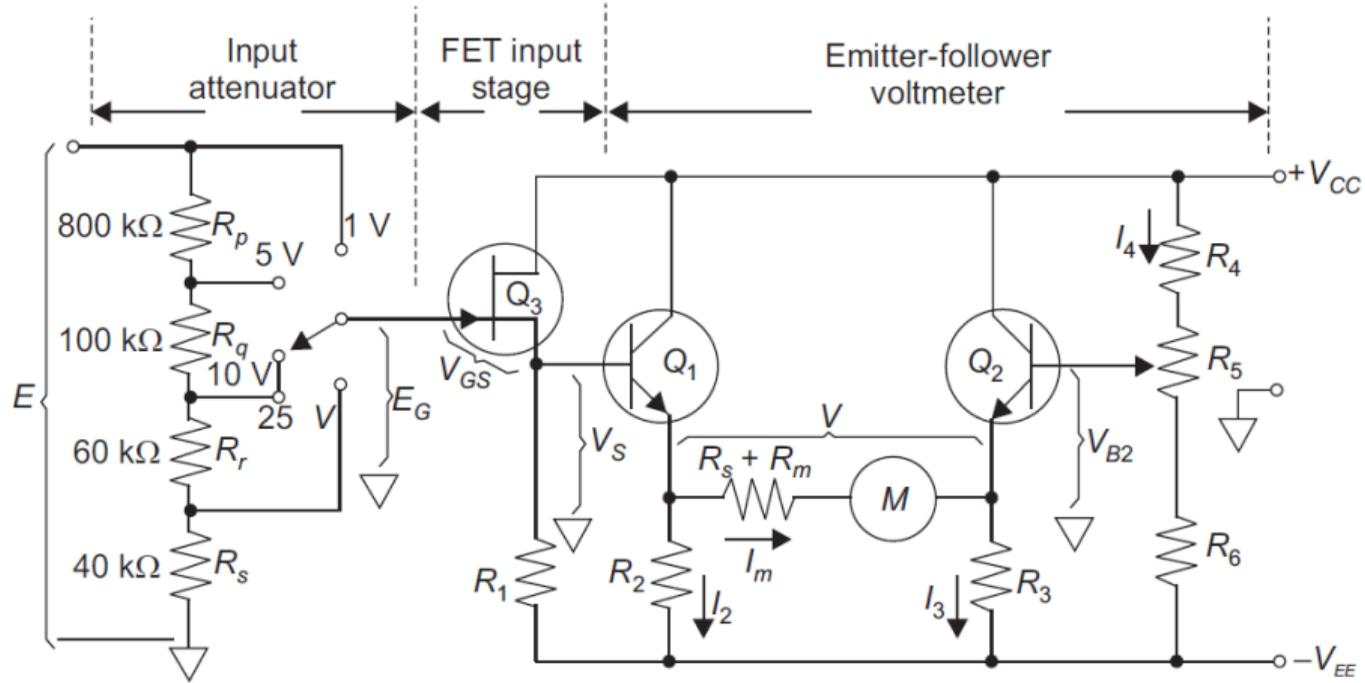

Advantage:

The Field Effect Transistor (FET) provide extremely high input resistance.

End of Lecture

Best Wishes

haitham.elhussieny@feng.bu.edu.eg