

Chapter 5

BJT Biasing Circuits

5.1 The DC Operation Point [5]

DC Bias:

Bias establishes the dc operating point for proper linear operation of an amplifier. If an amplifier is not biased with correct dc voltages on the input and output, it can go into saturation or cutoff when an input signal is applied. Figure 5.1 shows the effects of proper and improper dc biasing of an invert amplifier.

 


Figure 5.1 Examples of linear and nonlinear operation of an inverting amplifier (the triangle symbol). [5]

In part (a), the output signal is an amplified replica of the input signal except that it is inverted, which means that it is 180° out of the phase with the input. Part (b) illustrates limiting of the positive portion of the output voltage for a result of a dc operating point (Q-point) being too close to cutoff. Part (c) shows limiting of the negative portion of the output voltage as a result of a dc operating point being too close to saturation.

Linear Operation:

The region along the load line including all points between saturation and cutoff is generally known as the linear region of the transistor's operation. The output voltage in this region is ideally a linear reproduction of the input. Figure 5.2 shows an example of the linear operation of a transistor. AC quantities are indicated by lower case italic subscripts.


 


Figure 5.2 Variations in collector current and collector-to-emitter voltage as a result of a variation in base current. [5]

Assume a sinusoidal voltage, V_{in} , is superimposed on V_{BB} , causing the base current to vary sinusoidally $100 \mu\text{A}$ above and below its Q-point value of $300 \mu\text{A}$. This causes the collector current (I_C) to vary 10 mA above and below its Q-


point value of 30 mA. As a result, the collector-to-emitter voltage varies 2.2 V above and below its Q-point value of 3.4 V. Point A on the load line corresponds to the positive peak of the sinusoidal input voltage. Point B corresponds to the negative peak, and point Q corresponds to the zero value of the sine wave. V_{CEQ} , I_{CQ} , and I_{BQ} are dc Q-point values with no input sinusoidal voltage applied.

Waveform Distortion:

 

(a) Transistor is driven into saturation because the Q-point is too close to saturation for the given input signal.

 (b) Transistor is driven into cutoff because the Q-point is too close to cutoff for the given input signal.



(c) Transistor is driven into both saturation and cutoff because the input signal is too large.

Figure 5.3 Graphical load line illustration of a transistor being driven into saturation and/or cutoff. [5]

Under certain input signal conditions, the location of Q-point on the load line cause one peak of the load line can cause one peak of the V_{ce} waveform to be limited or clipped, as shown in Figure 5.3(a) and (b). In each case, the input signal is too large for the Q-point location and is driving the transistor into cutoff or saturation during a portion of the input cycle. When both peaks are limited, the transistor is being driven into both saturation and cutoff by an excessively large input signal.

Example 1: Determine the Q-point and find the maximum peak value of the base current for linear operation. Assume $\beta_{DC} = 200$.

 


Figure 5.4 For Example 1. [5]

Solution:

The Q-point is defined by I_C and V_{CE}

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{10V - 0.7V}{47K\Omega} = 198\mu A = I_{BQ}$$

$$I_C = \beta_{DC} I_B = (200)(198\mu A) = 39.6mA = I_{CQ}$$

$$\begin{aligned} V_{CE} &= V_{CC} - I_C R_C = 20V - 13.07 \\ &= 6.93V = V_{CEQ} \end{aligned}$$

$$*I_{C(sat)} = \frac{V_{CC} - V_{CE(sat)}}{R_C} = I_{C(sat)} = \frac{V_{CC}}{R_C} = \frac{20V}{330\Omega}$$

$$*I_{C(cutoff)} = 0$$

$$I_{C(sat)} - I_{CQ} = 60.6 - 39.6 = 21mA$$

$$I_{CQ} - I_{C(cutoff)} = 39.6 - 0 = 39.6mA$$

∴ Q-point is in closer to saturation than the cutoff

∴ 21mA is the maximum peak variation ($I_{C(max)}$) of the collector current

$$\therefore I_{b(peak)} = \frac{I_{C(peak)}}{\beta_{DC}} = \frac{21mA}{200} = 105\mu A \text{ _____\#}$$

 


Figure 5.5 For Example 1. [5]

5.2 Base Bias [5]

As shown in Figure 5.6 (a), two dc voltage supplies are needed to bias a BJT which is not practical. In a simple biasing circuit, V_{BB} is eliminated by connecting the resistor R_B to the supply V_{CC} . This biasing circuit is called base bias, or fixed bias, see Figure 5.6 (b).

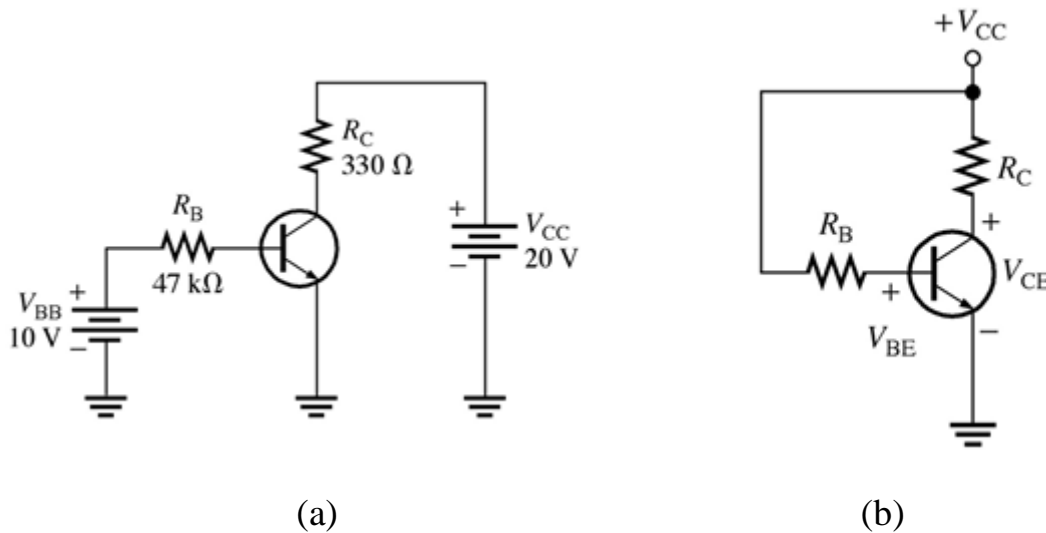


Figure 5.6 An npn transistor with base bias. [5]

The analysis of this circuit for the linear region is as follow.

Using KVL :

$$V_{CC} - V_{R_B} - V_{BE} = 0$$

Substituting $I_B R_B$ for V_{R_B}

$$V_{CC} - I_B R_B - V_{BE} = 0$$

Then solving for I_B ,

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

Kirchhoff's voltage law applied around the collector circuit gives the following equation:

$$V_{CC} - I_C R_C - V_{CE} = 0$$

Solving for V_{CE} ,

$$V_{CE} = V_{CC} - I_C R_C$$

Substituting this expression for I_B into the formula $I_C = \beta_{DC} I_B$ yields

$$I_C = \beta_{DC} \left(\frac{V_{CC} - V_{BE}}{R_B} \right)$$

Q-Point Stability of Base Bias:

In the last equation, I_C is dependent on β_{DC} . The disadvantage of this is that β_{DC} varies with temperature and collector current. The variation in β_{DC} causes I_C and V_{CE} to change, thus changing the Q-point of the transistor. This makes the base bias circuit extremely beta-dependent and very unstable.

Example 2: (a) Determine the Q-point values of I_C and V_{CE} for the circuit in Figure 5.7. Assume $V_{CE} = 8 \text{ V}$, $R_B = 360 \text{ k}\Omega$ and $R_C = 2 \text{ k}\Omega$.

(b) Construct the dc load line and plot the Q-point.

 


Figure 5.7 For Example 2. [5]

Solution:

$$(a) I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{8V - 0.7V}{360K\Omega} = 20.28\mu A$$

$$I_C = \beta_{DC} I_B = 100 * 20.28\mu A = 2.028mA$$

$$V_{CE} = V_{CC} - I_C R_C = 8V - (2.028mA)(2K\Omega) = 3.94V$$

$$(b) \text{ Assume } V_{CE(sat)} = 0V \therefore I_{C(sat)} = \frac{V_{CC}}{R_C} = \frac{8V}{2K\Omega} = 4mA$$

$$\text{and Assume } I_{C(cutoff)} = 0A \therefore V_{CE(cutoff)} = V_{CC} = 8V$$

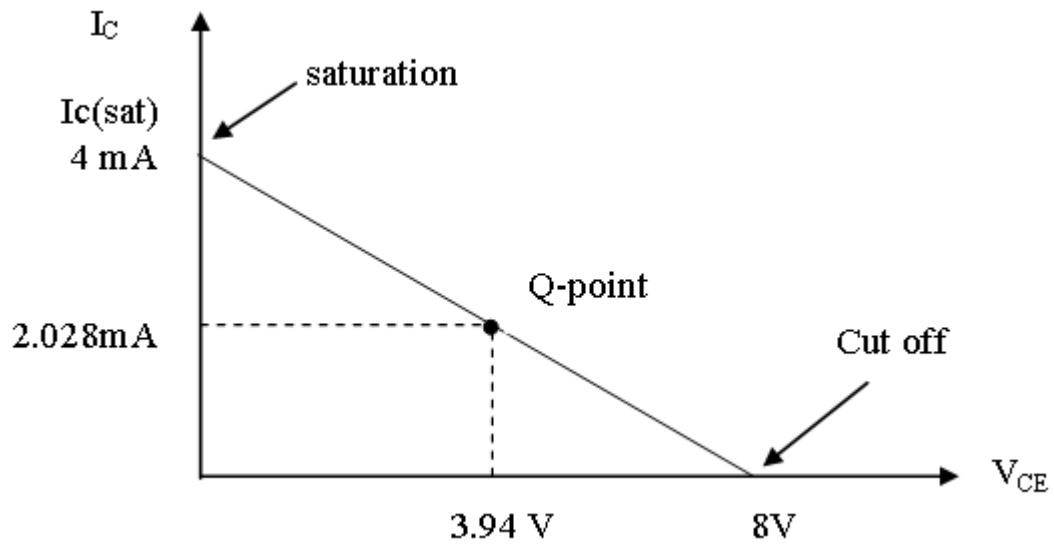


Figure 5.8 For Example 2.

Example 3: Determine the Q-point values of I_C and V_{CE} for the circuit in Figure 5.9. Find $I_{C(sat)}$ and $V_{CE(cut\ off)}$, and then construct the dc load line and plot the Q-point. ** Assume $I_C \cong I_E$ to find $I_{C(sat)}$ and $V_{CE(cut\ off)}$ **

 


Figure 5.9 For Example 3.

Solution:

Left loop:

$$V_{CC} - V_{R_B} - V_{BE} - V_{R_E} = 0$$

$$V_{CC} - I_B R_1 - V_{BE} - I_E R_E = 0$$

$$\text{As } I_E = I_B + I_C = (\beta_{DC} + 1)I_B$$

$$\therefore V_{CC} - I_B R_1 - V_{BE} - 101I_B R_E = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_1 + 101R_E} = \frac{20 - 0.7}{2.7 \text{ M}\Omega + 101(3.3 \text{ k}\Omega)}$$

$$= 6.363 \mu\text{A}$$

$$\therefore I_C = \beta_{DC} I_B = 0.636 \text{ mA}$$

$$I_E = I_B + I_C = 0.643 \text{ mA}$$

Right loop:

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

Solving for V_{CE} ,

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

$$\begin{aligned} V_{CE} &= 20 - (0.636) * 10 - (0.643) * 3.3 \\ &= 11.52 \text{ V} \end{aligned}$$

\therefore Q-point is at $I_C = 0.636 \text{ mA}$ and $V_{CE} = 11.52 \text{ V}$

$$V_{CE} = V_C - V_E = (V_{CC} - I_C R_C) - (I_E R_E)$$

$$I_E \cong I_C; V_{CE} = V_{CC} - I_C (R_C + R_E)$$

at saturation: $V_{CE} = 0$

$$\therefore I_{C(sat)} = \frac{V_{CC}}{R_C + R_E} = \frac{20V}{(10 + 3.3)K\Omega} = 1.504 \text{ mA}$$

at cutoff: $I_{C(cutoff)} = 0 \text{ A}$

$$\therefore V_{CE(cutoff)} = V_{CC} = 20V$$

 


Figure 5.10 For Example 3.

Example 4: Determine whether the transistor is biased in cutoff, saturation or linear region.

- (a) $R_B = 75K\Omega$, $R_C = 1K\Omega$; saturation
- (b) $R_B = 150K\Omega$, $R_C = 1K\Omega$; linear
- (c) $R_B = 75K\Omega$, $R_C = 2K\Omega$; saturation

 


Figure 5.11 For Example 4. [5]

Solution:

$$(a) \text{ As } V_{CE} = V_{CC} - I_C R_C$$

$$\therefore I_{C(sat)} = \frac{V_{CC}}{R_C} = \frac{12V}{1K\Omega} = 12mA$$

$$I_C = \beta_{DC} \left[\frac{V_{CC} - V_{BE}}{R_B} \right] = 100 \left[\frac{12 - 0.7}{75K\Omega} \right]$$

$$= 15.067mA$$

As $I_C > I_{C(sat)}$ \therefore This transistor is biased in saturation region.

$$(b) \text{ As } V_{CE} = V_{CC} - I_C R_C$$

$$\therefore I_{C(sat)} = \frac{V_{CC}}{R_C} = \frac{12V}{1K\Omega} = 12mA$$

$$I_C = \beta_{DC} \left[\frac{V_{CC} - V_{BE}}{R_B} \right] = 100 \left[\frac{12 - 0.7}{150\text{K}\Omega} \right]$$

$$= 7.533\text{mA}$$

As $I_C < I_{C(\text{sat})}$: This transistor is biased in linear region.

(c) As $V_{CE} = V_{CC} - I_C R_C$

$$\therefore I_{C(\text{sat})} = \frac{V_{CC}}{R_C} = \frac{12\text{V}}{2\text{K}\Omega} = 6\text{mA}$$

$$I_C = \beta_{DC} \left[\frac{V_{CC} - V_{BE}}{R_B} \right] = 100 \left[\frac{12 - 0.7}{75\text{K}\Omega} \right]$$

$$= 7.533\text{mA}$$

As $I_C > I_{C(\text{sat})}$ \therefore This transistor is biased in saturation region.

5.3 Collector-Feedback Bias [5]

In Figure 5.12, the base resistor R_B is connected to the collector rather than to V_{CC} . The collector voltage provides the bias for the base-emitter junction. The negative feedback creates an “offsetting” effect that tends to keep the Q-point stable. If I_C tries to increase, it drops more voltage across R_C , thereby causing V_C to decrease. When V_C decreases, there is a decrease in voltage across R_B , which decreases I_B . The decrease in I_B produces less I_C which drops less voltage across R_C and thus offsets the decrease in V_C .

 


Figure 5.12 Collector-feedback bias. [5]

Applying KVL:

$$\begin{aligned}V_{CC} &= V_{RC} + V_{RB} + V_{BE} \\ &= (I_C + I_B)R_C + I_B R_B + V_{BE} \\ &= \beta_{DC} I_B R_C + I_B R_C + I_B R_B + V_{BE} \\ &= (\beta_{DC} + 1)I_B R_C + I_B R_B + V_{BE}\end{aligned}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta_{DC} + 1)R_C}$$

$$I_{CQ} = \frac{\beta_{DC} (V_{CC} - V_{BE})}{R_B + (\beta_{DC} + 1)R_C}$$

$$\begin{aligned}V_{CEQ} &= V_{CC} - (I_{CQ} + I_B)R_C \\ &\approx V_{CC} - I_{CQ}R_C \quad ; \beta_{DC} \gg 1\end{aligned}$$

$$\therefore V_{CE} \approx V_{CC} - I_C R_C$$

Q-Point Stability over Temperature:

It is known that β_{DC} varies directly with temperature, and V_{BE} varies inversely with temperature. As the temperature goes up in a collector-feedback circuit, β_{DC} goes up and V_{BE} goes down. This increase in β_{DC} acts to increase I_C . The decrease in V_{BE} acts to increase I_B which, in turns also acts to increase I_C . As I_C tries to increase, the voltage drop across R_C also tries to increase. This tends to reduce the collector voltage and therefore the voltage across R_B , thus reducing I_B and offsetting the attempted increase in I_C and the attempted decrease in V_C . The result is that the collector-feedback circuit maintains a relatively stable Q-point. Moreover, the reverse action occurs when the temperature decreases.

Example 5: Calculate the Q-point values (I_C and V_{CE}) for this circuit.

 


Figure 5.13 For Example 5. [5]

Solution:

at Q - point :

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta_{DC} + 1)R_C} = \frac{10 - 0.7}{100 + (100 + 1)} = 8.38 \mu\text{A}$$

$$I_C = \frac{\beta_{DC}(V_{CC} - V_{BE})}{R_B + (\beta_{DC} + 1)R_C} = 100 \times 8.38 \mu\text{A} = 0.838 \text{ mA}$$

$$V_{CE} = V_{CC} - (I_C + I_B)R_C = 10 - (0.838 + 0.00838) \times 10 = 1.536 \text{ V}$$

\therefore Q - point is at $I_C = 0.838 \text{ mA}$ and $V_{CE} = 1.536 \text{ V}$

at cut off and saturation mode :

$$\text{As } V_{CE} = V_{CC} - (I_C + I_B)R_C$$

But we usually assume that $I_C \gg I_B$ to find $I_{C(\text{sat})}$ and $V_{CE(\text{cutoff})}$

$$\text{Therefore } V_{CE} \approx V_{CC} - I_C R_C$$

$$\therefore I_{C(\text{sat})} = \frac{V_{CC}}{R_C} = 1 \text{ mA}$$

$$V_{CE(\text{cutoff})} = V_{CC} = 10 \text{ V}$$

5.4 Emitter Bias [5]

Emitter bias uses both a positive ($+V_{CC}$) and a negative ($-V_{EE}$) supply voltage. In the circuit shown in Figure 5.14, the V_{EE} supply voltage forward-biases the base-emitter junction, Kirchhoff's voltage law applied around the base-emitter circuit in Figure 5.14 (a), which has been redrawn in Figure 5.14 (b) for analysis, gives the follow equation:

$$-V_{EE} + V_{R_B} + V_{BE} + V_{R_E} = 0$$

Using Ohm's law,

$$-V_{EE} + I_B R_B + V_{BE} + I_E R_E = 0$$

Solving for V_{EE} ,

$$I_B R_B + V_{BE} + I_E R_E = V_{EE}$$

Substituting for I_E ,

$$I_B R_B + V_{BE} + (\beta_{DC} + 1)I_B R_E = V_{EE}$$

Then solving for I_B ,

$$I_B = \frac{V_{EE} - V_{BE}}{R_B + (\beta_{DC} + 1)R_E}, \quad \text{Since } I_C = \beta_{DC} I_B, \quad I_C = \frac{\beta_{DC}(V_{EE} - V_{BE})}{R_B + (\beta_{DC} + 1)R_E}$$

The emitter voltage with respect to ground is

$$V_E = -V_{EE} + I_E R_E$$

The base voltage with respect to ground is

$$V_B = V_E + V_{BE}$$

The collector voltage with respect to ground is

$$V_C = V_{CC} - I_C R_C$$

$$\begin{aligned} \therefore V_{CE} &= V_C - V_E = (V_{CC} - I_C R_C) - (-V_{EE} + I_E R_E) = V_{CC} + V_{EE} - I_C R_C - I_E R_E \\ &\approx (V_{CC} + V_{EE}) - I_C (R_C + R_E), \quad \text{if } \beta_{DC} \gg 1 \end{aligned}$$

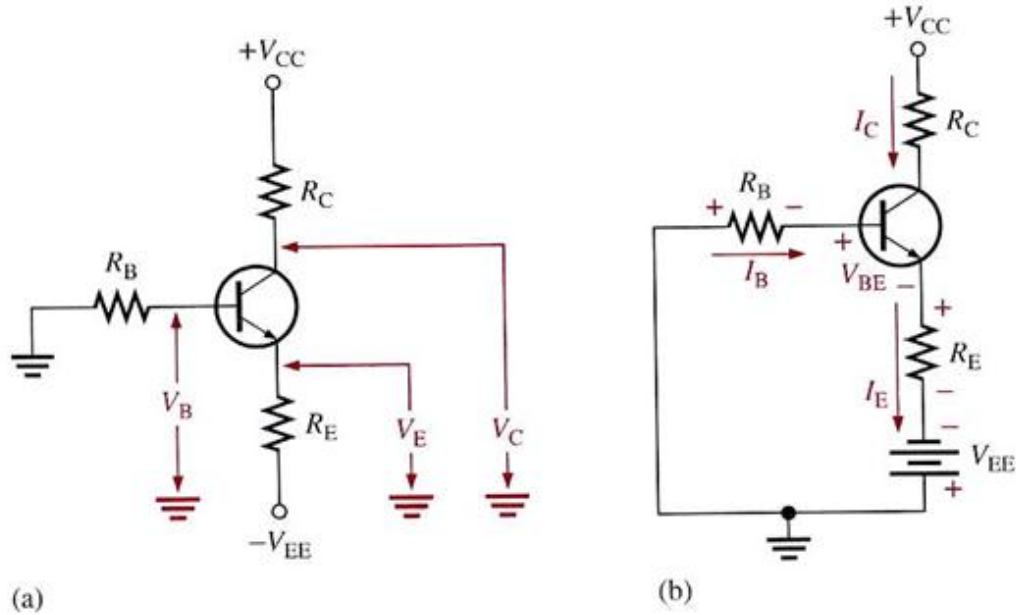


Figure 5.14 Emitter bias [5]

Q-Point Stability of Emitter Bias:

The formula for I_E shows that the emitter bias circuit is dependent on V_{BE} and β_{DC} , both of which change with temperature and current

$$I_C = \frac{\beta_{DC}(V_{EE} - V_{BE})}{R_B + (\beta_{DC} + 1)R_E} = \frac{V_{EE} - V_{BE}}{\frac{R_B}{\beta_{DC}} + \frac{(\beta_{DC} + 1)R_E}{\beta_{DC}}}$$

$$\text{If } \beta_{DC} \gg 1, \quad I_C \approx \frac{V_{EE} - V_{BE}}{\frac{R_B}{\beta_{DC}} + R_E}, \quad \text{If } R_E \gg R_B/\beta_{DC}, \quad I_C \approx \frac{V_{EE} - V_{BE}}{R_E}$$

This condition makes I_C independent of β_{DC}

$$\text{If } V_{EE} \gg V_{BE}, \text{ the } V_{BE} \text{ term can be dropped, } \quad I_C \approx \frac{V_{EE}}{R_E}$$

This condition makes I_C independent of V_{BE}

As I_C is independent of β_{DC} and V_{BE} , emitter bias can provide a stable Q-point if properly designed.

Example 6: Determine whether the transistor is biased in cutoff, saturation or linear region.

- (a) $R_B = 330\Omega$, $R_E = 3K\Omega$, $R_C = 1.6K\Omega$
 (b) $R_B = 150\Omega$, $R_E = 1K\Omega$, $R_C = 1.6K\Omega$
 (c) $R_B = 150\Omega$, $R_E = 500\Omega$, $R_C = 4 K\Omega$

 


Figure 5.15 For Example 6.

Solution:

$$(a) \text{ As } I_C = \frac{\beta_{DC}(V_{EE} - V_{BE})}{R_B + (\beta_{DC} + 1)R_E}$$

$$\therefore I_{CQ} = \frac{220(5 - 0.7)}{330\Omega + (220 + 1) \times 3\text{ k}\Omega} = 1.426\text{ mA}$$

from $V_{CE} \approx (V_{CC} + V_{EE}) - I_C(R_C + R_E)$, $\beta_{DC} \gg 1$

$$\therefore I_{C(sat)} = \frac{V_{CC} + V_{EE}}{R_C + R_E} = \frac{5 + 25}{3 + 1.6} = 6.522\text{ mA}$$

As $I_{CQ} < I_{C(sat)}$, \therefore this transistor is operated in active mode.

$$(b) \text{ As } I_C = \frac{\beta_{DC}(V_{EE} - V_{BE})}{R_B + (\beta_{DC} + 1)R_E}$$

$$\therefore I_{CQ} = \frac{220(5 - 0.7)}{150 \Omega + (220 + 1) \times 1 \text{ k}\Omega} = 4.278 \text{ mA}$$

from $V_{CE} \approx (V_{CC} + V_{EE}) - I_C(R_C + R_E)$, $\beta_{DC} \gg 1$

$$\therefore I_{C(sat)} = \frac{V_{CC} + V_{EE}}{R_C + R_E} = \frac{5 + 25}{1 + 1.6} = 11.538 \text{ mA}$$

As $I_{CQ} < I_{C(sat)}$, \therefore this transistor is operated in active mode.

(c) As $I_C = \frac{\beta_{DC}(V_{EE} - V_{BE})}{R_B + (\beta_{DC} + 1)R_E}$

$$\therefore I_{CQ} = \frac{220(5 - 0.7)}{150 \Omega + (220 + 1) \times 500 \Omega} = 8.55 \text{ mA}$$

from $V_{CE} \approx (V_{CC} + V_{EE}) - I_C(R_C + R_E)$, $\beta_{DC} \gg 1$

$$\therefore I_{C(sat)} = \frac{V_{CC} + V_{EE}}{R_C + R_E} = \frac{5 + 25}{500 \Omega + 4 \text{ k}\Omega} = 6.67 \text{ mA}$$

As $I_{CQ} > I_{C(sat)}$, \therefore this transistor is operated in saturation mode.

Example 7: Determine I_C , V_{CE} , $I_{C(sat)}$ and $V_{CE(\text{cut off})}$. Also, construct DC load line and plot Q-point. Assume $\beta_{DC} = 220$ and $I_E \cong I_C$.

 


Figure 5.16 For Example 7.

Solution:

$$\text{As } I_C = \frac{\beta_{DC}(V_{EE} - V_{BE})}{R_B + (\beta_{DC} + 1)R_E}$$
$$\therefore I_{CQ} = \frac{220(15 - 0.7)}{330 \Omega + (220 + 1) \times 3 \text{ k}\Omega} = 4.743 \text{ mA}$$

$$V_{CE} = V_C - V_E = (V_{CC} - I_C R_C) - (-V_{EE} + I_E R_E)$$

Assume $I_C \approx I_E$,

$$V_{CE} \approx (V_{CC} + V_{EE}) - I_C (R_C + R_E)$$
$$= (15 + 15) - 4.743 \text{ mA} (1.6 \text{ k}\Omega + 3 \text{ k}\Omega)$$
$$= 8.182 \text{ V}$$

$$V_{CE} \cong (V_{CC} + V_{EE}) - I_C (R_C + R_E)$$

at saturation mode:

$$V_{CE(sat)} = 0$$

$$I_{C(sat)} = \frac{V_{CC} + V_{EE}}{R_C + R_E} = \frac{30}{4.6 \text{ k}\Omega} = 6.522 \text{ mA}$$

at cutoff mode:

$$I_{C(cutoff)} = 0$$

$$V_{CE(cutoff)} = V_{CC} + V_{EE} = 30 \text{ V}$$

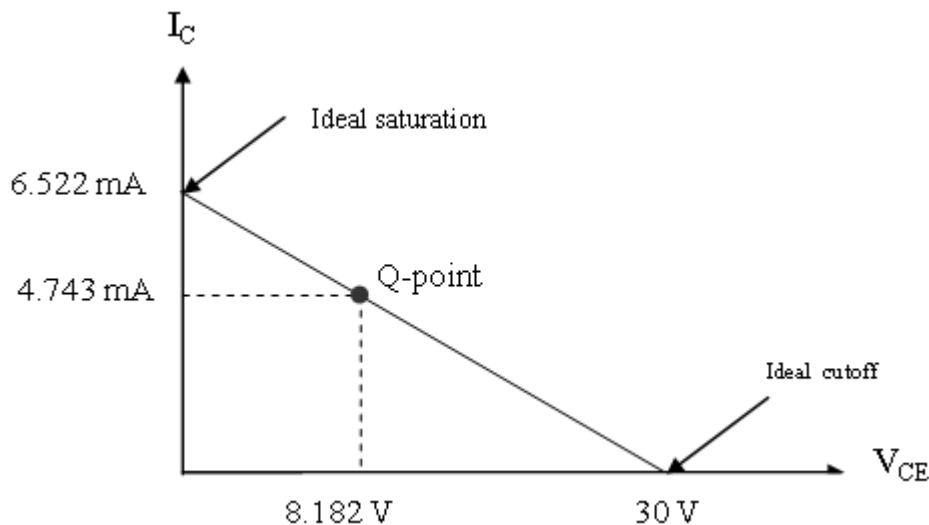


Figure 5.17

5.5 Voltage-Divider Bias [7]

The voltage-divider bias circuit is shown in Figure 5.18. In this figure, V_{CC} is used as the single bias source. A dc bias voltage at the base of the transistor can be developed by a resistive voltage divider consisting of R_1 and R_2 . There are two current paths between point A and ground: one through R_2 and the other through the base-emitter junction of the transistor and R_E .

 


Figure 5.18 Voltage-divider bias. [7]

Thevenin's Theorem Applied to Voltage-Divider Bias:

We can replace the original circuit of voltage-divider bias circuit shown in Figure 5.19 (a) with the thevenin equivalent circuit shown in Figure 5.19 (b). Apply Thevenin's theorem to the circuit left of point A, with V_{CC} replaced by a short to ground and the transistor disconnected from the circuit. The voltage at point A with respect to ground is

$$V_{TH} = \frac{R_2}{R_1 + R_2} V_{CC}$$

and the resistance is

$$R_{TH} = R_1 // R_2$$

 


Figure 5.19 Thevenizing the bias circuit. [7]

Applying KVL,

$$V_{TH} - V_{R_{TH}} - V_{BE} - V_{R_E} = 0$$

Substituting, using Ohm's law, and solving for V_{TH}

$$V_{TH} = I_E R_{TH} + V_{BE} + I_E R_E = I_B R_{TH} + V_{BE} + (\beta_{DC} + 1) I_B R_E$$

$$I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (\beta_{DC} + 1) R_E}, \quad I_{CQ} = \frac{\beta_{DC} (V_{TH} - V_{BE})}{R_{TH} + (\beta_{DC} + 1) R_E}$$

$$V_{CEQ} = V_{CC} - I_C R_C - I_E R_E \\ \approx V_{CC} - (R_C + R_E) I_{CQ}; \quad \beta_{DC} \gg 1$$

Stability of Voltage-Divider Bias:

$$\text{As } I_{CQ} = \frac{\beta_{DC} (V_{TH} - V_{BE})}{R_{TH} + (\beta_{DC} + 1) R_E}$$

Here assume $\beta_{DC} \gg 1$

$$\therefore I_{CQ} \approx \frac{\beta_{DC} (V_{TH} - V_{BE})}{R_{TH} + \beta_{DC} R_E}, \text{ then } I_{CQ} \approx \frac{V_{TH} - V_{BE}}{\frac{R_{TH}}{\beta_{DC}} + R_E}$$

$$\text{If } R_E \gg R_{TH}/\beta_{DC}, \text{ then } I_C \cong \frac{V_{TH} - V_{BE}}{R_E}$$

This last equation shows that I_C is independent of β_{DC} . Therefore, the voltage-divider bias is widely used because reasonably good stability is achieved with a single supply voltage.

Example 8: Determine V_{CE} and I_C in the voltage-divider biased transistor circuit. Assume $\beta_{DC} = 100$ and $I_E \cong I_C$.

 


Figure 5.20 For Example 8. [7]

Solution:

$$V_{TH} = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{5.6}{10 + 5.6} \times 10 = 3.59 \text{ V}$$

$$R_{TH} = R_1 // R_2 = 5.6 // 10 = 3.59 \text{ k}\Omega$$

$$I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (\beta_{DC} + 1)R_E} = \frac{3.59 - 0.7}{3.59 \text{ k}\Omega + (100 + 1)560 \Omega}$$

$$= 48.046 \mu\text{A}$$

$$I_{CQ} = \frac{\beta_{DC}(V_{TH} - V_{BE})}{R_{TH} + (\beta_{DC} + 1)R_E} = 100 \times 48.046 \mu\text{A}$$

$$= 4.805 \text{ mA}$$

$$V_{CEQ} \approx V_{CC} - (R_C + R_E)I_{CQ}$$

$$\approx 10 - (1 \text{ k}\Omega + 560 \Omega) \times 4.805 \text{ mA}$$

$$= 2.504 \text{ V}$$

Example 9: Determine V_{CE} and I_C in the voltage-divider biased transistor circuit. Assume $\beta_{DC} = 50$ and $I_E = I_B + I_C$.

 


Figure 5.21 For Example 9.

Solution:

$$V_{TH} = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{1}{6.8 + 1} \times 20 = 2.564 \text{ V}$$

$$I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (\beta_{DC} + 1)R_E} = \frac{2.564 - 0.7}{0.872 \text{ k}\Omega + (50 + 1)1 \text{ k}\Omega}$$

$$= 35.935 \mu\text{A}$$

$$I_C = \frac{\beta_{DC}(V_{TH} - V_{BE})}{R_{TH} + (\beta_{DC} + 1)R_E} = 50 \times 35.935 \mu\text{A}$$

$$= 1.797 \text{mA}$$

Here $I_E = I_B + I_C = 1.797 \text{mA} + 35.935 \mu\text{A}$

$\therefore I_E = 1.833 \text{mA}$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

$$= 20 - 1.797 \times 1 - 1.833 \times 1$$

$$= 16.37 \text{V}$$

Example 10: Determine Q-point (I_C, V_{CE}), I_{RC} and I_{RL} . Assume $\beta_{DC} = 200$ and $I_E \cong I_C$.

 


Figure 5.22 For Example 10.

Solution:

$$V_{TH} = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{5}{5 + 5} \times 20 = 10 \text{ V}$$

$$R_{TH} = R_1 // R_2 = 5 // 5 = 2.5 \text{ k}\Omega$$

$$I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (\beta_{DC} + 1)R_E} = \frac{10 - 0.7}{2.5 \text{ k}\Omega + (200 + 1)2 \text{ k}\Omega}$$

$$= 22.99 \mu\text{A}$$

$$I_{CQ} = \frac{\beta_{DC}(V_{TH} - V_{BE})}{R_{TH} + (\beta_{DC} + 1)R_E} = 200 \times 22.99 \mu\text{A}$$

$$= 4.598 \text{ mA}$$

$$\approx I_E$$

 


Figure 5.23 For Example 10.

$$I_{R_C} = I_C + I_{R_L}$$

$$\frac{20 - V_C}{1 \text{ k}\Omega} = 4.598 + \frac{V_C}{R_L}$$

$$V_C = 10.268 \text{ V}$$

$$V_E = I_E R_E \approx 4.598 \times 2 \text{ k}\Omega = 9.196 \text{ V}$$

$$V_{CE} = V_C - V_E = 1.072 \text{ V}$$

$$I_{R_C} = \frac{20 - 10.268}{1 \text{ k}\Omega} = 9.732 \text{ mA}$$

$$I_{R_L} = \frac{10.268}{2 \text{ k}\Omega} = 5.134 \text{ mA}$$

Practice Problem 1: Determine I_E , I_B , I_C , β_{DC} , α_{DC} and V_{EC} in the circuit.

 


Figure 5.24 For Practice Problem 1.

Practice Problem 2: Assume $\beta_{DC} = 150$, $V_{CE(sat)} = 0 \text{ V}$ and $I_{C(cut\ off)} = 0 \text{ A}$.

(a) Let $V_{BB} = 10 \text{ V}$, determine the Q-point value of I_C and V_{CE} .

(b) If $I_C/I_B = 5$, find V_{BB} such that $I_C/I_B = 5$. And determine I_B , I_C and I_E .

 


Figure 5.25 For Practice Problem 2.

5.6 Homework 8

1. Determine the Q-point and construct dc load line for this transistor.

 


Figure 5.26 For problem 1. [7]

2. Assume $\beta_{DC} = 100$ and $I_E \cong I_C$.

- Find V_E , V_C
- Determine Q-point of this transistor
- Construct DC load line and plot Q-point
- Calculate I_C if R_B is changed from $10 \text{ k}\Omega$ to be $1 \text{ k}\Omega$

 


Figure 5.27 For problem 2.

3. Find the values of I_B , I_C , I_E and V_{CE} . Assume $\beta_{DC} = 100$, and $I_E = I_B + I_C$.

 


Figure 5.28 For problem 3.

4. For the circuit shown in this figure, the Q-point is at $I_C = 1 \text{ mA}$ and $V_{CE} = 24 \text{ V}$ when $\beta_{DC} = 60$. Assume $I_C \cong I_E$, $V_{CE(sat)} = 0 \text{ V}$ and $I_{C(cut\ off)} = 0 \text{ A}$.

- Determine the values of R_C and R_B .
- Construct the DC load line and plot the Q-point.

 


Figure 5.29 For problem 4.

5. (a) Determine the Q-point.

(b) Find the maximum peak value of base current for linear operation. Assume $\beta_{DC} = 220$.

 


Figure 5.30 For problem 5.

6. (a) Determine the DC operating point (Q-point) and construct the DC load line for the transistor in Figure 6. Assume $I_C \cong I_E$, $V_{CE(sat)} = 0\text{ V}$ and $\beta_{DC} = \beta_{ac} = 150$.

(b) Suppose an AC voltage source (V_{in}) is connected to the base terminal of the transistor to make $I_b = 100\text{ }\mu\text{A}_{P}$. Draw the waveform of the total collector current i_c (DC current + AC current i.e., $I_C + I_c$) and that of the total voltage at collector with respect to emitter v_{ce} (DC voltage + AC voltage i.e., $V_{CE} + V_{ce}$). Also determine the minimum and maximum values of both waveforms.

 


Figure 5.31 For problem 6.

7. Consider the circuit shown in Figure 5.32. Assume $\beta_{DC} = 100$, $V_{CE(sat)} = 0\text{ V}$ and $I_{C(cut\ off)} = 0\text{ A}$.

(a) Determine the value of R_B to make $I_B = 50\ \mu\text{A}$, and then find V_{CE} in the circuit.

(b) Determine the value of R_B to make $I_C/I_B = 10$.

 


Figure 5.32 For problem 7.

8. (a) Determine the Q-point and construct the DC load line for the transistor in this circuit. Assume $V_{CE(sat)} = 0 \text{ V}$, $I_{C(\text{cut off})} = 0 \text{ mA}$, $I_C \cong I_E$ and $\beta_{DC} = \beta_{ac} = 150$.

(b) Suppose an AC voltage source (V_{in}) is connected to the base terminal of the transistor to make $I_{b(\text{peak})} = 5 \mu\text{A}_P$. Draw the waveform of the total collector current i_c (DC current + AC current i.e., $I_C + I_c$) and that of the total voltage at collector with respect to emitter v_{ce} (DC voltage + AC voltage i.e., $V_{CE} + V_{ce}$). Also determine the minimum and maximum values of both waveforms.

 


Figure 5.33 For problem 8.

9. (a) Consider the circuit in Figure 5.34 (a) and then find R_{TH} and V_{TH} for the base terminal as shown in Figure 5.34 (b).

(b) Find the values of I_B , I_C and I_{RL} in the circuit of Figure 4(b). Assume $\beta_{DC} = 100$.

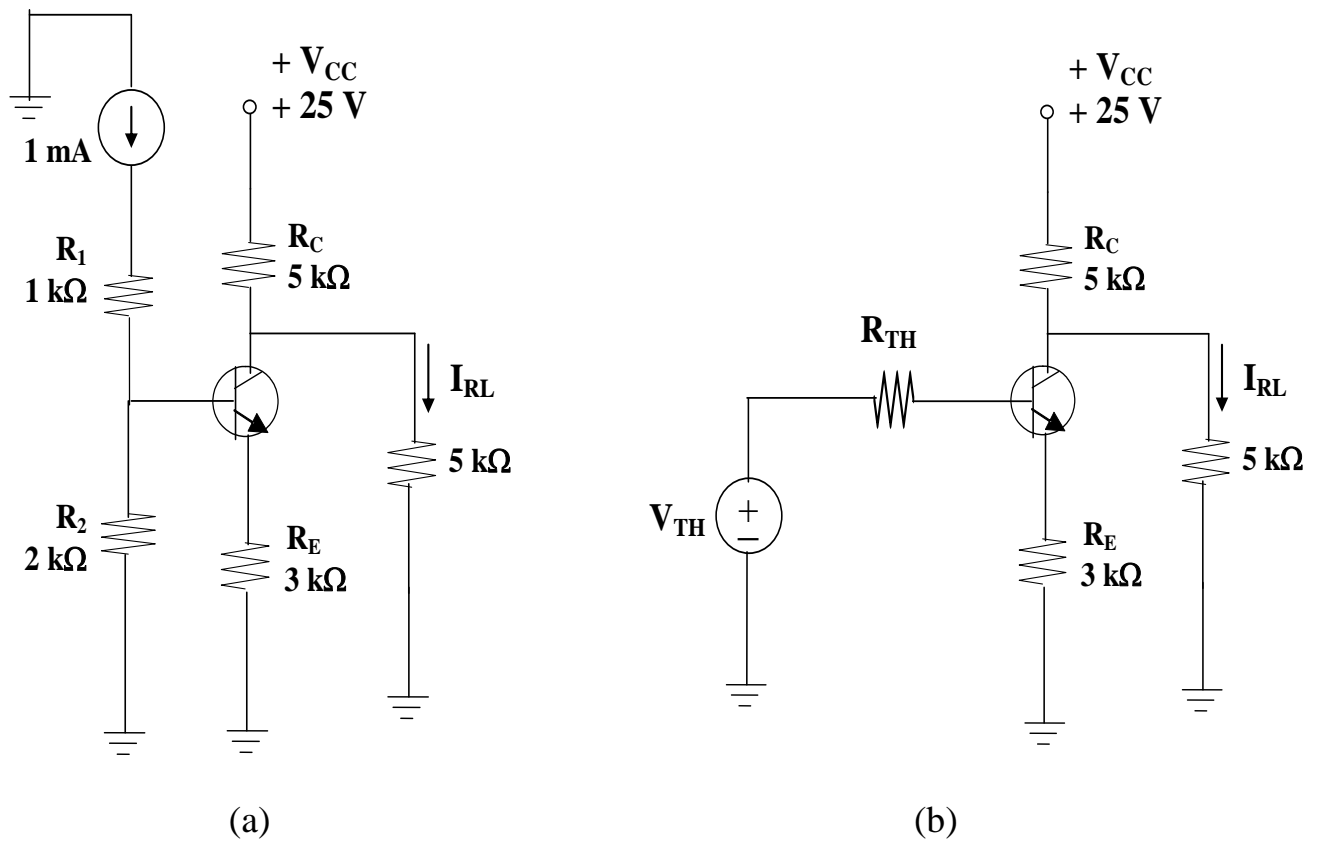


Figure 5.34 For problem 9.

10. Consider the circuit shown in Figure 5.35. Assume $\beta_{DC} = 50$, $V_{CE(sat)} = 0$ V and $I_{C(cut\ off)} = 0$ A.

(a) Let $V_{BB} = 15$ V, determine the Q-point value of I_C and V_{CE} in the circuit.

(b) Determine the value of V_{BB} to make $I_C/I_B = 10$, and then calculate I_B , I_C and I_E .

 


Figure 5.35 For problem 10.