

“

# Advanced Automatic Control

If you have a smart project, you can say "I'm an engineer"

”

---

## Lecture 3

Staff boarder

Prof. Dr. Mostafa Zaki Zahran

Dr. Mostafa Elsayed Abdelmonem

# Advanced Automatic Control


## MDP 444

---

- **Lecture aims:**
  - Facilitate combining and manipulating differential equations
  - Identify the equations of motion of systems
  - Understand the mathematical modeling of all systems and combination
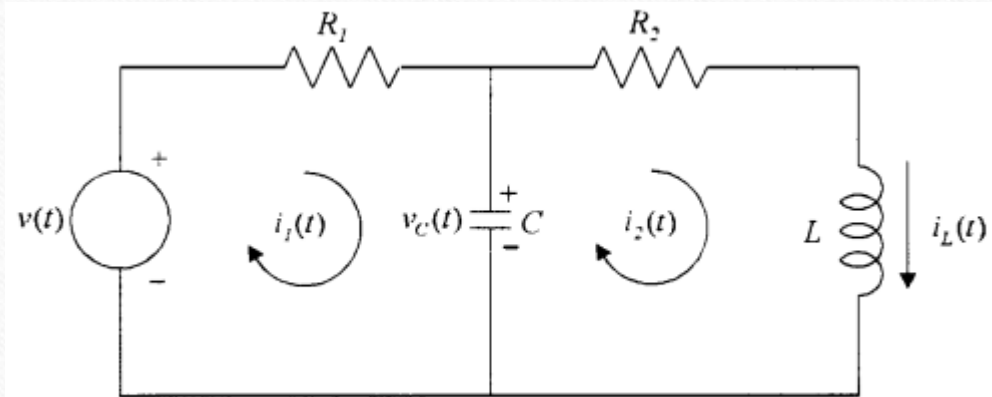
# Modeling of electrical system

- Kirchhoff's laws:
  1. Kirchhoff's voltage law. The algebraic sum of the voltages in a loop is equal to zero.
  2. Kirchhoff's current law. The algebraic sum of the currents in a node is equal to zero.





# Modeling of electrical system

- Kirchoff's laws:  
Kirchoff's voltage law. The algebraic sum of the voltages in a loop is equal to zero.

- Loop (1)


- $V(t) = V_R + V_C$

$$R_1 i_1(t) + \frac{1}{C} \int_0^t i_1(t) dt - \frac{1}{C} \int_0^t i_2(t) dt = v(t)$$

- Loop (2)

- $0 = V_R + V_C$
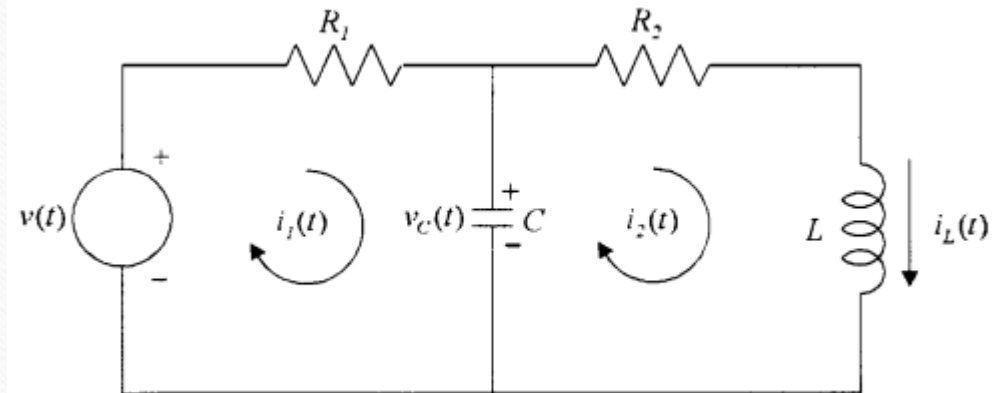
$$-\frac{1}{C} \int_0^t i_1(t) dt + R_2 i_2(t) + L \frac{di_2}{dt} + \frac{1}{C} \int_0^t i_2(t) dt = 0$$



# Modeling of electrical system

- Transfer from time domain to frequency domain:

$$R_1 i_1(t) + \frac{1}{C} \int_0^t i_1(t) dt - \frac{1}{C} \int_0^t i_2(t) dt = v(t)$$


$$\left[ R_1 + \frac{1}{Cs} \right] I_1(s) - \frac{1}{Cs} I_2(s) = V(s)$$

$$-\frac{1}{C} \int_0^t i_1(t) dt + R_2 i_2(t) + L \frac{di_2}{dt} + \frac{1}{C} \int_0^t i_2(t) dt = 0$$

$$-\frac{1}{Cs} I_1(s) + \left[ R_2 + Ls + \frac{1}{Cs} \right] I_2(s) = 0$$

- Transfer function
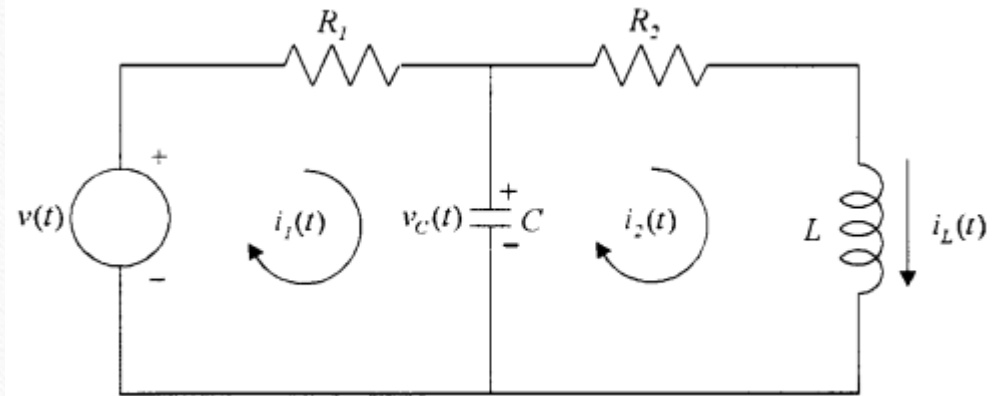
$$\frac{I_2(s)}{V(s)} = \frac{Cs}{(R_1 Cs + 1)(LCs^2 + R_2 Cs + 1) - 1} = \frac{1}{R_1 LCs^2 + (R_1 R_2 C + L)s + R_1 + R_2}$$



# Modeling of electrical system

- Analogous to Kirchhoff's laws for networks is d'Alembert's law for mechanical systems which is stated as follows:  
D'Alembert's law of forces: The sum of all forces acting upon a point mass is equal to zero.


Element	Physical variable	Linear operator	Inverse operator
Electrical Networks			
Resistor R	Voltage $v(t)$ Current $i(t)$	$v(t) = Ri(t)$	$i(t) = \frac{1}{R}v(t)$
Inductor L		$v(t) = L \frac{d}{dt}i(t)$	$i(t) = \frac{1}{L} \int_0^t v(t) dt$
Capacitor C		$v(t) = \frac{1}{C} \int_0^t i(t) dt$	$i(t) = C \frac{d}{dt}v(t)$
Mechanical Systems			
Friction coefficient B	Force $f(t)$ Velocity $v(t)$	$f(t) = Bv(t)$	$v(t) = \frac{1}{B}f(t)$
Mass m		$f(t) = m \frac{d}{dt}v(t)$	$v(t) = \frac{1}{m} \int_0^t f(t) dt$
Spring constant K		$f(t) = K \int_0^t v(t) dt$	$v(t) = \frac{1}{K} \frac{d}{dt}f(t)$



# Mathematical Modeling Of Electronic Circuits

- *Operational amplifiers*, often called *op-amps*, are important building blocks in modern electronic systems. They are used in filters in control systems and to amplify signals in sensor circuits.

$$e_o = K(e_2 - e_1) = -K(e_1 - e_2)$$

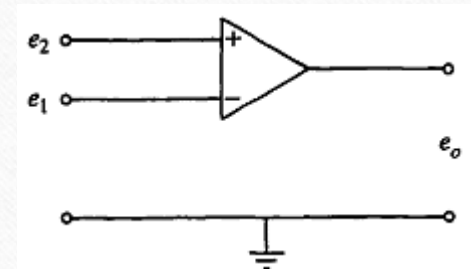

- The input e1 to the minus terminal of the amplifier is inverted; the input e2 to the plus terminal is not inverted.)

# Mathematical Modeling Of Electronic Circuits

- Let us obtain the voltage ratio  $e_o/e_i$ . In the derivation, we assume the voltage at the minus terminal as  $e'$ . This is called an *imaginary short*. Consider again the amplifier system


$$i_1 = \frac{e_i - e'}{R_1}, \quad i_2 = \frac{e' - e_o}{R_2}$$

$$\frac{e_i - e'}{R_1} = \frac{e' - e_o}{R_2}$$

- $e' = 0$ . Hence, we have

$$\frac{e_i}{R_1} = \frac{-e_o}{R_2}$$

$$e_o = -\frac{R_2}{R_1} e_i$$

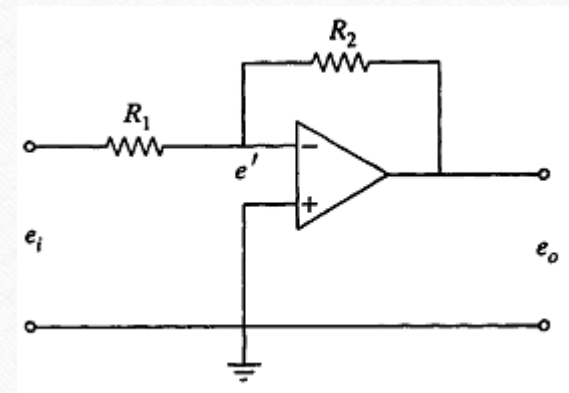




# Mathematical Modeling Of Electronic Circuits

- Obtain the relationship between the output  $e_o$  and the inputs  $e_1$ ,  $e_2$ , and  $e_3$


$$i_1 = \frac{e_1 - e'}{R_1}, \quad i_2 = \frac{e_2 - e'}{R_2}, \quad i_3 = \frac{e_3 - e'}{R_3}, \quad i_4 = \frac{e' - e_o}{R_4}$$
$$\frac{e_1 - e'}{R_1} + \frac{e_2 - e'}{R_2} + \frac{e_3 - e'}{R_3} + \frac{e_o - e'}{R_4} = 0$$

- $e' = 0$ . Hence, we have
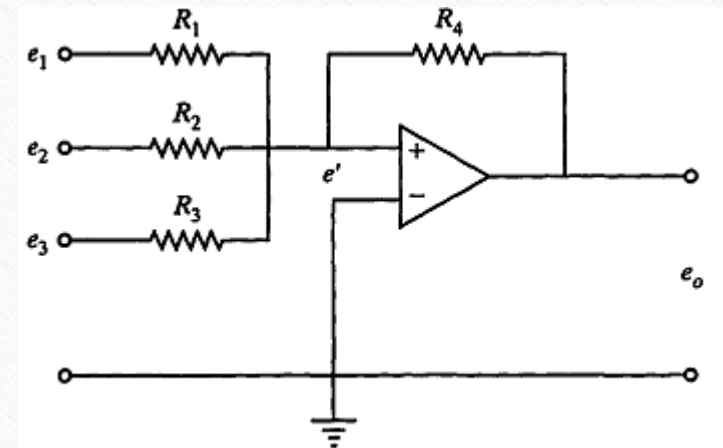
$$\frac{e_1}{R_1} + \frac{e_2}{R_2} + \frac{e_3}{R_3} + \frac{e_o}{R_4} = 0$$
$$e_o = -\frac{R_4}{R_1}e_1 - \frac{R_4}{R_2}e_2 - \frac{R_4}{R_3}e_3$$



# Modeling of Thermal System

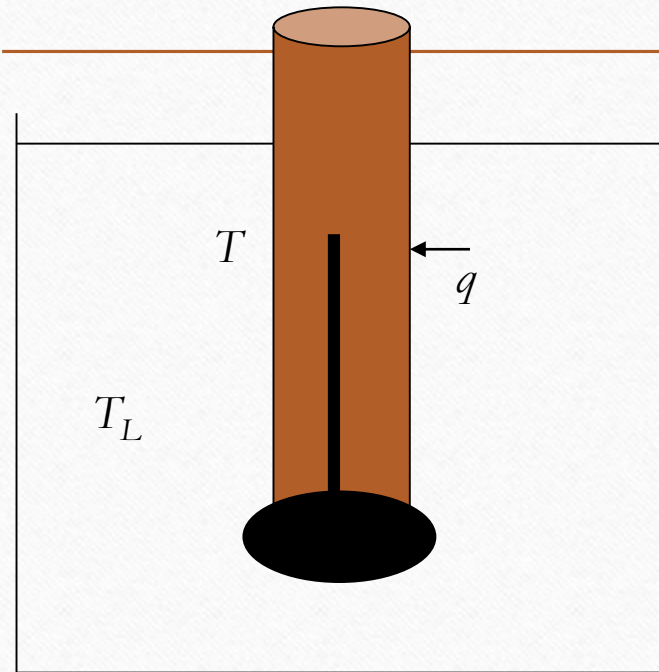

$q$  is the net rate of heat flow

$C$  is the capacitance

$R$  is the thermal resistance

$$q = \frac{T_L - T}{R}$$

$$q_1 - q_2 = C \frac{dT}{dt}; q = C \frac{dT}{dt}$$

$$C \frac{dT}{dt} = \frac{T_L - T}{R}$$

$$RC \frac{dT}{dt} + T = T_L$$

# Mathematical Modeling Of A Thermal System

- Input – output = stored

$$q_i(t) - q_o(t) = q_{stored}$$


$$q_{stored} = c \frac{d\theta(t)}{dt}$$

$$q_o = K\Delta\theta$$

- The coefficient  $K$  is given by

$$K = \frac{kA}{\Delta X} \quad \text{for conduction}$$
$$= HA \quad \text{for convection}$$
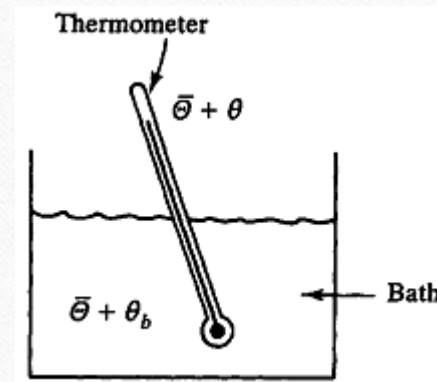
$$RC \frac{d\theta}{dt} + \theta = \theta_b$$




$$R = \frac{\text{change in temperature difference}}{\text{change in heat flow rate}}$$

$$R = \frac{d(\Delta\theta)}{dq} = \frac{\Delta\theta}{q}$$




# Modeling of Motors

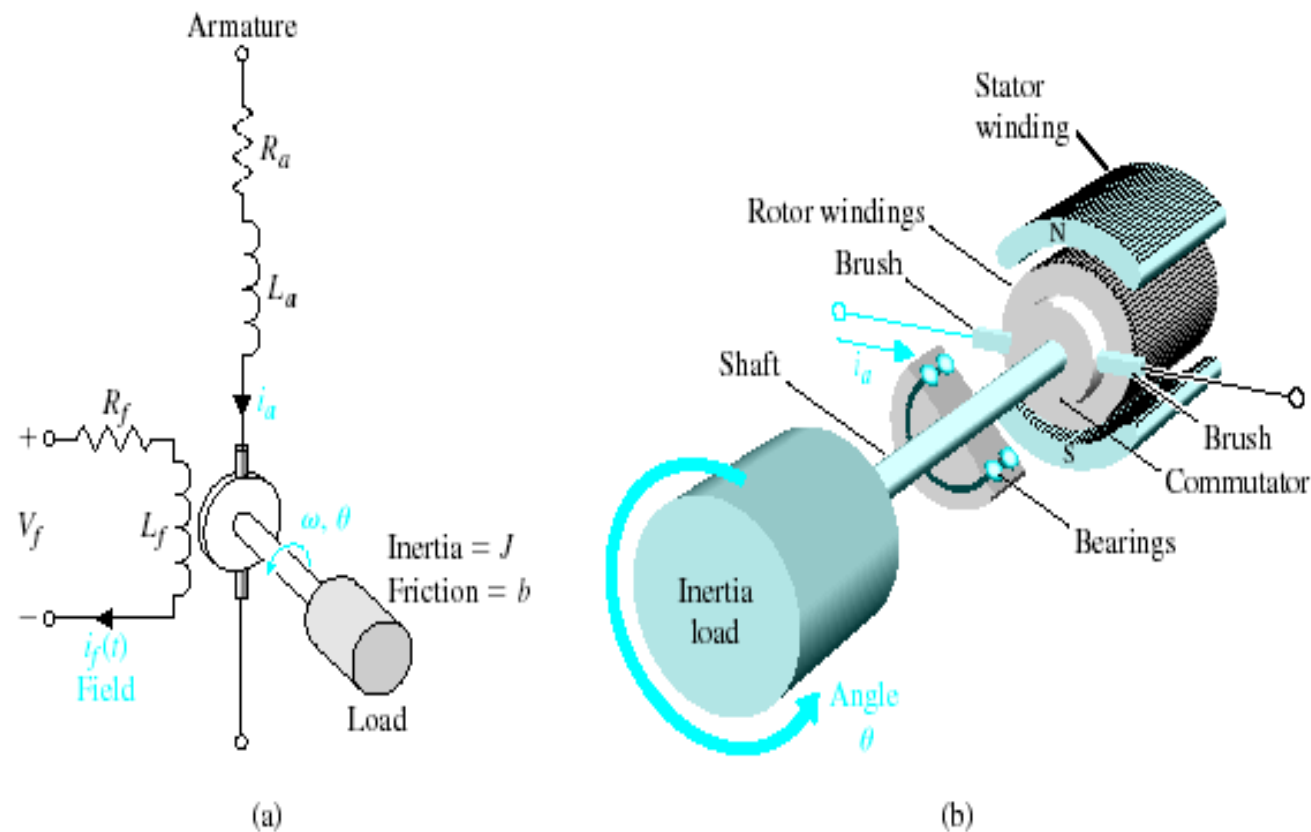


A dc motor (a) wiring diagram and (b) sketch.

# Modeling of Motors

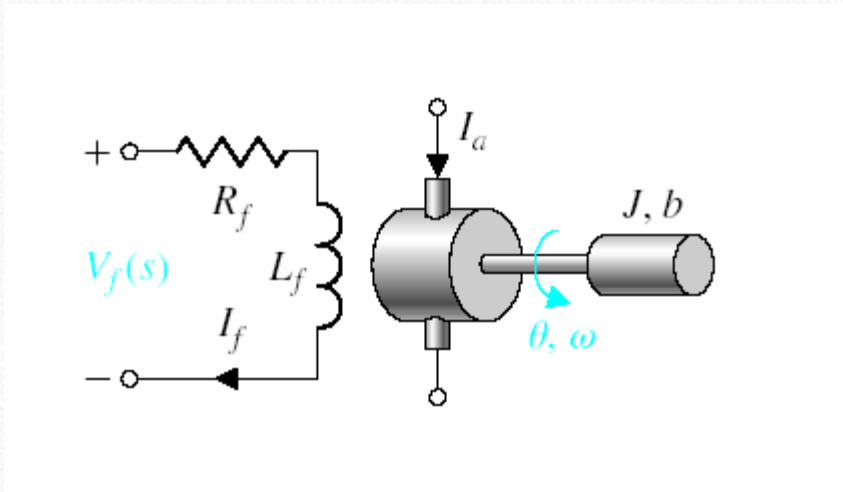
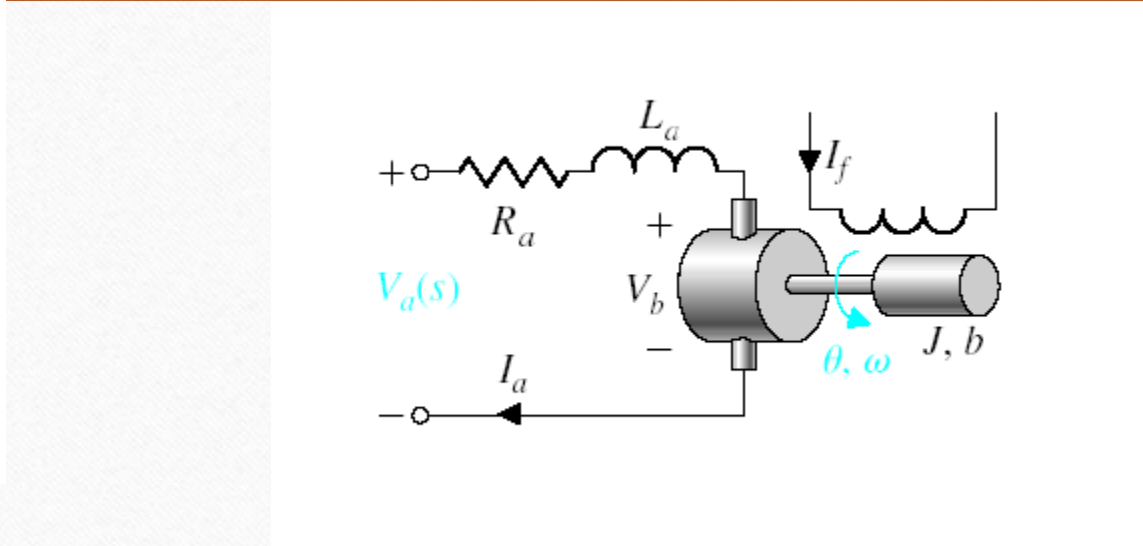
$$\frac{\theta(s)}{V_f(s)} = \frac{K_m}{s \cdot (J \cdot s + b) (L_f \cdot s + R_f)}$$



$$\frac{\theta(s)}{V_a(s)} = \frac{K_m}{s \cdot [(R_a + L_a \cdot s) (J \cdot s + b) + K_b \cdot K_m]}$$





# Analogy


- Force – voltage analogy

$$L \frac{di}{dt} + Ri + \frac{1}{C} \int i dt = e$$


In terms of the electric charge  $q$ , this last equation becomes

$$L \frac{d^2q}{dt^2} + R \frac{dq}{dt} + \frac{1}{C} q = e$$

Mechanical Systems	Electrical Systems
Force $p$ (torque $T$ )	Voltage $e$
Mass $m$ (moment of inertia $J$ )	Inductance $L$
Viscous-friction coefficient $b$	Resistance $R$
Spring constant $k$	Reciprocal of capacitance, $1/C$
Displacement $x$ (angular displacement $\theta$ )	Charge $q$
Velocity $\dot{x}$ (angular velocity $\dot{\theta}$ )	Current $i$

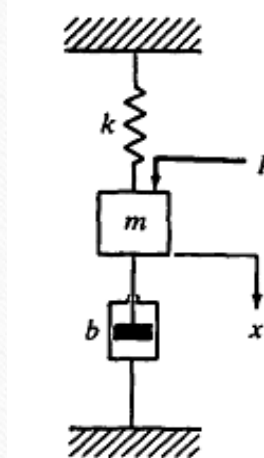
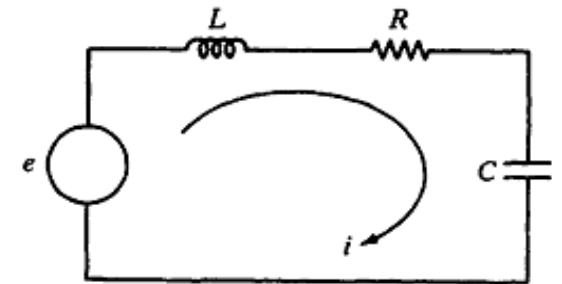
$$m \frac{d^2x}{dt^2} + b \frac{dx}{dt} + kx = p$$



$$L \frac{d^2q}{dt^2} + R \frac{dq}{dt} + \frac{1}{C} q = e$$

# Analogy


- Force – current analogy

$$\frac{1}{L} \int e \, dt + \frac{e}{R} + C \frac{de}{dt} = i_s$$


In terms of the magnetic flux  $\psi$ , this last equation becomes

$$C \frac{d^2\psi}{dt^2} + \frac{1}{R} \frac{d\psi}{dt} + \frac{1}{L} \psi = i_s$$

Mechanical Systems	Electrical Systems
Force $p$ (torque $T$ )	Current $i$
Mass $m$ (moment of inertia $J$ )	Capacitance $C$
Viscous-friction coefficient $b$	Reciprocal of resistance, $1/R$
Spring constant $k$	Reciprocal of inductance, $1/L$
Displacement $x$ (angular displacement $\theta$ )	Magnetic flux linkage $\psi$
Velocity $\dot{x}$ (angular velocity $\dot{\theta}$ )	Voltage $e$

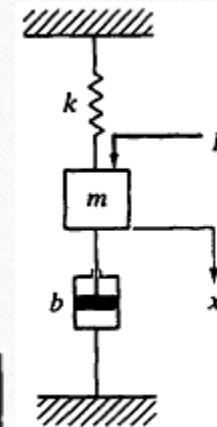

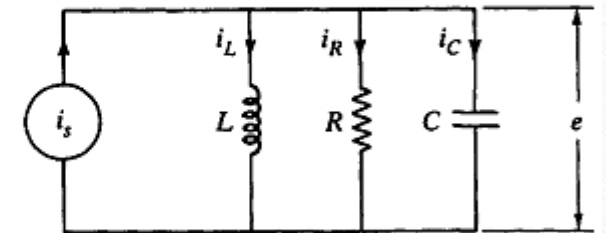
$$m \frac{d^2x}{dt^2} + b \frac{dx}{dt} + kx = p$$




$$C \frac{d^2\psi}{dt^2} + \frac{1}{R} \frac{d\psi}{dt} + \frac{1}{L} \psi = i_s$$

# Modeling of Motors


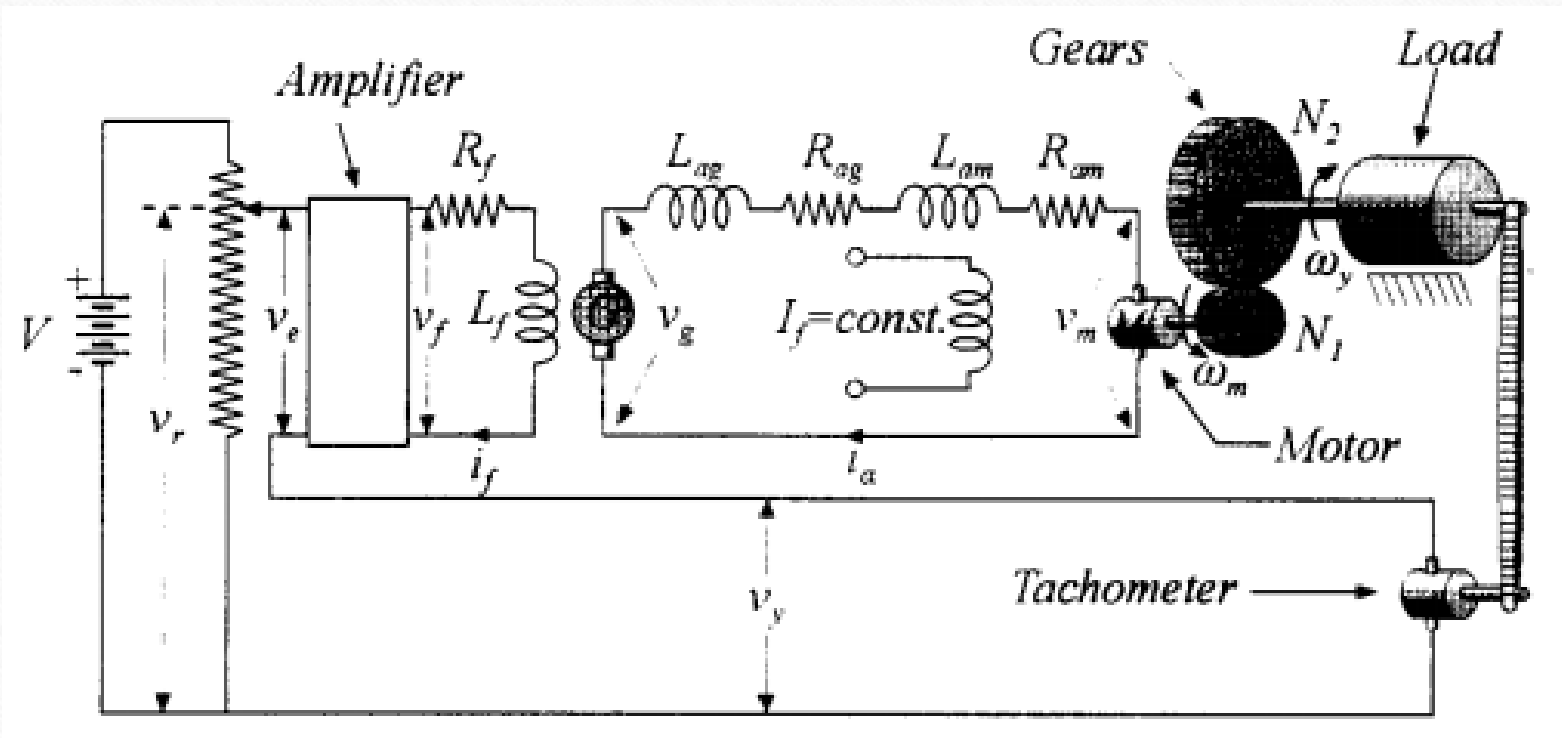




# Modeling of Motors

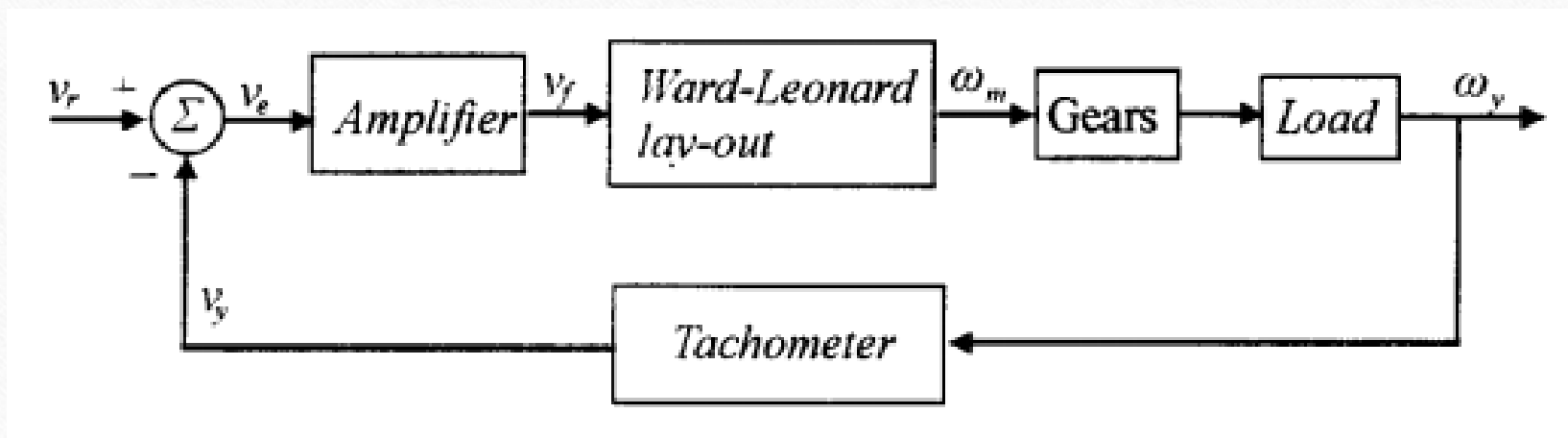

# Modeling of Motors

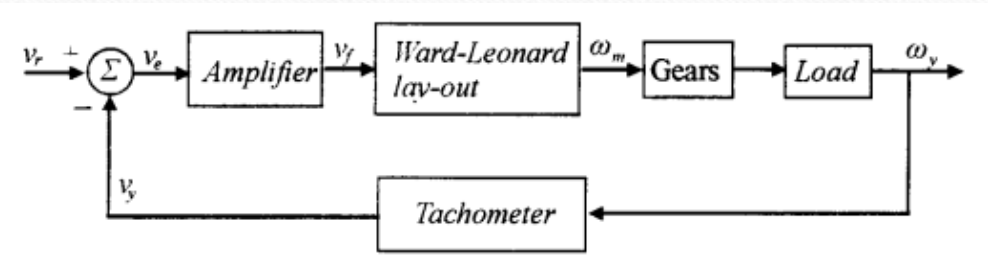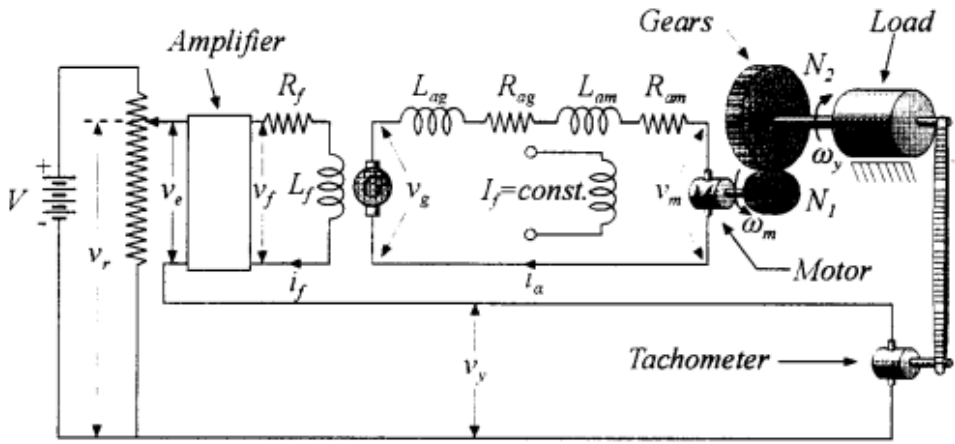

# Mathematical Modeling

The equations of the Ward–Leonard layout are as follows . The Kirchhoff's law of voltages of the excitation field of the generator G is

$$v_f = R_f i_f + L_f \frac{di_f}{dt}$$

The voltage  $v_g$  of the generator G is proportional to the current  $i_f$ , i.e.,

$$v_g = K_g i_f$$

The voltage  $v_m$  of the motor M is proportional to the angular velocity  $\omega_m$ , i.e.,


$$v_m = K_b \omega_m$$

The differential equation for the current  $i_a$  is

$$R_a i_a + L_a \frac{di_a}{dt} = v_g - v_m = K_g i_f - K_b \omega_m$$

The torque  $T_m$  of the motor is proportional to the current  $i_a$

$$T_m = K_m i_a$$

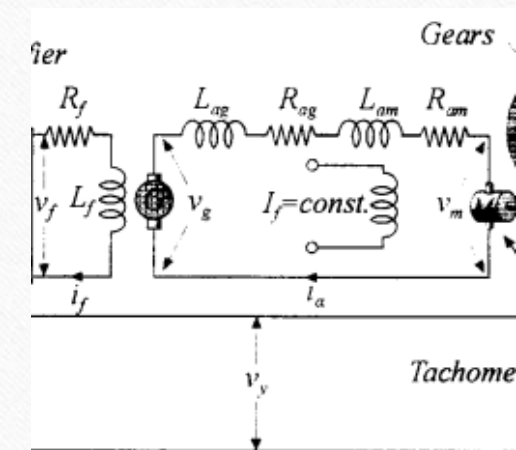






# Mathematical Modeling

The mathematical model of the Ward–Leonard layout are as follows .

$$\frac{\Omega_y(s)}{V_f(s)} = \frac{K_g K_m N}{(L_f s + R_f)[(L_a s + R_a)(J_m^* s + B_m^*) + K_m K_b]}$$
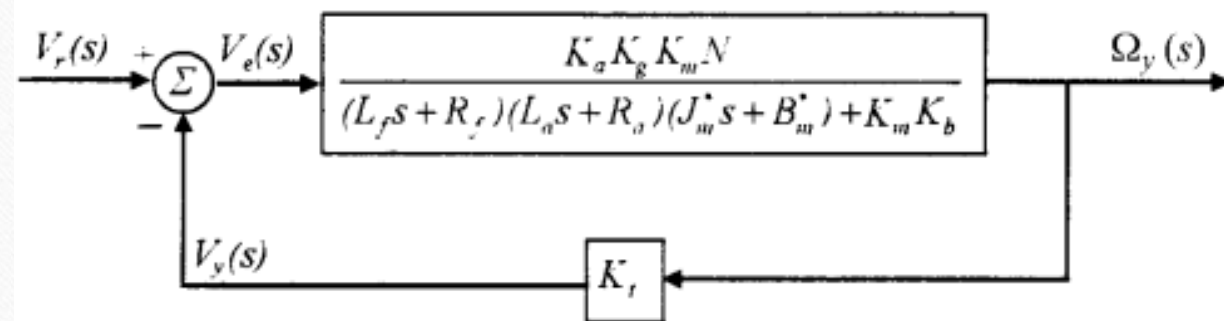
$$\frac{\Omega_y(s)}{v_e(s)} = \frac{K_a K_g K_m N}{(L_f s + R_f)[(L_a s + R_a)(J_m^* s + B_m^*) + K_m K_b]}$$





# Analogy


- Force – voltage analogy

$$L \frac{di}{dt} + Ri + \frac{1}{C} \int i dt = e$$


In terms of the electric charge  $q$ , this last equation becomes

$$L \frac{d^2q}{dt^2} + R \frac{dq}{dt} + \frac{1}{C} q = e$$

Mechanical Systems	Electrical Systems
Force $p$ (torque $T$ )	Voltage $e$
Mass $m$ (moment of inertia $J$ )	Inductance $L$
Viscous-friction coefficient $b$	Resistance $R$
Spring constant $k$	Reciprocal of capacitance, $1/C$
Displacement $x$ (angular displacement $\theta$ )	Charge $q$
Velocity $\dot{x}$ (angular velocity $\dot{\theta}$ )	Current $i$

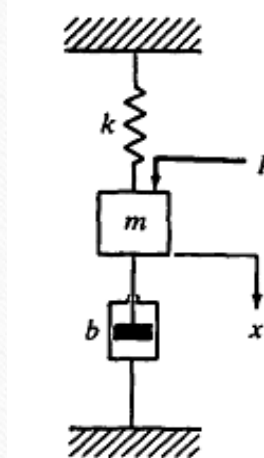
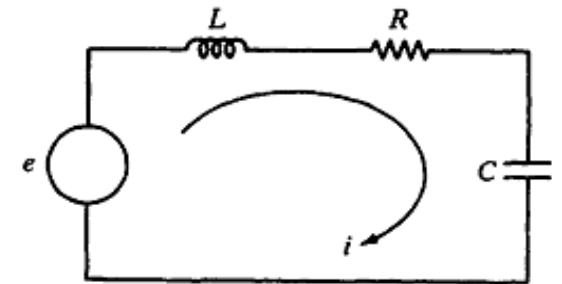
$$m \frac{d^2x}{dt^2} + b \frac{dx}{dt} + kx = p$$



$$L \frac{d^2q}{dt^2} + R \frac{dq}{dt} + \frac{1}{C} q = e$$



# Analogy


- Force – current analogy

$$\frac{1}{L} \int e \, dt + \frac{e}{R} + C \frac{de}{dt} = i_s$$


In terms of the magnetic flux  $\psi$ , this last equation becomes

$$C \frac{d^2\psi}{dt^2} + \frac{1}{R} \frac{d\psi}{dt} + \frac{1}{L} \psi = i_s$$

Mechanical Systems	Electrical Systems
Force $p$ (torque $T$ )	Current $i$
Mass $m$ (moment of inertia $J$ )	Capacitance $C$
Viscous-friction coefficient $b$	Reciprocal of resistance, $1/R$
Spring constant $k$	Reciprocal of inductance, $1/L$
Displacement $x$ (angular displacement $\theta$ )	Magnetic flux linkage $\psi$
Velocity $\dot{x}$ (angular velocity $\dot{\theta}$ )	Voltage $e$

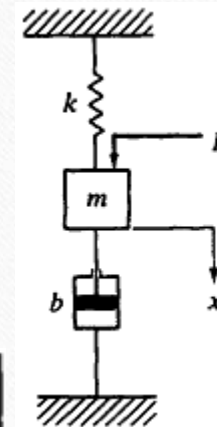
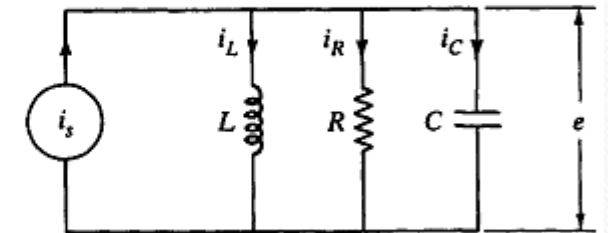
$$m \frac{d^2x}{dt^2} + b \frac{dx}{dt} + kx = p$$



$$C \frac{d^2\psi}{dt^2} + \frac{1}{R} \frac{d\psi}{dt} + \frac{1}{L} \psi = i_s$$

# Model Examples

- Stepper motor

