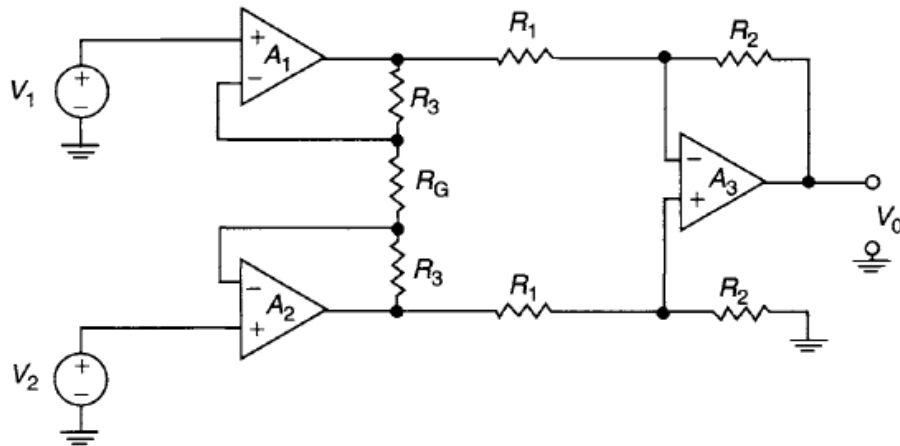


### Assignment (Measurements)

- Explain the operation and usage of the different types of signal conditioning for measurement devices such as filters and amplifiers.
- Draw a block diagram to show different parts of DAQ system, hence write the required technical specification during the selection of DAQ system.
- We are given a 12 bit analog input with a range of -10V to 10V. If we put in 2.735V, what will the integer value be after the A/D conversion? What is the error? What voltage can we calculate?
- For the instrumentation amplifier circuit shown in Figure,  
 $R_1 = 5\text{ k}\Omega$ ;  $R_2 = 20\text{ k}\Omega$ ;  $R_3 = 15\text{ k}\Omega$ ;  $R_G = 3\text{ k}\Omega$ ;  
 $V_1 = 10\text{ V}$ ;  $V_2 = 15\text{ V}$ .

Determine (a) the gain; (b) the output voltage.



- Draw the low-pass active filter with input resistance  $R_1$ ,

$$R_1 = 5\text{ k}\Omega; \quad R_2 = 20\text{ k}\Omega;$$

$$C = 2\text{ }\mu\text{F}.$$

Determine the closed-loop gain and the decibel value at which the filter rolls off.

- Draw the summing amplifier with output resistance  $R_f$ , so determine the following:

$$R_F = 10\text{ k}\Omega; \quad R_1 = 6\text{ k}\Omega; \quad R_2 = 6\text{ k}\Omega; \quad R_3 = 6\text{ k}\Omega;$$

$$V_1 = V_2 = V_3 = 5\text{ V}.$$

Determine the output voltage.

- g) Draw the differential amplifier with inputs resistance  $R_1$ ,

$$R_1 = 5 \text{ k}\Omega; \quad R_2 = 15 \text{ k}\Omega;$$

$$V_1 = 10 \text{ V}; \quad V_2 = 15 \text{ V}.$$

Determine the output voltage for these values and for when  $R^{\wedge} = R_2$ .

- h) You need to read an analog voltage that has a range of -10V to 10V to a precision of +/- 0.05V. What resolution of A/D converter is needed?
- i) We are given a 12 bit analog input with a range of -10V to 10V. If we put in 2.735V, what will the integer value be after the A/D conversion? What is the error? What voltage can we calculate?
- j) A first order instrument is to measure signals with frequency content up to 100 Hz with an inaccuracy of 5%. What is the maximum allowable time constant? What will be the phase shift at 50 and 100 Hz?