

Industrial Process Control

If you have a smart project, you can say "I'm an engineer"

Lecture 3

Staff boarder

Dr. Mostafa Elsayed Abdelmonem


Industrial Process Control

MDP 454

- **Lecture aims:**
 - Facilitate combining and manipulating differential equations
 - Identify the equations of motion of systems
 - Understand the mathematical modeling of all systems and combination

Modeling of electrical system

Electrical Inductance

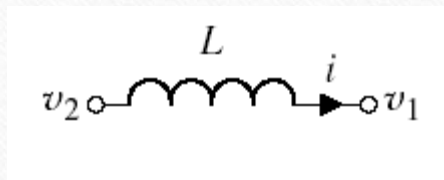

Describing Equation

source (i)

$$i = \frac{1}{L} \int v_{21} dt$$

Describing Equation

source (v)

$$v_{21} = L \frac{d}{dt} i$$


Electrical Capacitance



$$i = C \cdot \frac{d}{dt} v_{21}$$

$$v_{21} = \frac{1}{C} \int i dt$$

Electrical Resistance

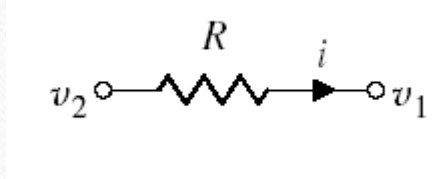


$$i = \frac{1}{R} \cdot v_{21}$$

$$v_{21} = iR$$

Modeling of electrical system


RLC circuit.

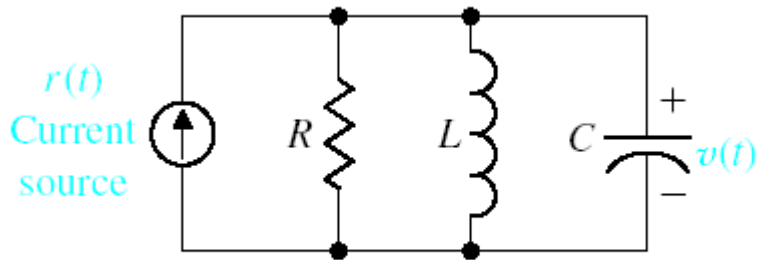

$$\frac{v(t)}{R} + C \cdot \frac{d}{dt} v(t) + \frac{1}{L} \cdot \int_0^t v(t) dt = r(t)$$

Modeling of electrical system


RLC circuit.

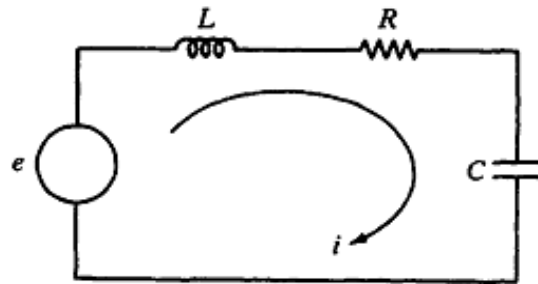

$$L \frac{di}{dt} + Ri + \frac{1}{C} \int i dt = e$$

Modeling of electrical system

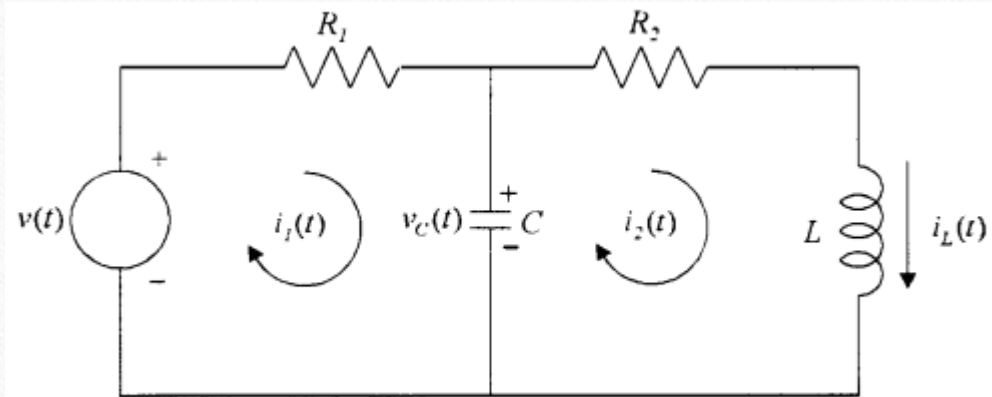- Kirchhoff's laws:
 1. Kirchhoff's voltage law. The algebraic sum of the voltages in a loop is equal to zero.
 2. Kirchhoff's current law. The algebraic sum of the currents in a node is equal to zero.



Modeling of electrical system

- Transfer from time domain to frequency domain:

$$R_1 i_1(t) + \frac{1}{C} \int_0^t i_1(t) dt - \frac{1}{C} \int_0^t i_2(t) dt = v(t)$$


$$\left[R_1 + \frac{1}{Cs} \right] I_1(s) - \frac{1}{Cs} I_2(s) = V(s)$$

$$-\frac{1}{C} \int_0^t i_1(t) dt + R_2 i_2(t) + L \frac{di_2}{dt} + \frac{1}{C} \int_0^t i_2(t) dt = 0$$

$$-\frac{1}{Cs} I_1(s) + \left[R_2 + Ls + \frac{1}{Cs} \right] I_2(s) = 0$$


- Transfer function
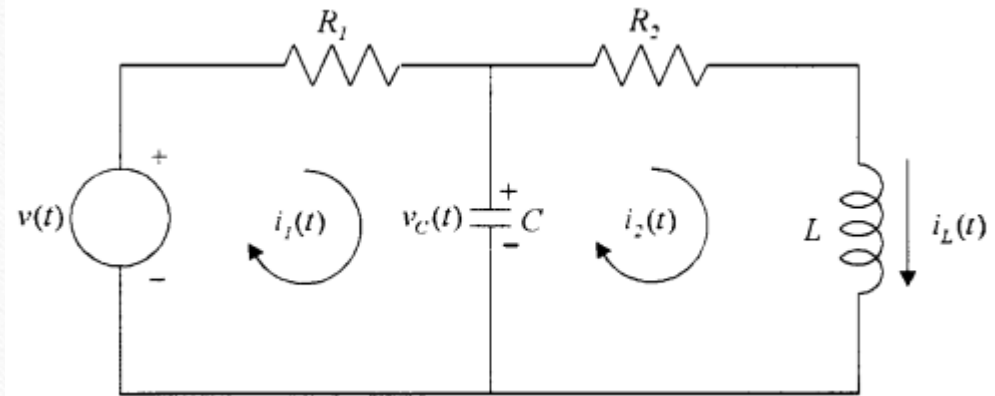
$$\frac{I_2(s)}{V(s)} = \frac{Cs}{(R_1 Cs + 1)(LCs^2 + R_2 Cs + 1) - 1} = \frac{1}{R_1 LCs^2 + (R_1 R_2 C + L)s + R_1 + R_2}$$



Modeling of electrical system

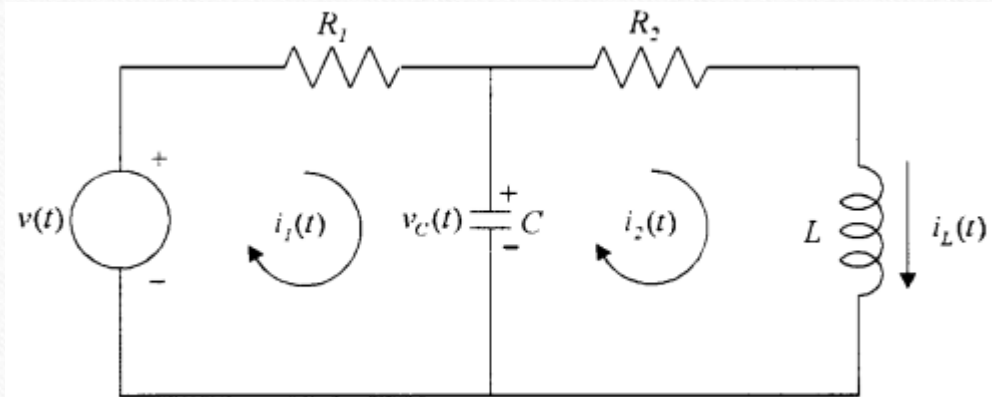- Kirchhoff's laws:
 1. Kirchhoff's voltage law. The algebraic sum of the voltages in a loop is equal to zero.
 2. Kirchhoff's current law. The algebraic sum of the currents in a node is equal to zero.



Modeling of electrical system

- Kirchoff's laws:
Kirchoff's voltage law. The algebraic sum of the voltages in a loop is equal to zero.

- Loop (1)


- $V(t) = V_R + V_C$

$$R_1 i_1(t) + \frac{1}{C} \int_0^t i_1(t) dt - \frac{1}{C} \int_0^t i_2(t) dt = v(t)$$

- Loop (2)

- $0 = V_R + V_C$
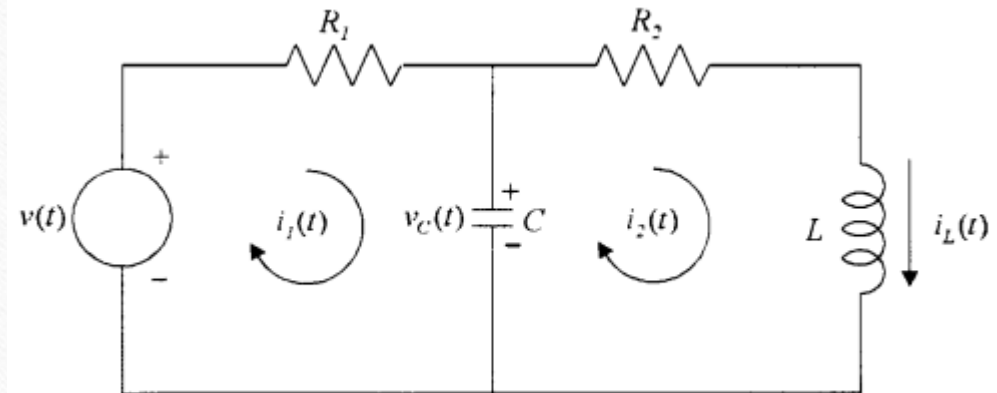
$$-\frac{1}{C} \int_0^t i_1(t) dt + R_2 i_2(t) + L \frac{di_2}{dt} + \frac{1}{C} \int_0^t i_2(t) dt = 0$$



Modeling of electrical system

- Transfer from time domain to frequency domain:

$$R_1 i_1(t) + \frac{1}{C} \int_0^t i_1(t) dt - \frac{1}{C} \int_0^t i_2(t) dt = v(t)$$


$$\left[R_1 + \frac{1}{Cs} \right] I_1(s) - \frac{1}{Cs} I_2(s) = V(s)$$

$$-\frac{1}{C} \int_0^t i_1(t) dt + R_2 i_2(t) + L \frac{di_2}{dt} + \frac{1}{C} \int_0^t i_2(t) dt = 0$$


$$-\frac{1}{Cs} I_1(s) + \left[R_2 + Ls + \frac{1}{Cs} \right] I_2(s) = 0$$

- Transfer function
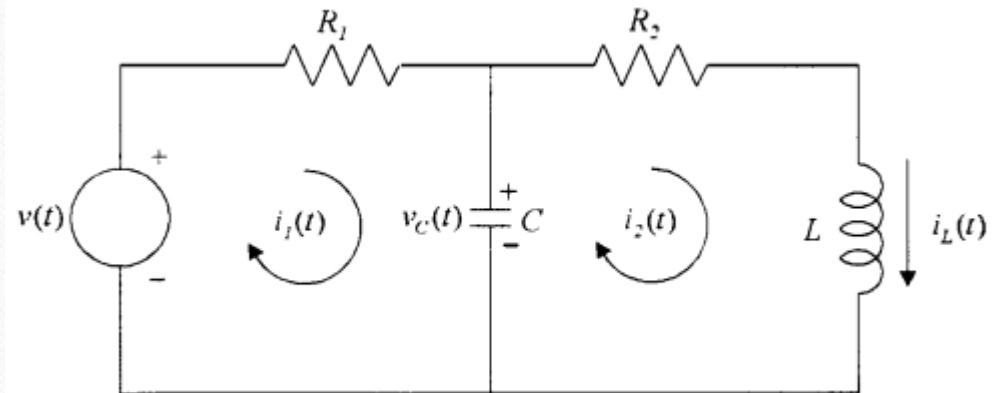
$$\frac{I_2(s)}{V(s)} = \frac{Cs}{(R_1 Cs + 1)(LCs^2 + R_2 Cs + 1) - 1} = \frac{1}{R_1 LCs^2 + (R_1 R_2 C + L)s + R_1 + R_2}$$




Modeling of electrical system

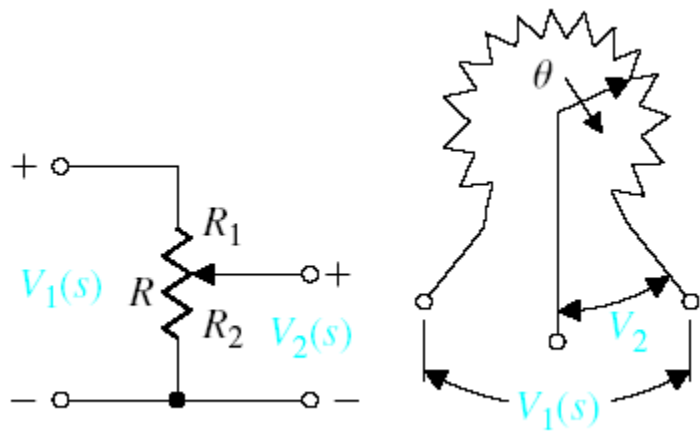

$$\frac{V_2(s)}{V_1(s)} = \frac{R_2}{R} = \frac{R_2}{R_1 + R_2}$$
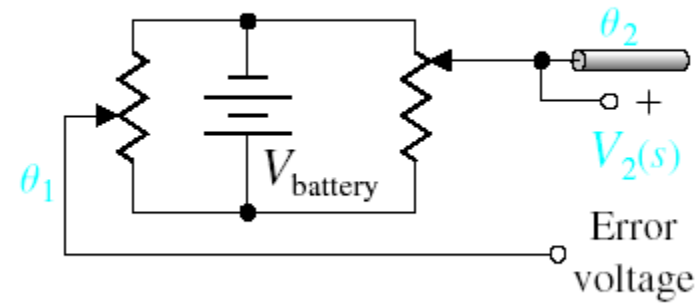
$$\frac{R_2}{R} = \frac{\theta}{\theta_{\max}}$$



$$V_2(s) = k_s(\theta_1(s) - \theta_2(s))$$

$$V_2(s) = k_s \cdot \theta_{\text{error}}(s)$$

$$k_s = \frac{V_{\text{battery}}}{\theta_{\max}}$$



Modeling of electrical system

- Analogous to Kirchhoff's laws for networks is d'Alembert's law for mechanical systems which is stated as follows:
D'Alembert's law of forces: The sum of all forces acting upon a point mass is equal to zero.

Element	Physical variable	Linear operator	Inverse operator
Electrical Networks			
Resistor R	Voltage $v(t)$ Current $i(t)$	$v(t) = Ri(t)$	$i(t) = \frac{1}{R}v(t)$
Inductor L		$v(t) = L \frac{d}{dt}i(t)$	$i(t) = \frac{1}{L} \int_0^t v(t) dt$
Capacitor C		$v(t) = \frac{1}{C} \int_0^t i(t) dt$	$i(t) = C \frac{d}{dt}v(t)$
Mechanical Systems			
Friction coefficient B	Force $f(t)$ Velocity $v(t)$	$f(t) = Bv(t)$	$v(t) = \frac{1}{B}f(t)$
Mass m		$f(t) = m \frac{d}{dt}v(t)$	$v(t) = \frac{1}{m} \int_0^t f(t) dt$
Spring constant K		$f(t) = K \int_0^t v(t) dt$	$v(t) = \frac{1}{K} \frac{d}{dt}f(t)$

Mathematical Modeling Of Electronic Circuits

The ideal op-amp.

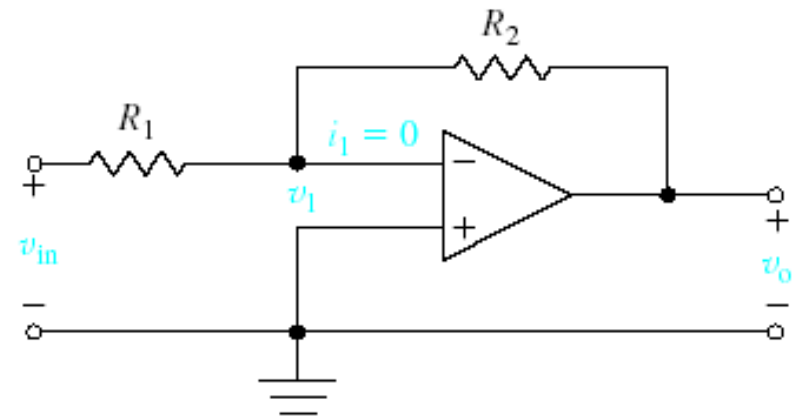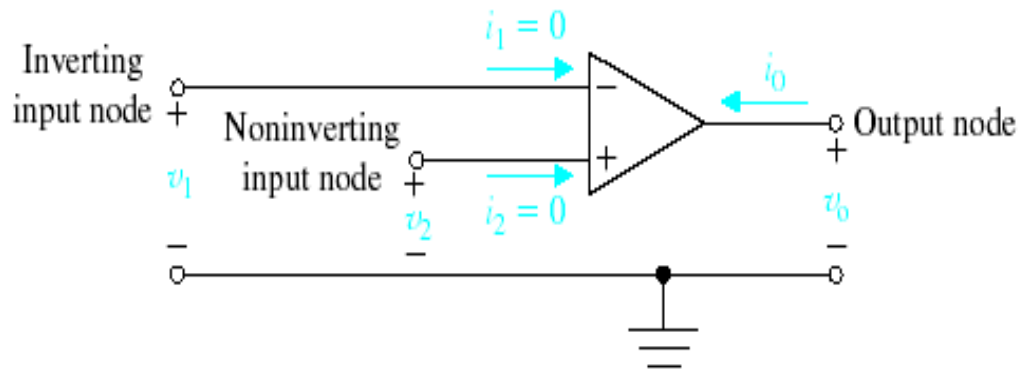


An inverting amplifier operating with ideal conditions.

Mathematical Modeling Of Electronic Circuits

- *Operational amplifiers*, often called *op-amps*, are important building blocks in modern electronic systems. They are used in filters in control systems and to amplify signals in sensor circuits.

$$e_o = K(e_2 - e_1) = -K(e_1 - e_2)$$

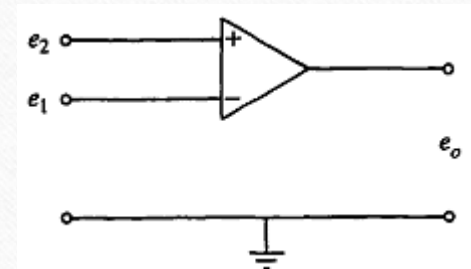

- The input e1 to the minus terminal of the amplifier is inverted; the input e2 to the plus terminal is not inverted.)

Mathematical Modeling Of Electronic Circuits

- Let us obtain the voltage ratio e_o/e_i . In the derivation, we assume the voltage at the minus terminal as e' . This is called an *imaginary short*. Consider again the amplifier system


$$i_1 = \frac{e_i - e'}{R_1}, \quad i_2 = \frac{e' - e_o}{R_2}$$

$$\frac{e_i - e'}{R_1} = \frac{e' - e_o}{R_2}$$

- $e' = 0$. Hence, we have

$$\frac{e_i}{R_1} = \frac{-e_o}{R_2}$$

$$e_o = -\frac{R_2}{R_1} e_i$$

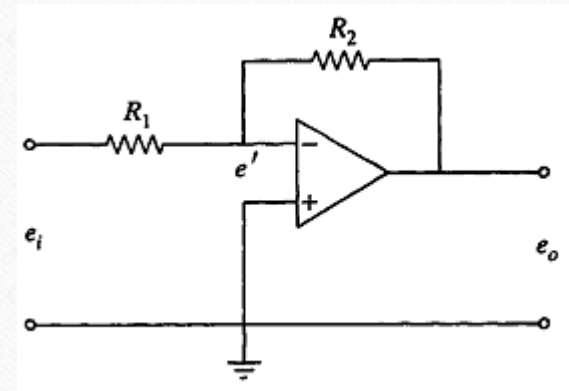


Mathematical Modeling Of Electronic Circuits

- Obtain the relationship between the output e_o and the inputs e_1 , e_2 , and e_3


$$i_1 = \frac{e_1 - e'}{R_1}, \quad i_2 = \frac{e_2 - e'}{R_2}, \quad i_3 = \frac{e_3 - e'}{R_3}, \quad i_4 = \frac{e' - e_o}{R_4}$$
$$\frac{e_1 - e'}{R_1} + \frac{e_2 - e'}{R_2} + \frac{e_3 - e'}{R_3} + \frac{e_o - e'}{R_4} = 0$$

- $e' = 0$. Hence, we have
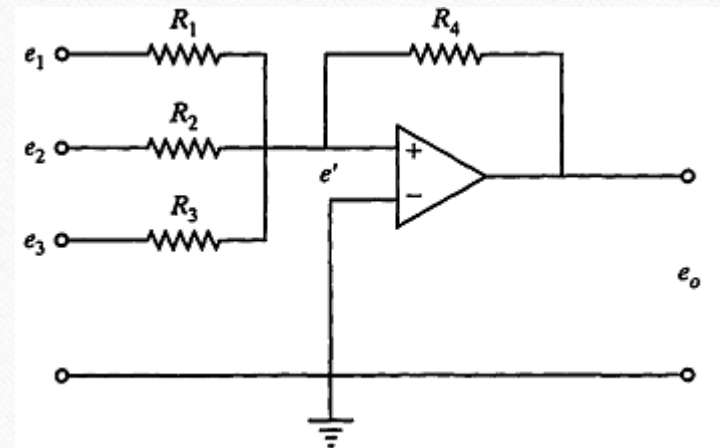
$$\frac{e_1}{R_1} + \frac{e_2}{R_2} + \frac{e_3}{R_3} + \frac{e_o}{R_4} = 0$$
$$e_o = -\frac{R_4}{R_1}e_1 - \frac{R_4}{R_2}e_2 - \frac{R_4}{R_3}e_3$$




Modeling of Motors

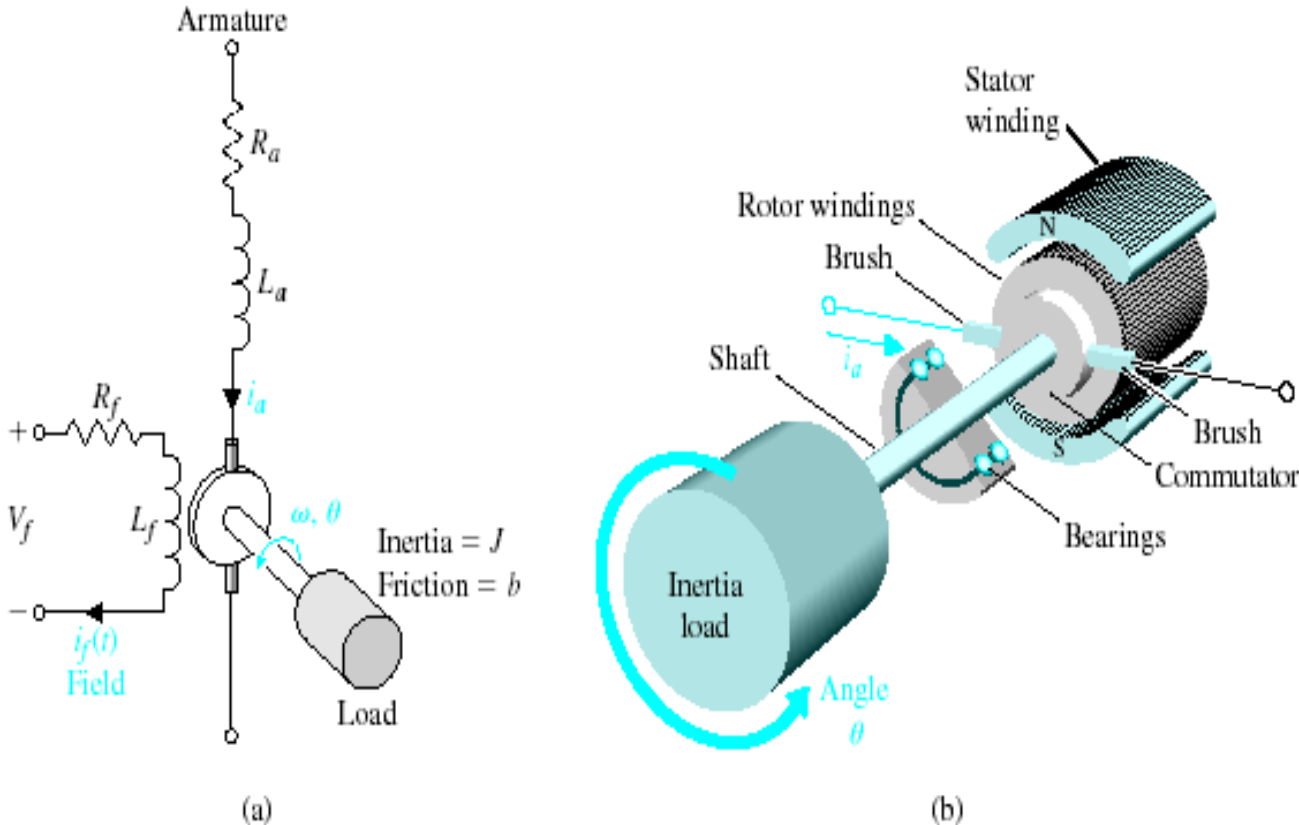


A dc motor (a) wiring diagram and (b) sketch.

Modeling of Motors

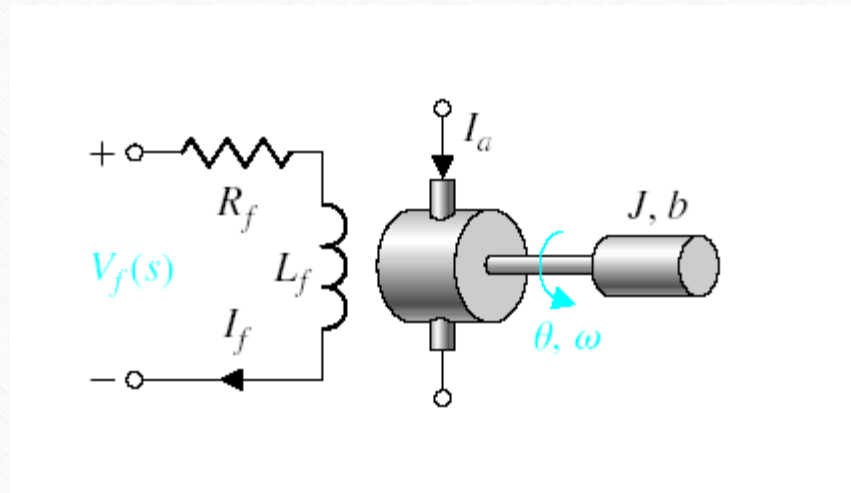

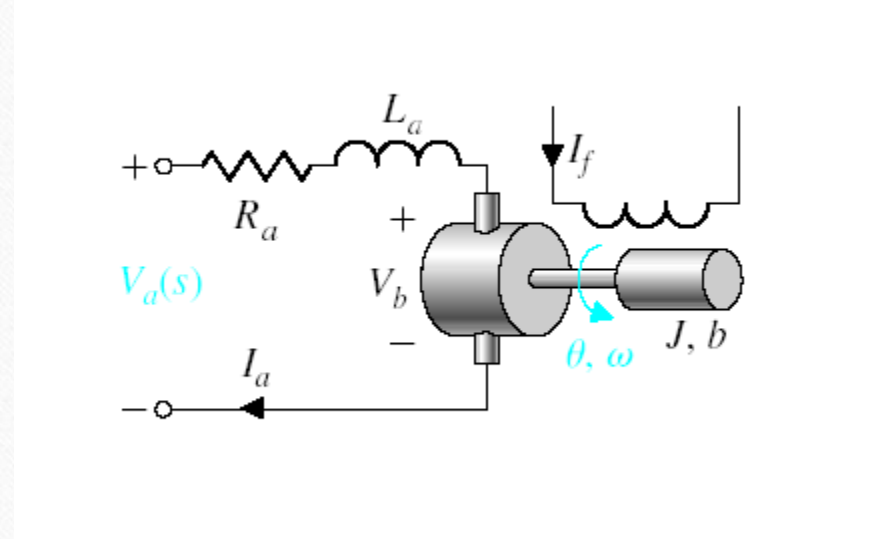
$$\frac{\theta(s)}{V_f(s)} = \frac{K_m}{s \cdot (J \cdot s + b) (L_f \cdot s + R_f)}$$




$$\frac{\theta(s)}{V_a(s)} = \frac{K_m}{s \cdot [(R_a + L_a \cdot s) (J \cdot s + b) + K_b \cdot K_m]}$$





Modeling of Motors

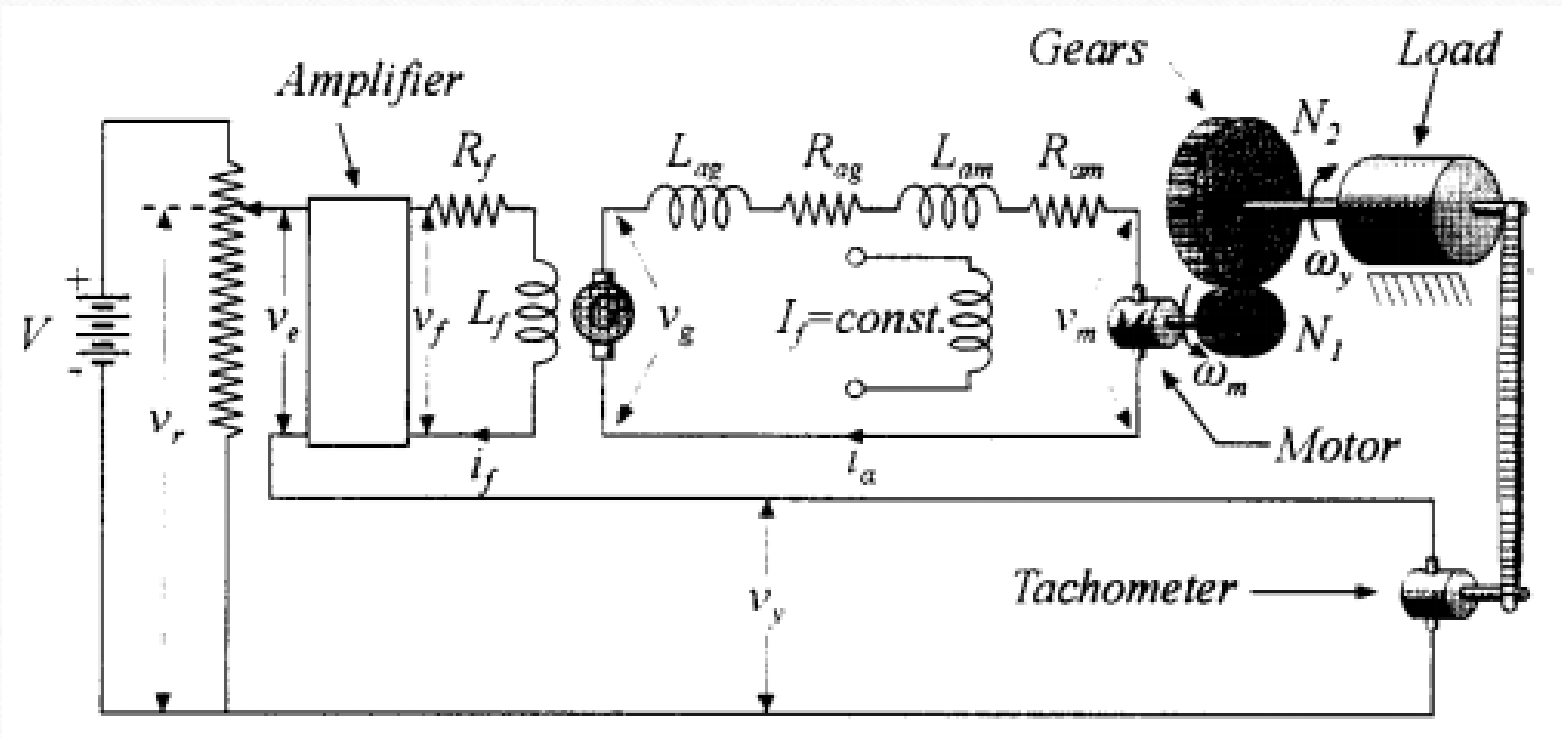

Modeling of Motors

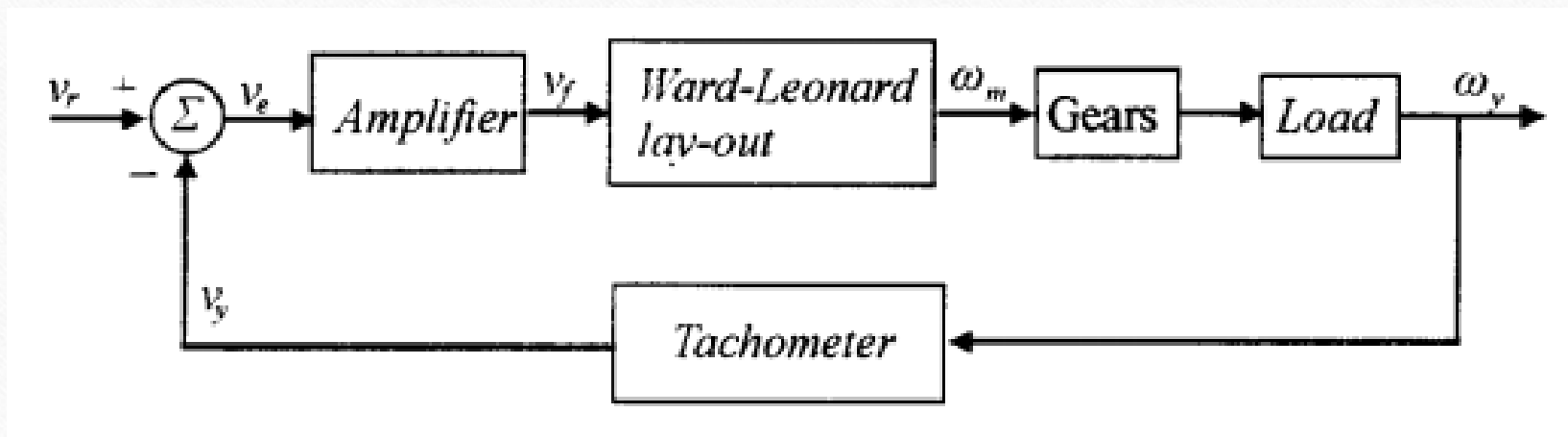

Modeling of Motors

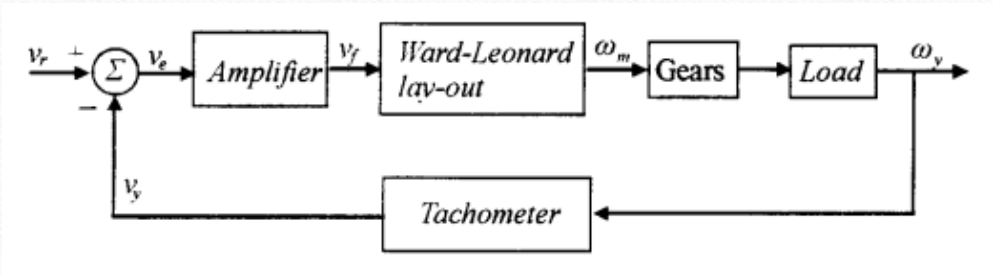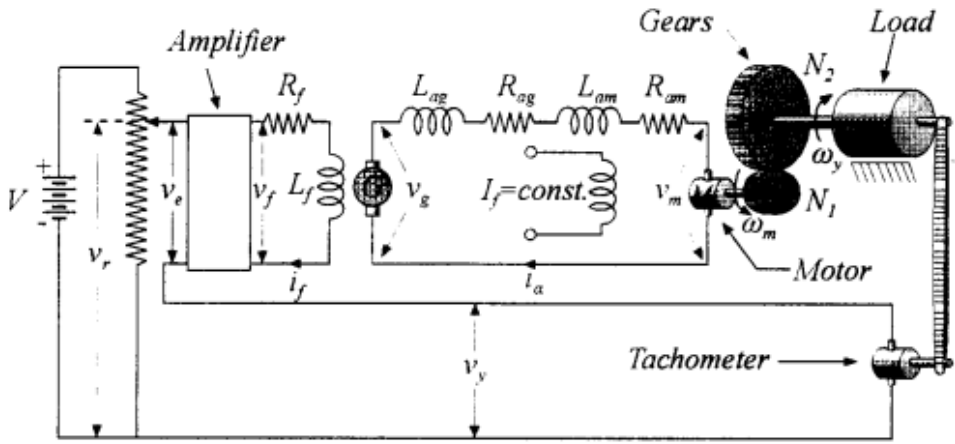

Mathematical Modeling

The equations of the Ward–Leonard layout are as follows . The Kirchhoff's law of voltages of the excitation field of the generator G is

$$v_f = R_f i_f + L_f \frac{di_f}{dt}$$

The voltage v_g of the generator G is proportional to the current i_f , i.e.,

$$v_g = K_g i_f$$

The voltage v_m of the motor M is proportional to the angular velocity ω_m , i.e.,


$$v_m = K_b \omega_m$$

The differential equation for the current i_a is

$$R_a i_a + L_a \frac{di_a}{dt} = v_g - v_m = K_g i_f - K_b \omega_m$$

The torque T_m of the motor is proportional to the current i_a

$$T_m = K_m i_a$$

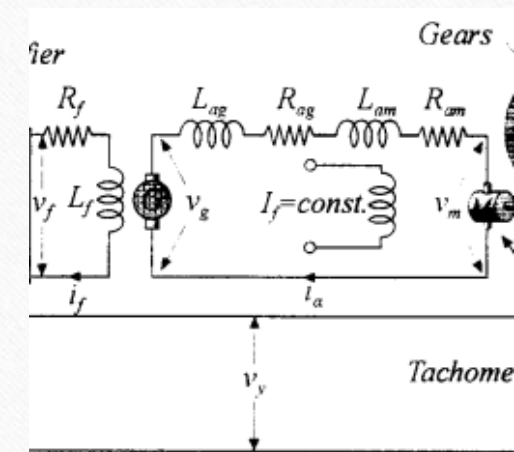

Mathematical Modeling

The equations of the Ward–Leonard layout are as follows . The Kirchhoff's law of voltages of the excitation field of the generator G is

The rotational motion of the rotor is described by

$$J_m^* \frac{d\omega_m}{dt} + B_m^* \omega_m = K_m i_a$$

where $J_m^* = J_m + N^2 J_L$ and $B_m^* = B_m + N^2 B_L$, where $N = N_1/N_2$.

Here, J_m is the moment of inertia and B_m the viscosity coefficient of the motor: likewise, for J_L and B_L of the load.

where use was made of the relation


$$\omega_y = N \omega_m.$$

The tachometer equation

$$v_y = K_t \omega_y$$

the amplifier equation

$$v_f = K_a v_e$$

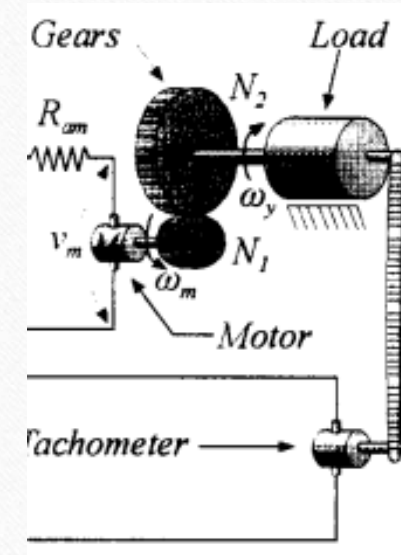


Mathematical Modeling

The mathematical model of the Ward–Leonard layout are as follows .

$$\frac{\Omega_y(s)}{V_f(s)} = \frac{K_g K_m N}{(L_f s + R_f)[(L_a s + R_a)(J_m^* s + B_m^*) + K_m K_b]}$$
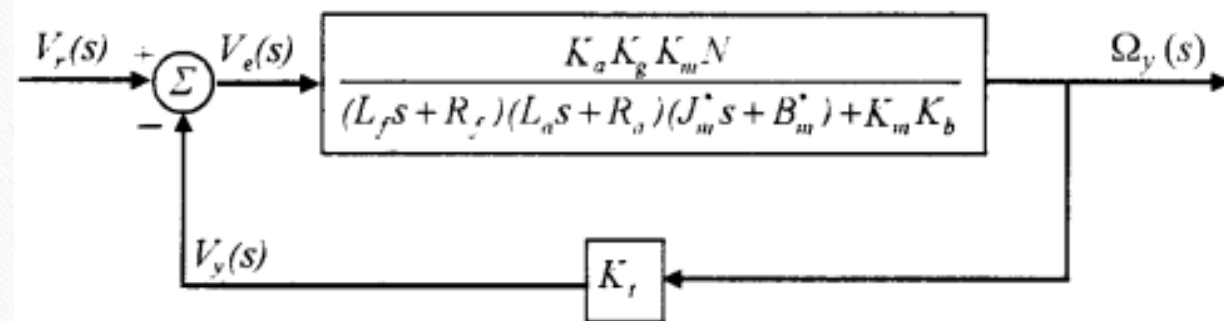
$$\frac{\Omega_y(s)}{v_e(s)} = \frac{K_a K_g K_m N}{(L_f s + R_f)[(L_a s + R_a)(J_m^* s + B_m^*) + K_m K_b]}$$



Analogy


- Force – voltage analogy

$$L \frac{di}{dt} + Ri + \frac{1}{C} \int i dt = e$$


In terms of the electric charge q , this last equation becomes

$$L \frac{d^2q}{dt^2} + R \frac{dq}{dt} + \frac{1}{C} q = e$$

Mechanical Systems	Electrical Systems
Force p (torque T)	Voltage e
Mass m (moment of inertia J)	Inductance L
Viscous-friction coefficient b	Resistance R
Spring constant k	Reciprocal of capacitance, $1/C$
Displacement x (angular displacement θ)	Charge q
Velocity \dot{x} (angular velocity $\dot{\theta}$)	Current i

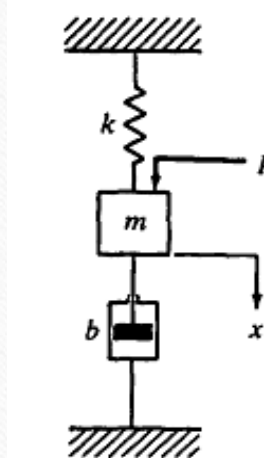
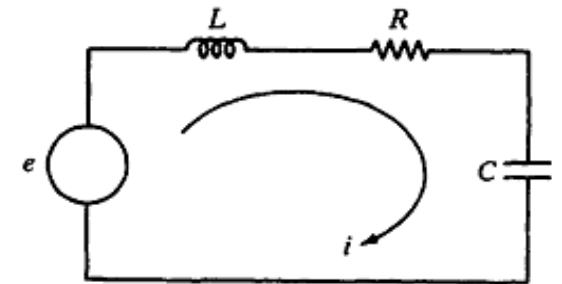
$$m \frac{d^2x}{dt^2} + b \frac{dx}{dt} + kx = p$$



$$L \frac{d^2q}{dt^2} + R \frac{dq}{dt} + \frac{1}{C} q = e$$

Analogy


- Force – current analogy

$$\frac{1}{L} \int e \, dt + \frac{e}{R} + C \frac{de}{dt} = i_s$$


In terms of the magnetic flux ψ , this last equation becomes

$$C \frac{d^2\psi}{dt^2} + \frac{1}{R} \frac{d\psi}{dt} + \frac{1}{L} \psi = i_s$$

Mechanical Systems	Electrical Systems
Force p (torque T)	Current i
Mass m (moment of inertia J)	Capacitance C
Viscous-friction coefficient b	Reciprocal of resistance, $1/R$
Spring constant k	Reciprocal of inductance, $1/L$
Displacement x (angular displacement θ)	Magnetic flux linkage ψ
Velocity \dot{x} (angular velocity $\dot{\theta}$)	Voltage e

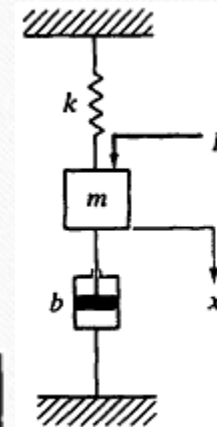
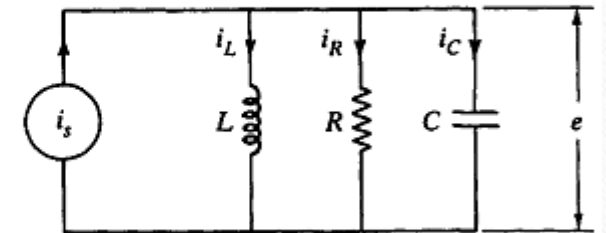
$$m \frac{d^2x}{dt^2} + b \frac{dx}{dt} + kx = p$$



$$C \frac{d^2\psi}{dt^2} + \frac{1}{R} \frac{d\psi}{dt} + \frac{1}{L} \psi = i_s$$

Model Examples

- Stepper motor

