

Benha University
Faculty of Engineering (at Shoubra)
Electrical Engineering Department
Preparatory year



Midterm Exam 'B'
Subject: Computer - ECE 001
Date: Thursday 31/03/2016
Duration: 1 hour
№ of Questions: 4 in 2 page(s)
Total Mark: 15

Attempt *all* the following questions:

Question 1:

(4 Marks)

Celsius to Fahrenheit Temperature Converter:

Write a complete C++ program that converts Celsius temperatures to Fahrenheit temperatures. The formula is as follows:

$$F = C \times 9/5 + 32$$

The program should ask the user to enter a temperature in Celsius, and then display the temperature converted to Fahrenheit.

```
#include <iostream>
using namespace std;
int main () {

float C, F;
cout << "Please enter a temp. in Celsius";
cin >> C;
F = (C * (9/5)) + 32;
cout << F ;
return 0;
}
```





Attempt *all* the following questions:

Question 2:

(4 Marks)

Determine the output of the following flowcharts:

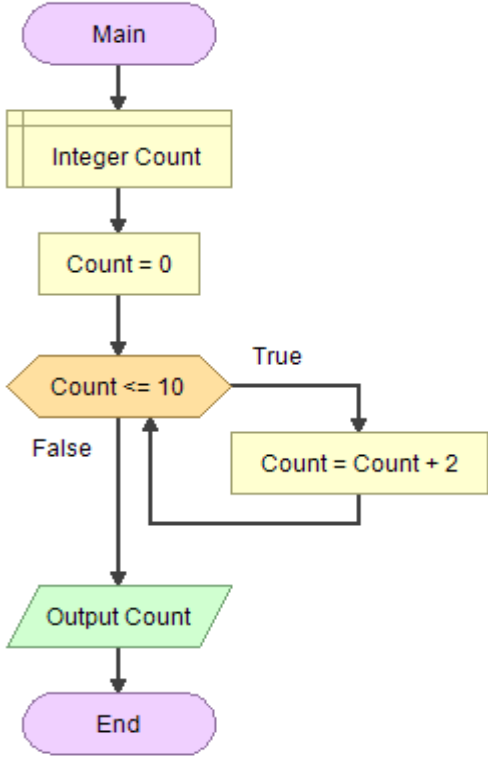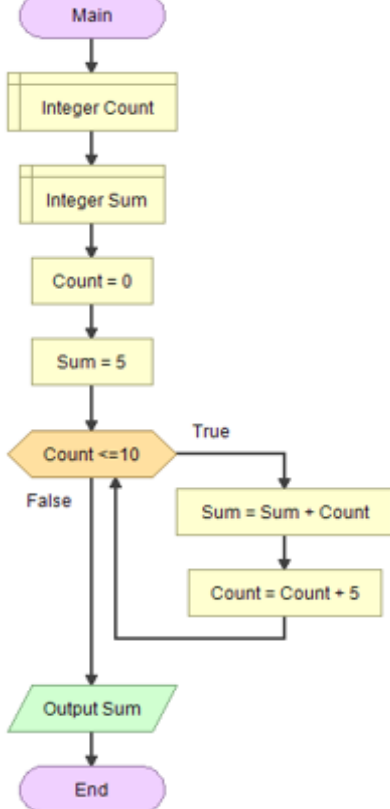a) (2 Marks)	b) (2 Marks)
 <pre> graph TD Main([Main]) --> Count[Integer Count] Count --> Init[Count = 0] Init --> Cond{Count <= 10} Cond -- True --> Add[Count = Count + 2] Add --> Cond Cond -- False --> Out[/Output Count/] Out --> End([End]) </pre>	 <pre> graph TD Main([Main]) --> Count[Integer Count] Count --> Sum[Integer Sum] Sum --> Init[Count = 0] Init --> Sum5[Sum = 5] Sum5 --> Cond{Count <= 10} Cond -- True --> AddSum[Sum = Sum + Count] AddSum --> AddCount[Count = Count + 5] AddCount --> Cond Cond -- False --> Out[/Output Sum/] Out --> End([End]) </pre>
<p>Answer</p> <p>12</p>	<p>Answer</p> <p>20</p>



Attempt *all* the following questions:

Question 3:

(3 Marks)


Choose the best answer:

1. The value $(101011)_2$ in a decimal system is
 (a) 43 (b) 42 (c) 44 (d) A4
2. The value $(245)_8$ in a decimal system is
 (a) 165 (b) 101100101 (c) 69 (d) A5
3. The value $(74)_{10}$ in a hexadecimal decimal system is
 (a) 104 (b) 740 (c) 4A (d) A4
4. A scanner is an example of a(n)
 (a) processing device (b) output device (c) storage device (d) input device
5. A touchscreen device is an example of a(n)
 (a) processing device (b) output device (c) storage device (d) input/output device
6. The last step in the machine cycle is
 (a) fetch (b) execute (c) decode (d) store

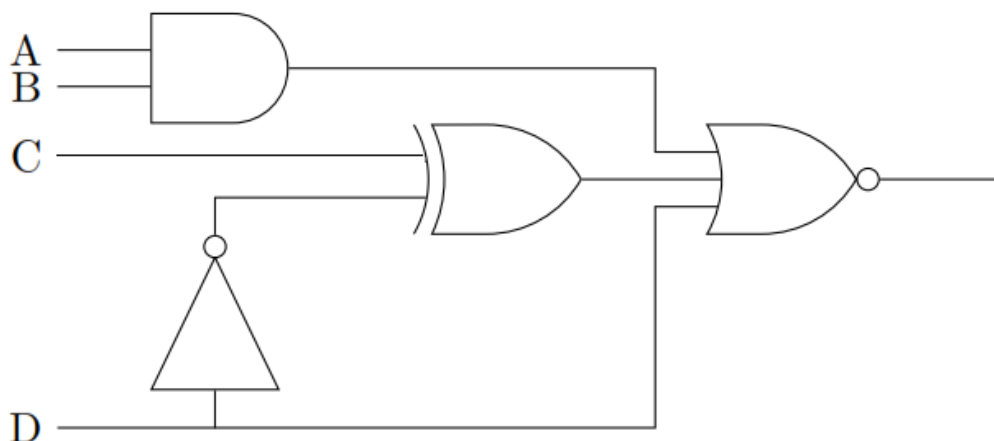Question 4:

(4 Marks)

State the Boolean expression and the truth table of the following logic circuit:



Benha University
Faculty of Engineering (at Shoubra)
Electrical Engineering Department
Preparatory year



Midterm Exam 'B'
Subject: Computer - ECE 001
Date: Thursday 31/03/2016
Duration: 1 hour
№ of Questions: 4 in 2 page(s)
Total Mark: 15

Attempt *all* the following questions:

$$\text{Output} = (A \cdot B + C \oplus D' + D)'$$

A	B	C	D	D'	A and B	Xor	Output
0	0	0	0	1	0	1	0
0	0	0	1	0	0	0	0
0	0	1	0	1	0	0	1
0	0	1	1	0	0	1	0
0	1	0	0	1	0	1	0
0	1	0	1	0	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	0	0	1	0
1	0	0	0	1	0	1	0
1	0	0	1	0	0	0	0
1	0	1	0	1	0	0	1
1	0	1	1	0	0	1	0
1	1	0	0	1	1	1	0
1	1	0	1	0	1	0	0
1	1	1	0	1	1	0	1
1	1	1	1	0	1	1	0

Good Luck
Dr. Shady Yehia Elmashad
Dr. Ahmed Bayoumi