Benha University
Faculty of Engineering (at Shoubra)
Electrical Engineering Department
Preparatory year



Midterm Exam 'B'

**Subject:** Computer - ECE 001 **Date:** Thursday 31/03/2016

**Duration:** 1 hour

**№ of Questions:** 4 in 2 page(s)

**Total Mark: 15** 

Attempt *all* the following questions:

Question 1: (4 Marks)

## Celsius to Fahrenheit Temperature Converter:


Write a complete C++ program that converts Celsius temperatures to Fahrenheit temperatures. The formula is as follows:

$$F = C \times 9/5 + 32$$

The program should ask the user to enter a temperature in Celsius, and then display the temperature converted to Fahrenheit.

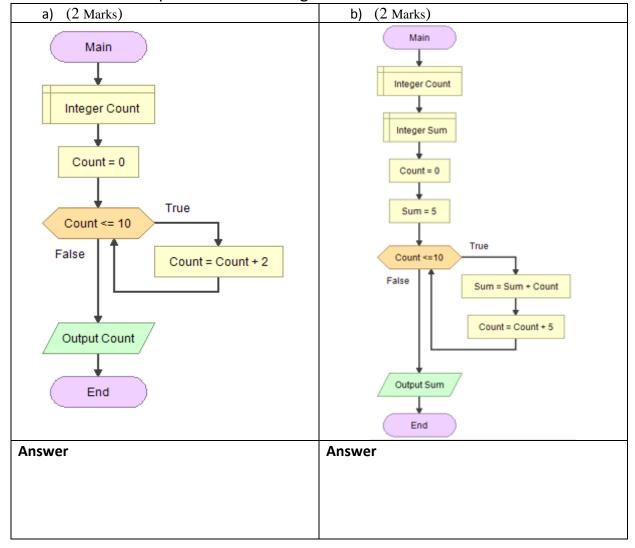Question 2: (4 Marks)

Determine the output of the following flowcharts:



Benha University
Faculty of Engineering (at Shoubra)
Electrical Engineering Department
Preparatory year



Midterm Exam 'B'

**Subject:** Computer - ECE 001 **Date:** Thursday 31/03/2016

**Duration:** 1 hour

**№ of Questions:** 4 in 2 page(s)

**Total Mark: 15** 

Attempt *all* the following questions:

Question 3: (3 Marks)

## **Choose the best answer:**

- 1. The value (101011)<sub>2</sub> in a decimal system is
- (a) 43
- (b) 42

(c) 44

(d) A4


- 2. The value (245)<sub>8</sub> in a decimal system is
- (a) 165
- (b) 101100101
- (c) 69

- (d) A5
- 3. The value (74)<sub>10</sub> in a hexadecimal decimal system is
- (a) 104
- (b) 740
- (c) 4A

- (d) A4
- 4. A scanner is an example of a(n) ......
- (a) processing device
- (b) output device (c) storage device (d) input device
- 5. A touchscreen device is an example of a(n) ......
- (a)processing device (b)output device (c)storage device (d)input/output device
- 6. The last step in the machine cycle is ......
- (a) fetch
- (b) execute
- (c) decode
- (d) store
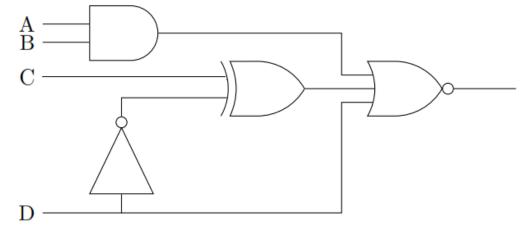
## Question 4: (4 Marks)

State the Boolean expression and the truth table of the following logic circuit:



Good Luck Dr.Shady Yehia Elmashad Dr.Ahmed Bayoumi